
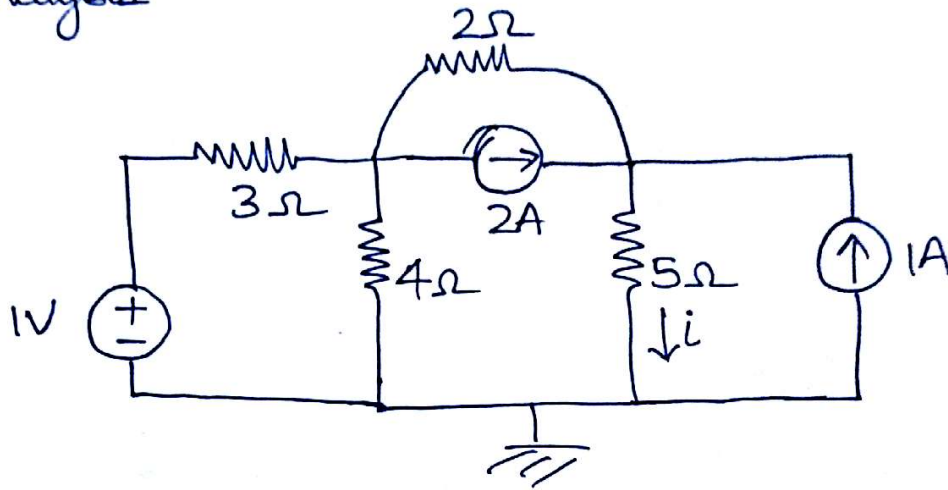


# Tutorial-1

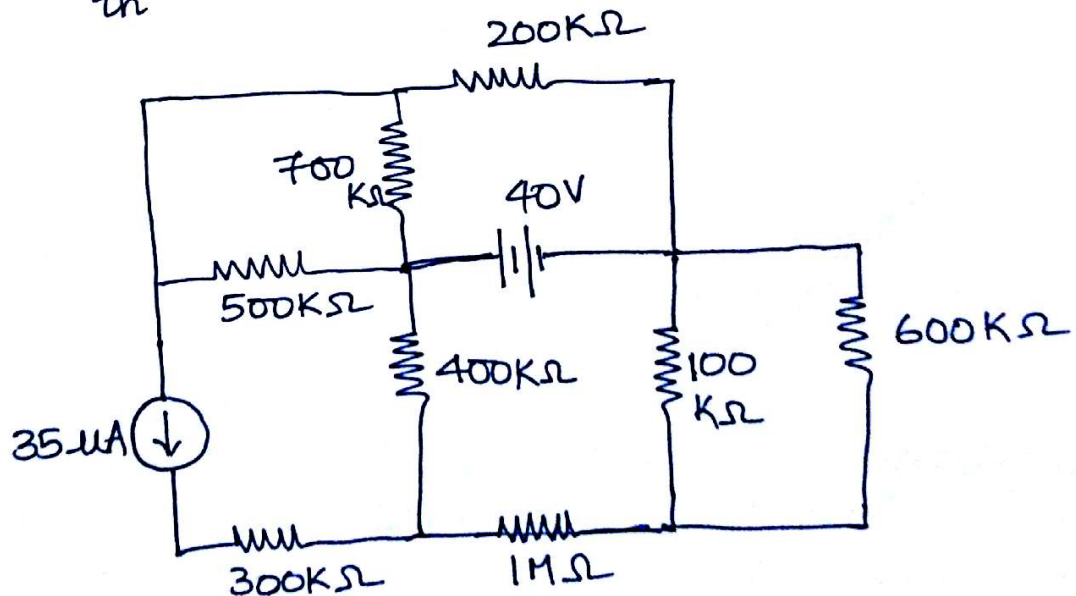- 1) Determine the current  $I$  through the  $5\Omega$  resistor using node analysis



- 2) Find the Thevenin Equivalent circuit with respect to the ~~100K~~  $100\text{K}\Omega$  resistor. You must use Superposition to find  $V_{th}$ .



3) Find the current through  $4\Omega$  resistor using mesh analysis.



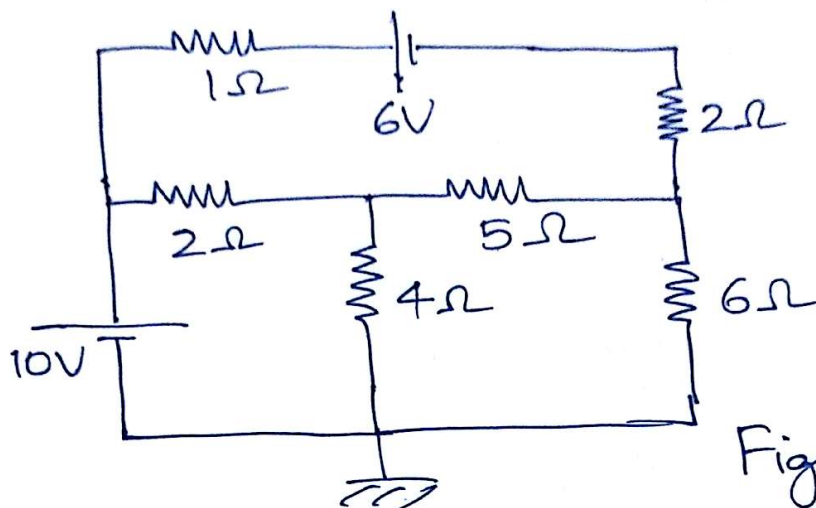


Figure 3

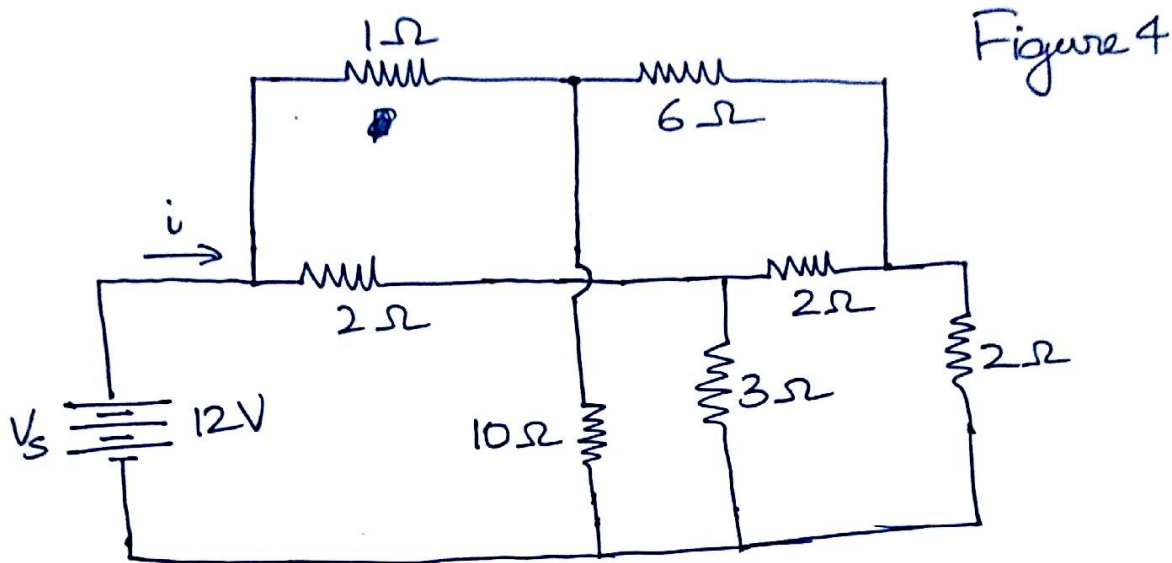4) The nonseries-parallel circuit shown in Figure 4 is known as a twin T-network. Determine the resistance  $R_{eq} = \frac{V_s}{I}$  loading the battery.



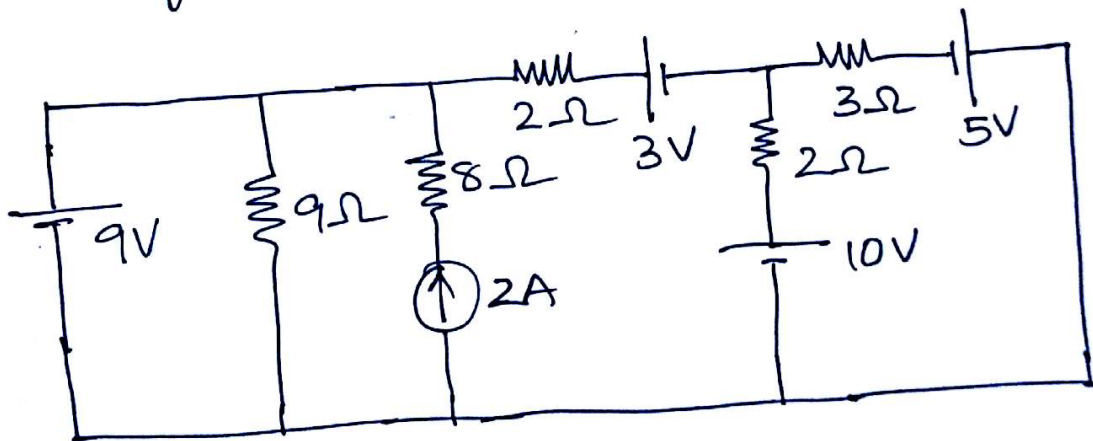5) In the circuit of Figure 5, find the Thevenin equivalent circuit existing between the terminals of 3Ω resistor.



b) Also find the power dissipated across 3Ω.