

## Tutorial 9

### JFET

Pinch-off conditions

$$\textcircled{1} \quad \text{For } V_{GS} \geq 0V \longrightarrow V_{GD} = V_{GS} - V_{DS} = 0 - V_{DS} = V_p$$

(Remember  $V_p$  is a negative number)

if the channel is @ pinch off, then

$$V_{DS} = -V_p$$

\textcircled{2} For  $V_{GS} < 0V$

channel is pinched off when

$$V_{GD} = V_{GS} - V_{DS}$$

↳ the value of  $V_{GD}$  when  
this condition is satisfied  
is  $V_p$

$$\text{Thus, } V_{GD} = V_{GS} - V_{DS} = V_p$$


$$V_{DS} = V_{GS} - V_p$$

$I_{DSS}$  ← saturation current value for  $V_{GS} = 0V$ .

$$i_D = I_{DSS} \frac{2I_{DSS}}{-V_p} \left(1 - \frac{V_{GS}}{V_p}\right) V_{DS} \quad \leftarrow \text{ohmic region}$$

$$i_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2 \quad \leftarrow \text{for active region}$$

Ex 8.1

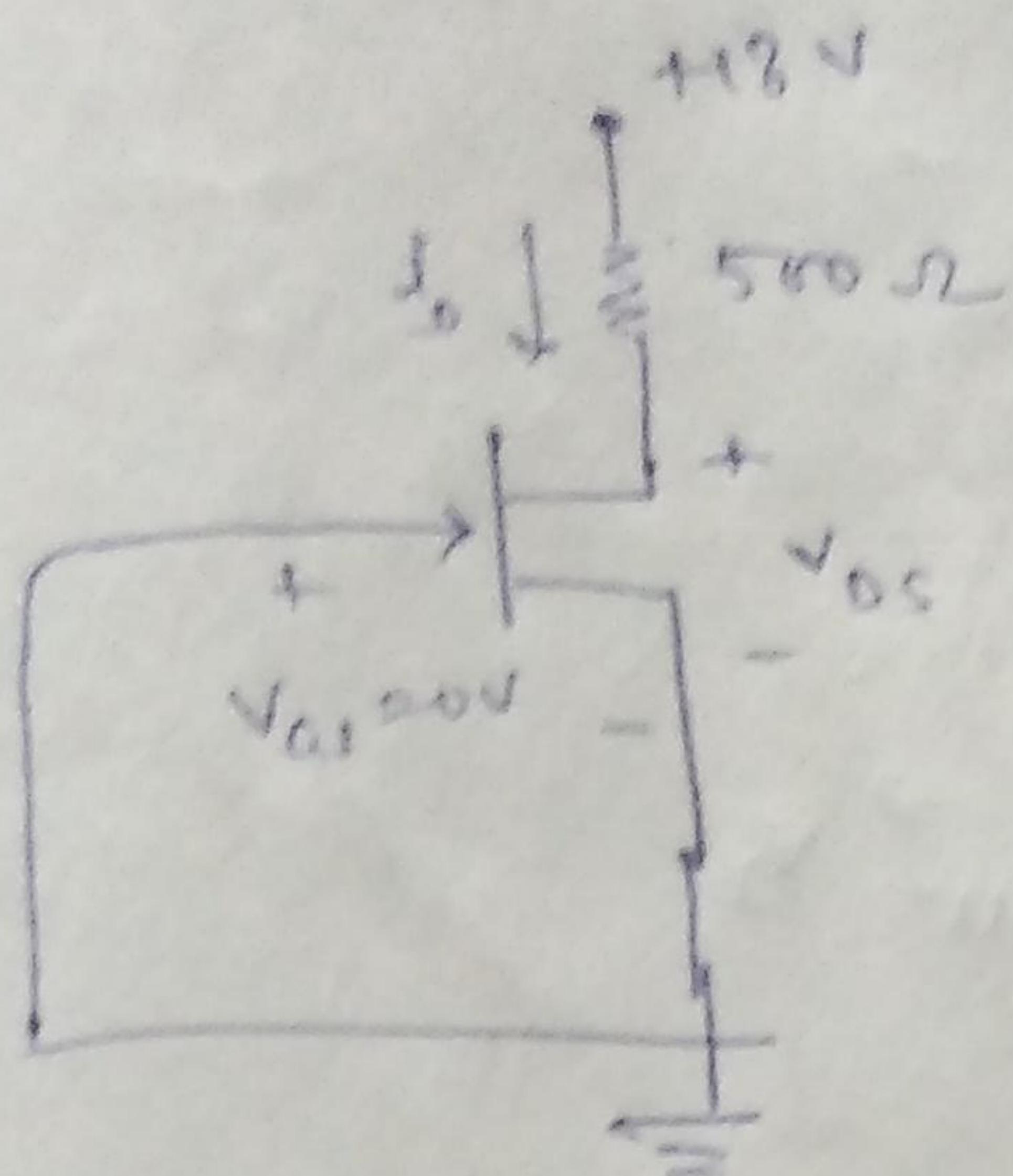

By drain law

$$I_D = \frac{18 - V_{DS}}{500} \quad \text{---(1)}$$


Assuming JFET is in active region, then

$$\begin{aligned} I_D &= I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2 \\ &= 8 \left(1 - \frac{0}{(-4)}\right)^2 = 8 \text{ mA} \end{aligned}$$

Substituting this  $I_D$  in eq. 1 to get  $V_{DS}$

$$I_D = \frac{18 - V_{DS}}{500} = 8 \text{ mA}$$
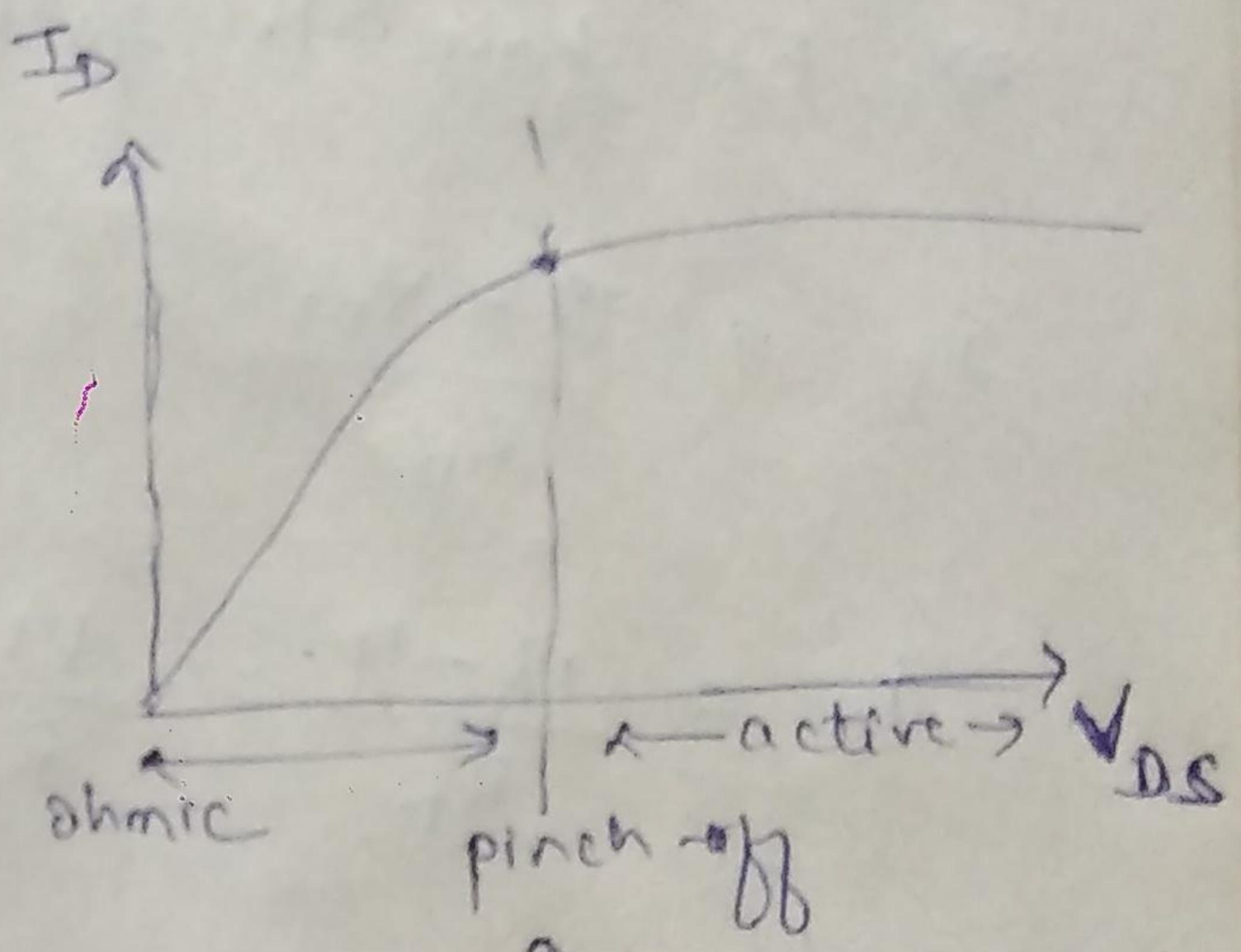
$$\Rightarrow V_{DS} = 14 \text{ volt} =$$



So below +4 volt it is  
ohmic region

and above +4 volt it  
is active region.


As we are getting  $V_{DS}$  at 14 volt -

$\Rightarrow$  JFET is in active region

$$-V_p = -(-4) = +4 \text{ volt}$$

This was our initial assumption. So now our initial assumption has been proved correct.

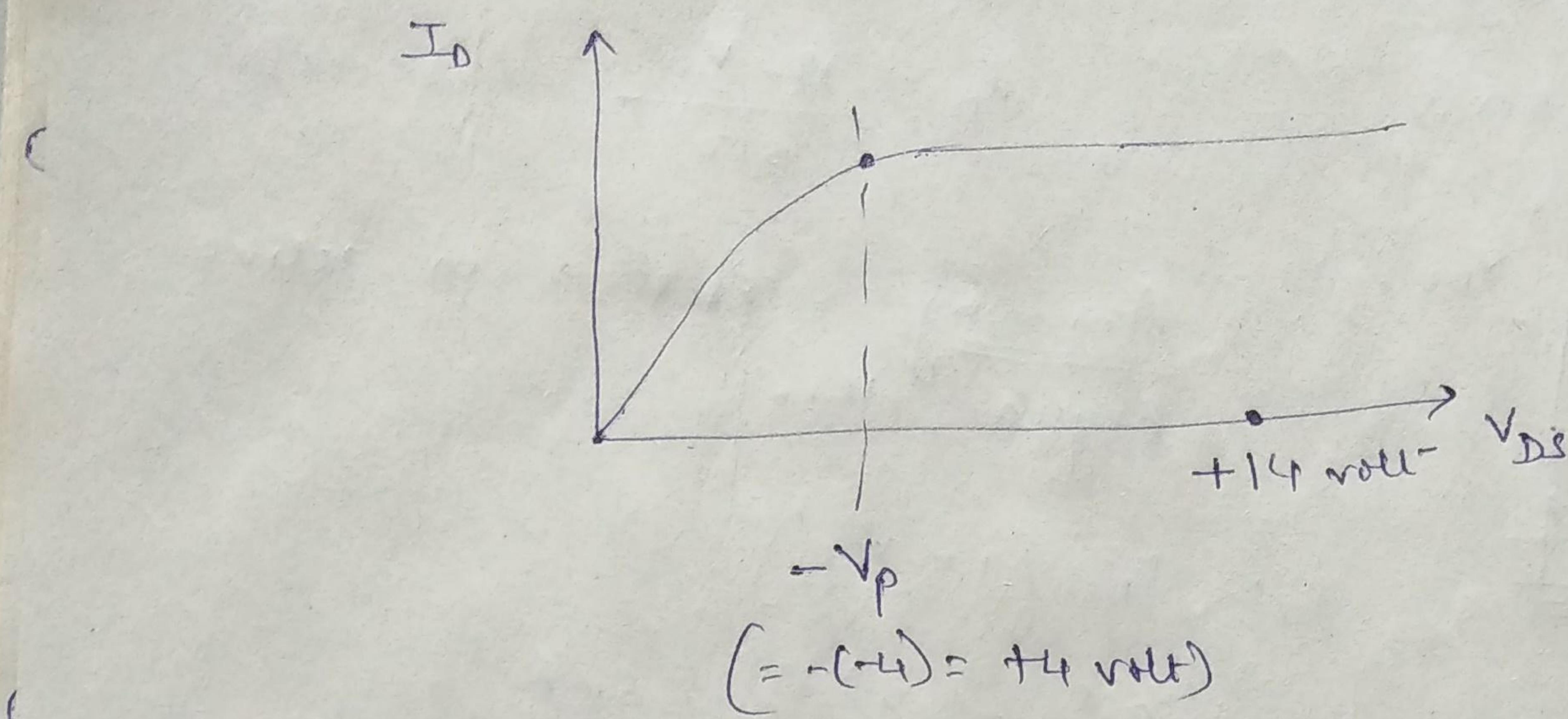Q.1 tutorial - extension of Ex 8.1 m Bobrow




So observe that  $R_D = 500\Omega$  is giving  $V_{DS}$  of +14 volt -  
But the question is asking for  $R_D$ , when ~~the~~ will  
be at pinch off.

⇒ We have to find  $R_D$  when  $V_{DS} = 4$  volt -

$$i_D = \frac{18 - V_{DS}}{R_D}$$
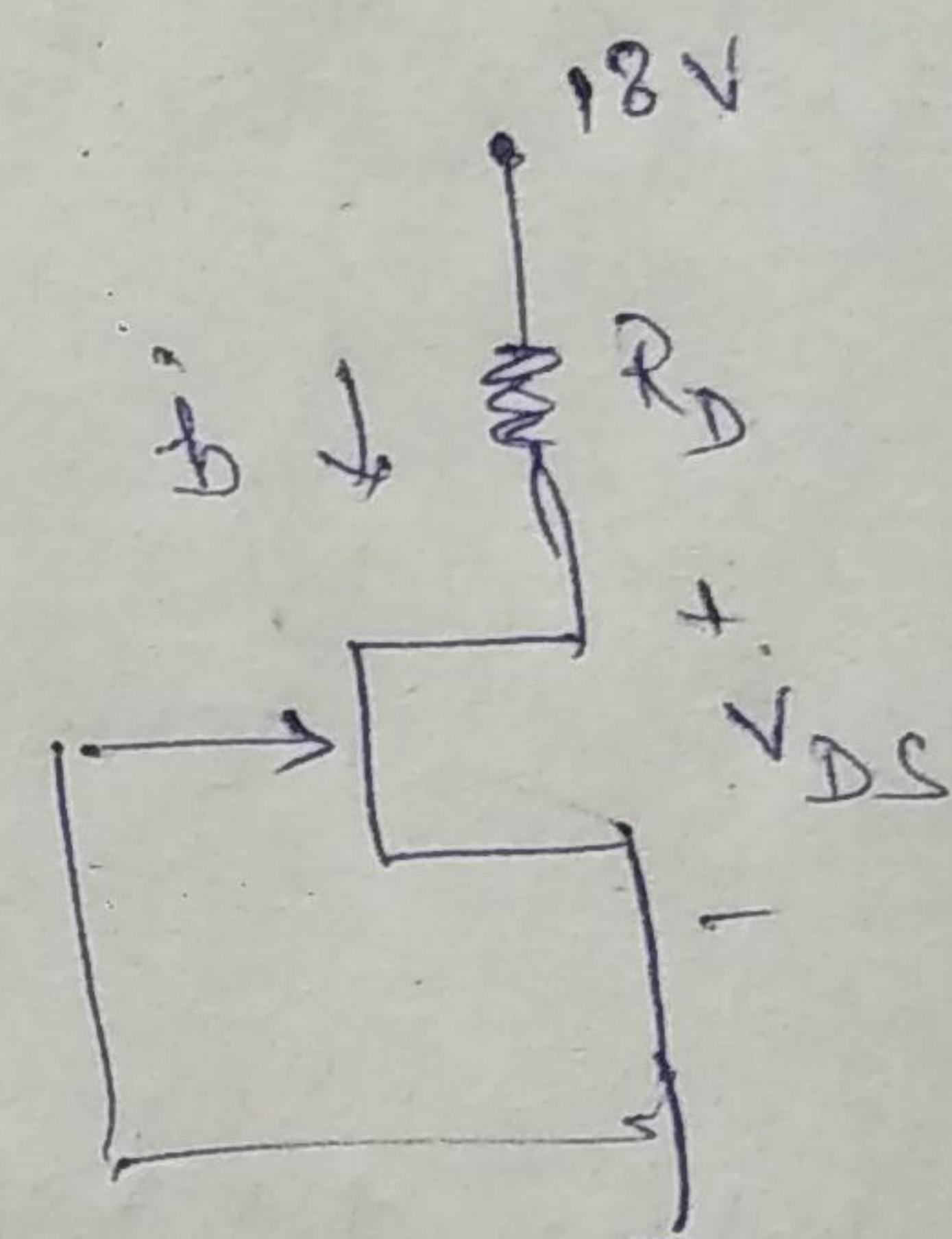
$$i_D = \frac{18 - 4}{R_D} = \frac{14}{R_D}$$



at pinch off, we can use current eq. for active region -

$$\begin{aligned} i_D &= I_{DSS} \left( 1 - \frac{V_{GS}}{V_p} \right)^2 \\ &= 8m \left( 1 - \frac{0}{V_p} \right)^2 = 8mA \end{aligned}$$

$$i_D = \frac{14}{R_D} \Rightarrow R_D = \frac{14}{8m} = \frac{14 \times 10^3}{8} = \underline{\underline{1.75 k\Omega}}$$

## Q.2 tutorial


- Ex 2.2 Bobelow

Here source and gate are not at same potential.


$$V_G = 0$$

$$V_S \neq 0 \leftarrow \text{not equal to zero}$$
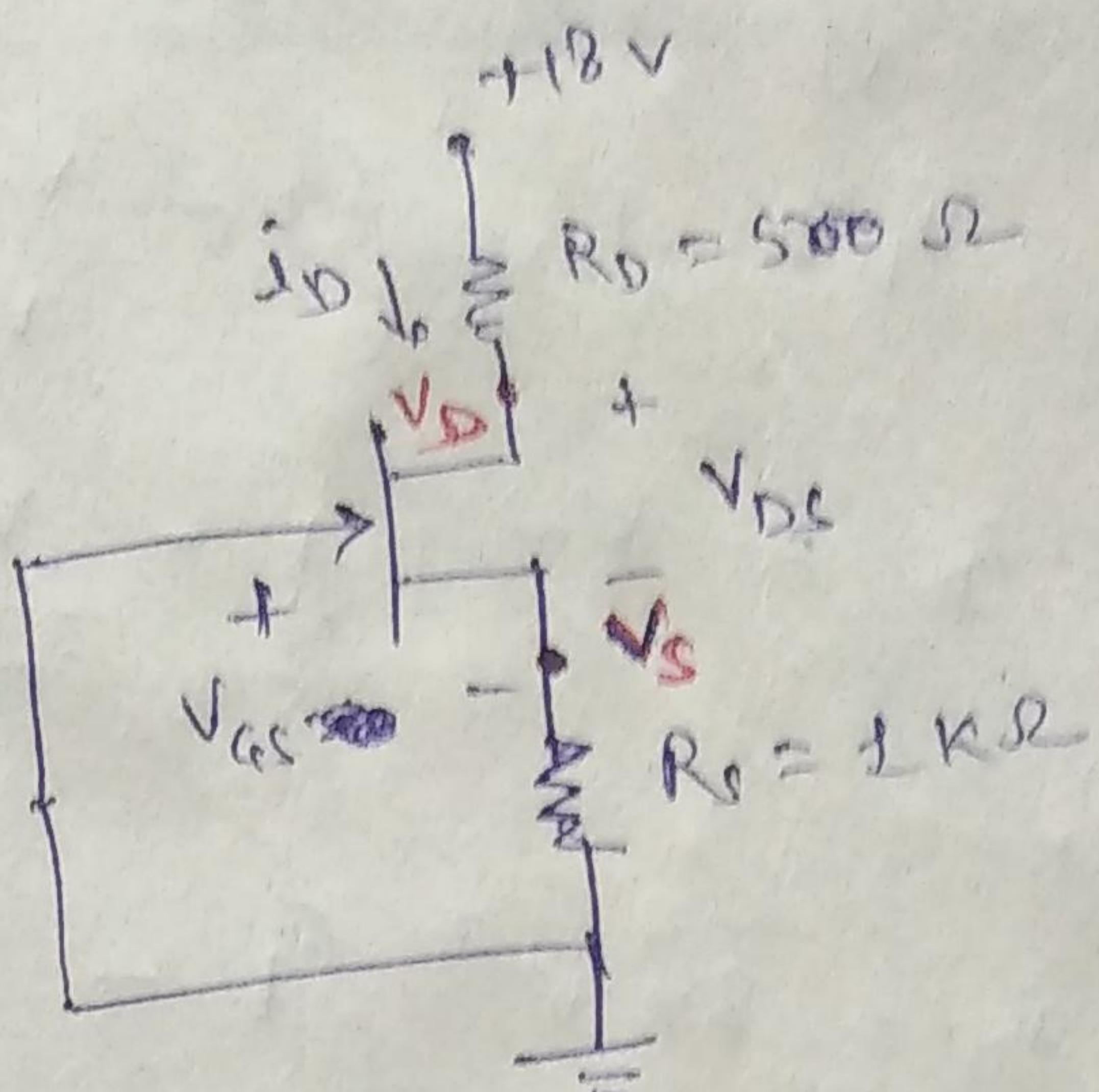
$$\hookrightarrow V_S = \text{drop across } R_S$$



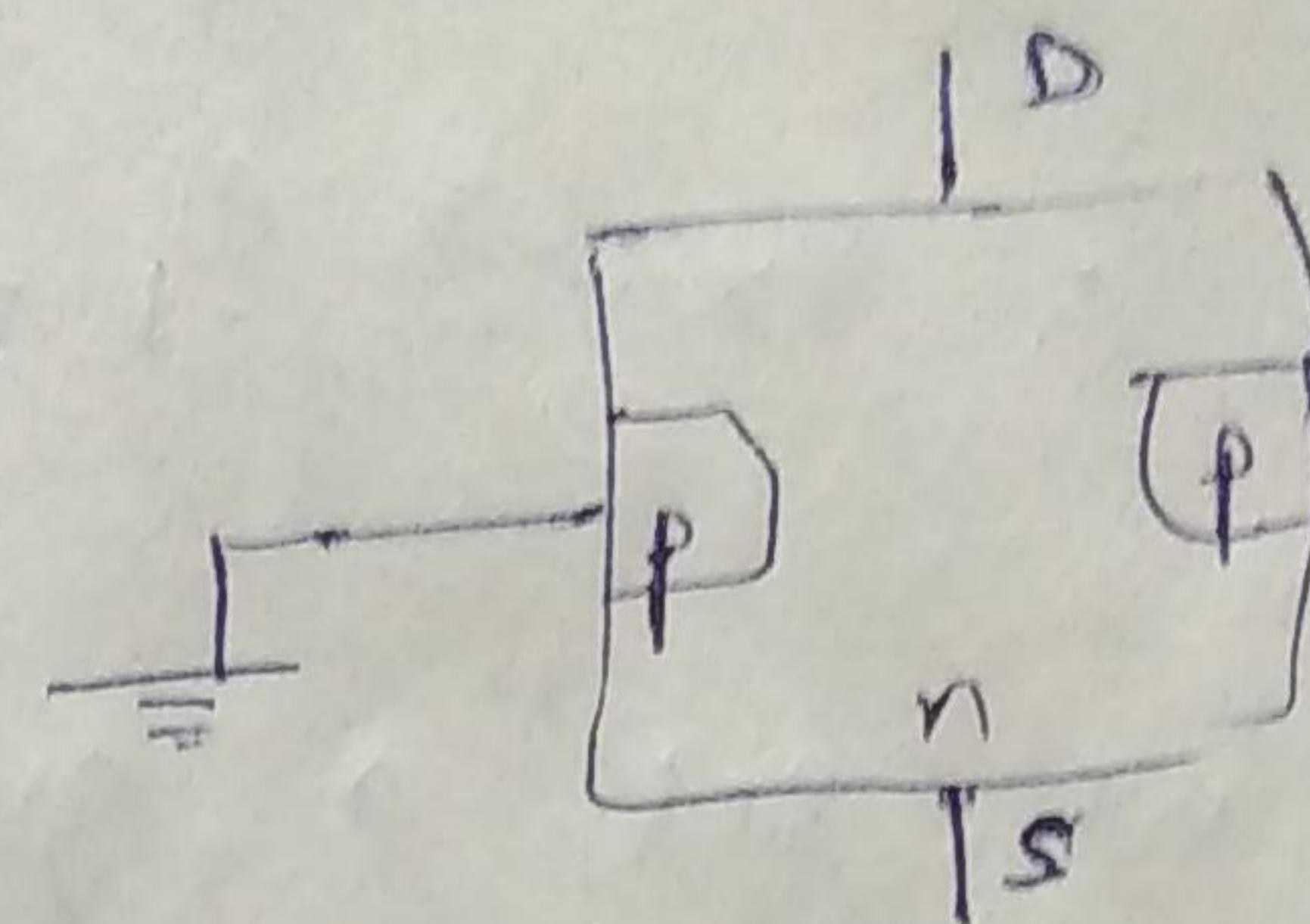Assuming that gate is reverse biased.  
 $\Rightarrow V_{GS} \leq 0V$



This is a pretty valid assumption — because if you see the top loop — the top node is at +18 volt and bottom at 0V — so every point in b/w these two nodes will have a voltage b/w +18 volt and 0 volt ~~even~~

$\Rightarrow V_S$  will be a positive value

$$\Rightarrow V_{GS} = V_G - V_S = 0 - V_S = -V_S$$

$\Rightarrow V_{GS} \leq 0V$  (we only know  $V_{GS} \leq 0$ , we don't know the exact value.)

$$i_D = \frac{18 - V_D}{500}$$

or

$$i_D = \frac{V_S}{1000}$$

$$\Rightarrow i_D = \frac{-V_{GS}}{1000}$$

$$\left. \begin{array}{l} V_{GS} = -V_S \\ V_S = -V_{GS} \end{array} \right\}$$

$$\Rightarrow V_{GS} = -1000 i_D$$

Assuming that JFET is in active region, then

$$i_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$\Rightarrow i_D = 8 \text{ mA} \left(1 - \frac{V_{GS}}{-4}\right)^2 = 8 \times 10^{-3} \left(1 - \frac{V_{GS}}{-4}\right)^2$$

$$\Rightarrow i_D = 8 \times 10^{-3} \left(1 - \frac{-1000 i_D}{-4}\right)^2$$

$$i_D = 8 \times 10^{-3} \left(1 - \frac{1000 i_D}{4}\right)^2$$

So we get a quadratic in  $i_D$  —

$$i_D^2 - (10 \times 10^{-3}) i_D + 16 \times 10^{-6} = 0$$

The solutions to this equation are —

$$i_{D_1} = 2 \times 10^{-3} \text{ Amp} \quad i_{D_2} = 8 \times 10^{-3} \text{ Amp}$$

But only one value of current can exist in the circuit. So which is the correct value?

→ Observe,  $i_{D_2} = 8 \text{ mA} = I_{DSS}$

$$\text{But } i_D = I_{DSS} \Rightarrow V_{GS} = 0 \text{ V}$$

But in our case  $V_{GS} < 0$

$\therefore i_D = I_{DSS}$  can not be the answer

Then,  $i_D = i_{D_1} = 2 \text{ mA}$

Book thinks —  
 $V_{GS} \leq 0$

But by our previous reasoning, we can write



$$V_{GS} < 0$$

→ Book approach (more analytical)

We assumed that device is in active region.

Case 1  $i_D = 8 \text{ mA}$
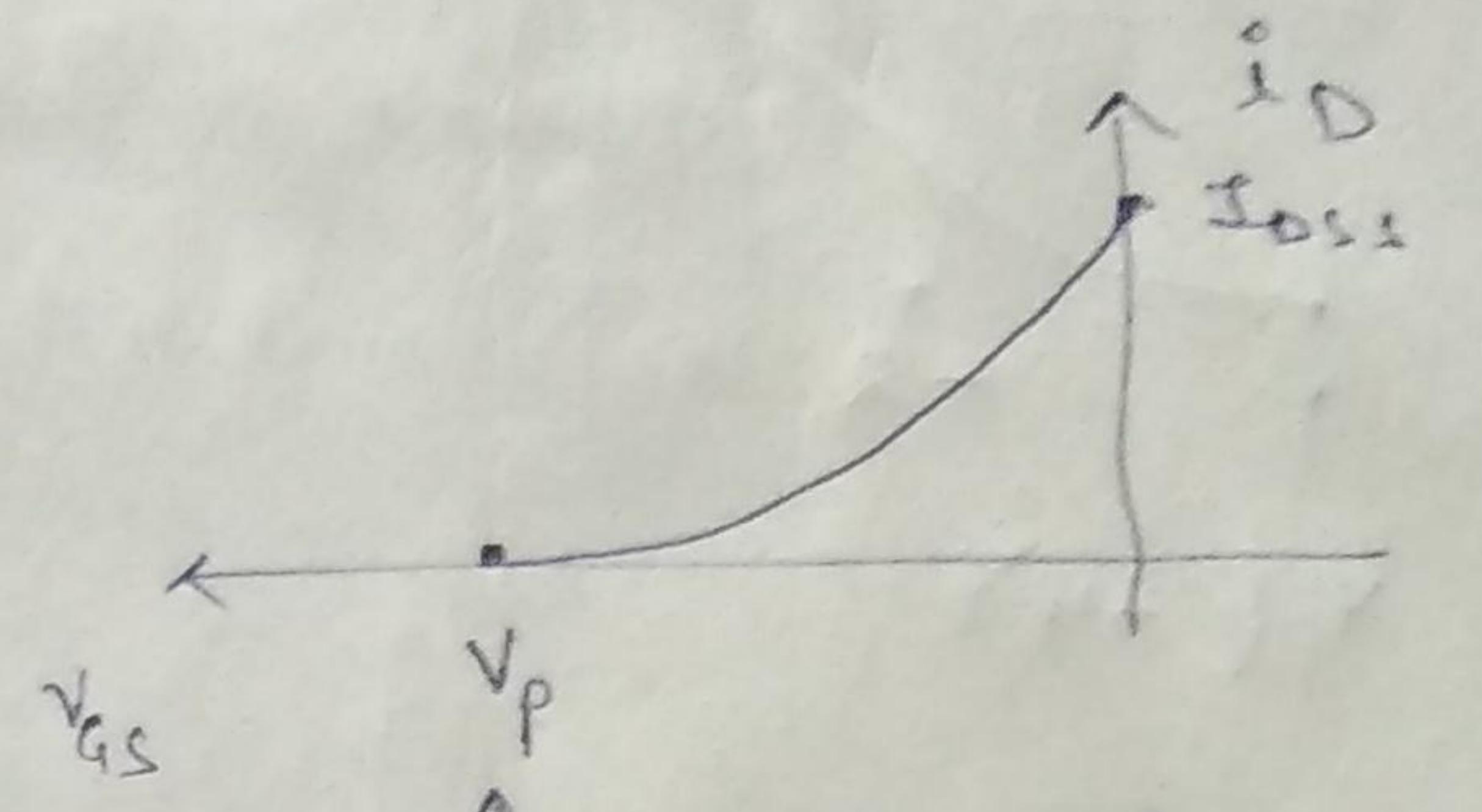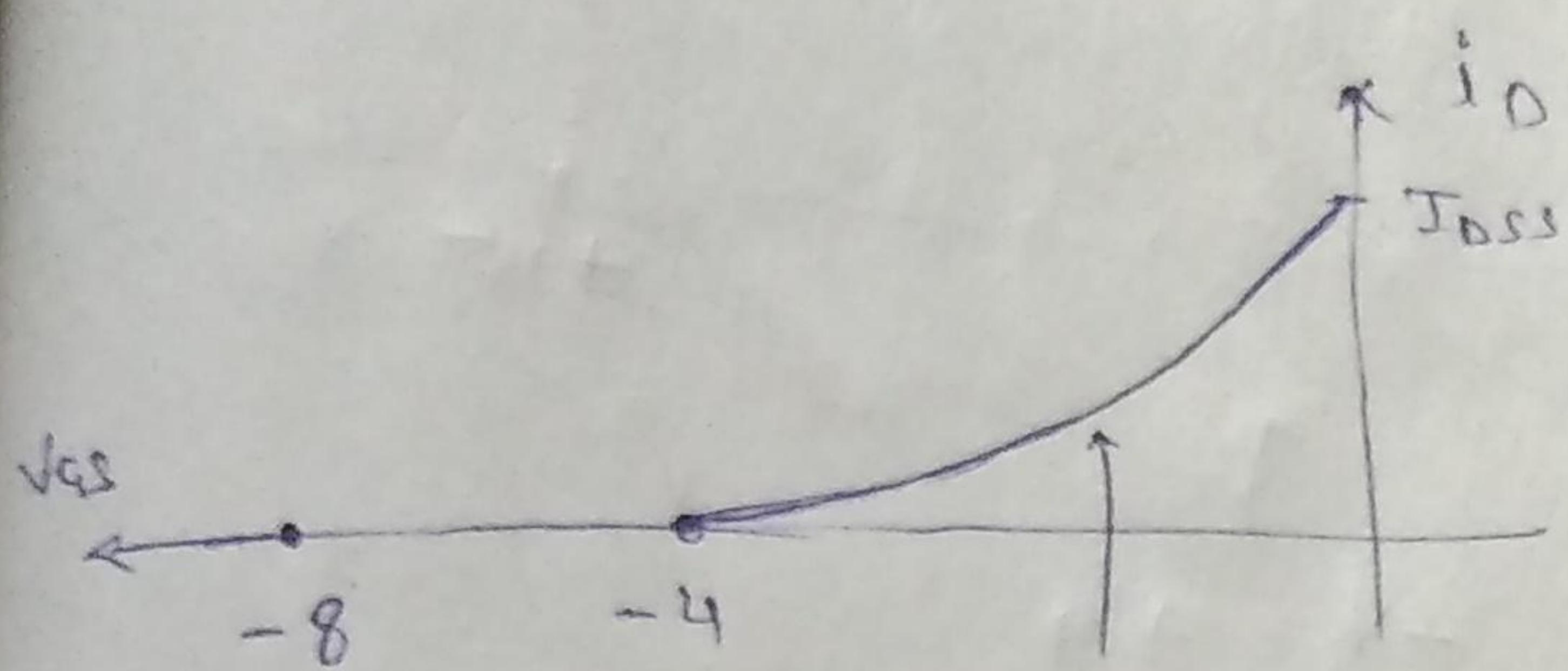
$$V_{GS} = -1000 i_D = -1000 (8 \times 10^{-3}) = -8 \text{ volt}$$



$$\text{plot of } i_D = I_{OSS} \left( 1 - \frac{V_{GS}}{V_p} \right)^2$$

$i_D(\text{active})$

negative value  
= (-4 volt)

As  $V_{GS} = -8 \text{ volt}$  is less than pinch off  
⇒ device is not in active region.

So here our assumption is contradicted.

Case 2  $i_D = 2 \text{ mA}$

$$V_{GS} = -1000 i_D = -1000 (2 \text{ mA}) = -2 \text{ volt}$$

$$-2 \text{ volt} > V_p$$

↑  
This supports that device is in active region.

Hence taking  $i_D = 2 \text{ mA}$  as the correct answer and moving forward.

$$i_D = 2 \text{ mA} \quad V_{GS} = -2 \text{ volt}$$

Writing KVL in top loop



$$18 - i_D R_D - V_{DS} - i_D R_L = 0$$

$$\Rightarrow 18 - 2 \times 10^{-3} \times 500 - V_{DS} - 2 \times 10^{-3} \times 1000 = 0 \Rightarrow V_{DS} = 15 \text{ volt}$$

$$i_D = 2 \text{ mA}$$

$$V_{GS} = -2 \text{ volt}$$

$$V_{DS} = 15 \text{ volt}$$

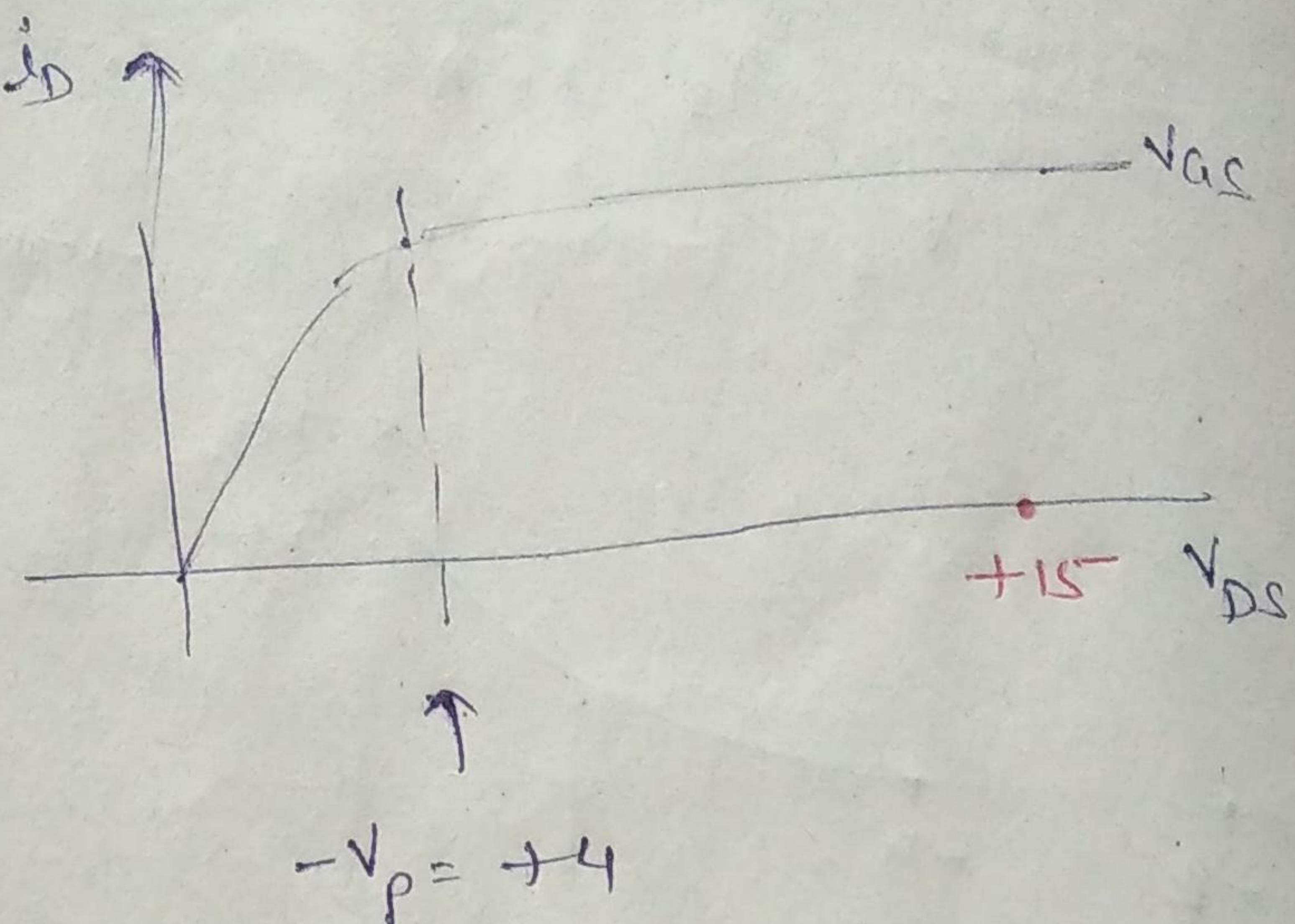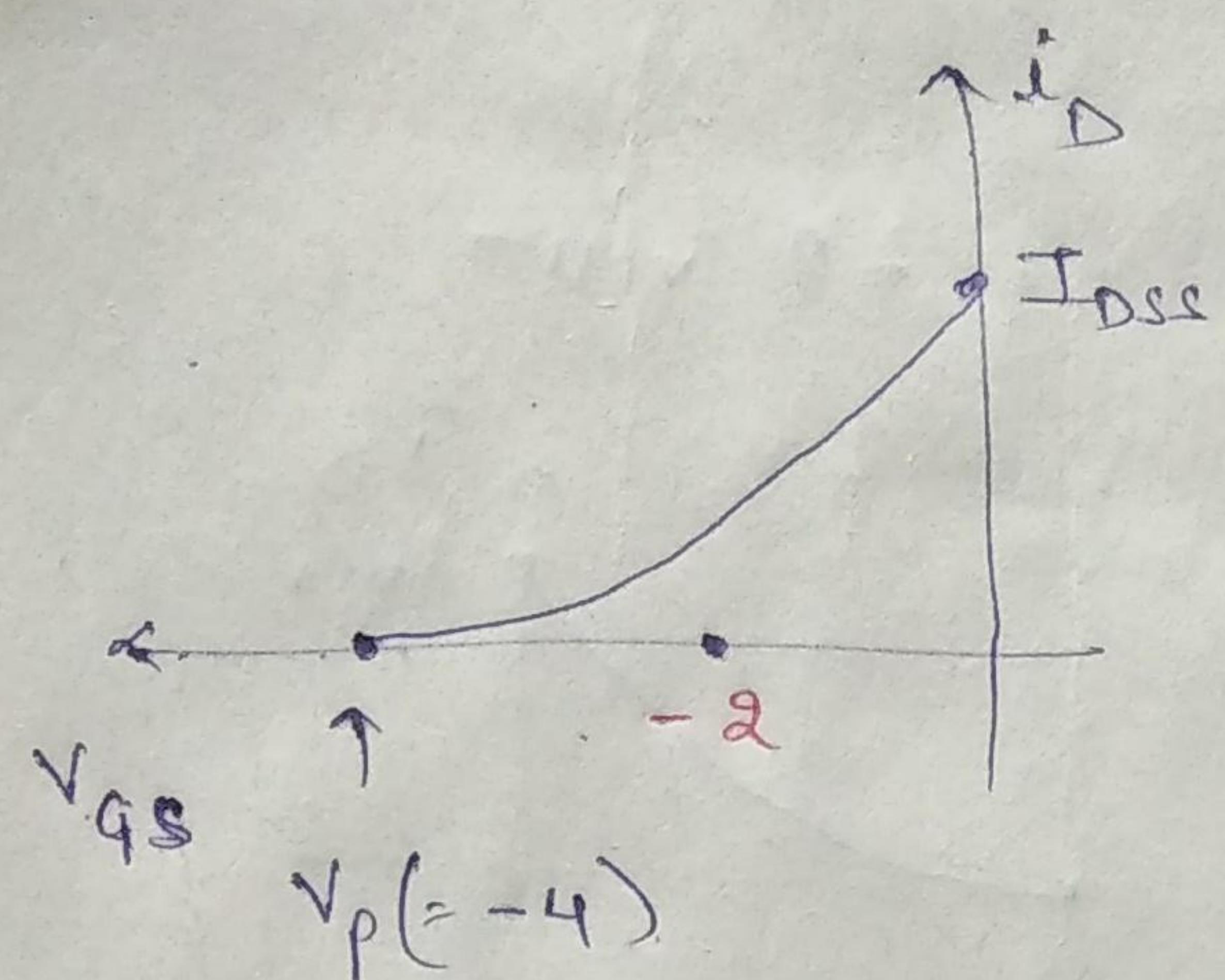

All these values are coherent, proving that device is in active region.

### Depletion MOSFET

depletion mode  
( $V_{GS} = \text{-ive}$ )

enhancement mode  
( $V_{GS} = \text{+ve}$ )


### Q3 tutorial - Ex 8.3 Bobrow

Given an n type depletion MOSFET

Given:  $I_{DSS} = 8 \text{ mA}$

$$V_p = -2 \text{ volt}$$

$$V_{GS} = 1 \text{ volt}$$

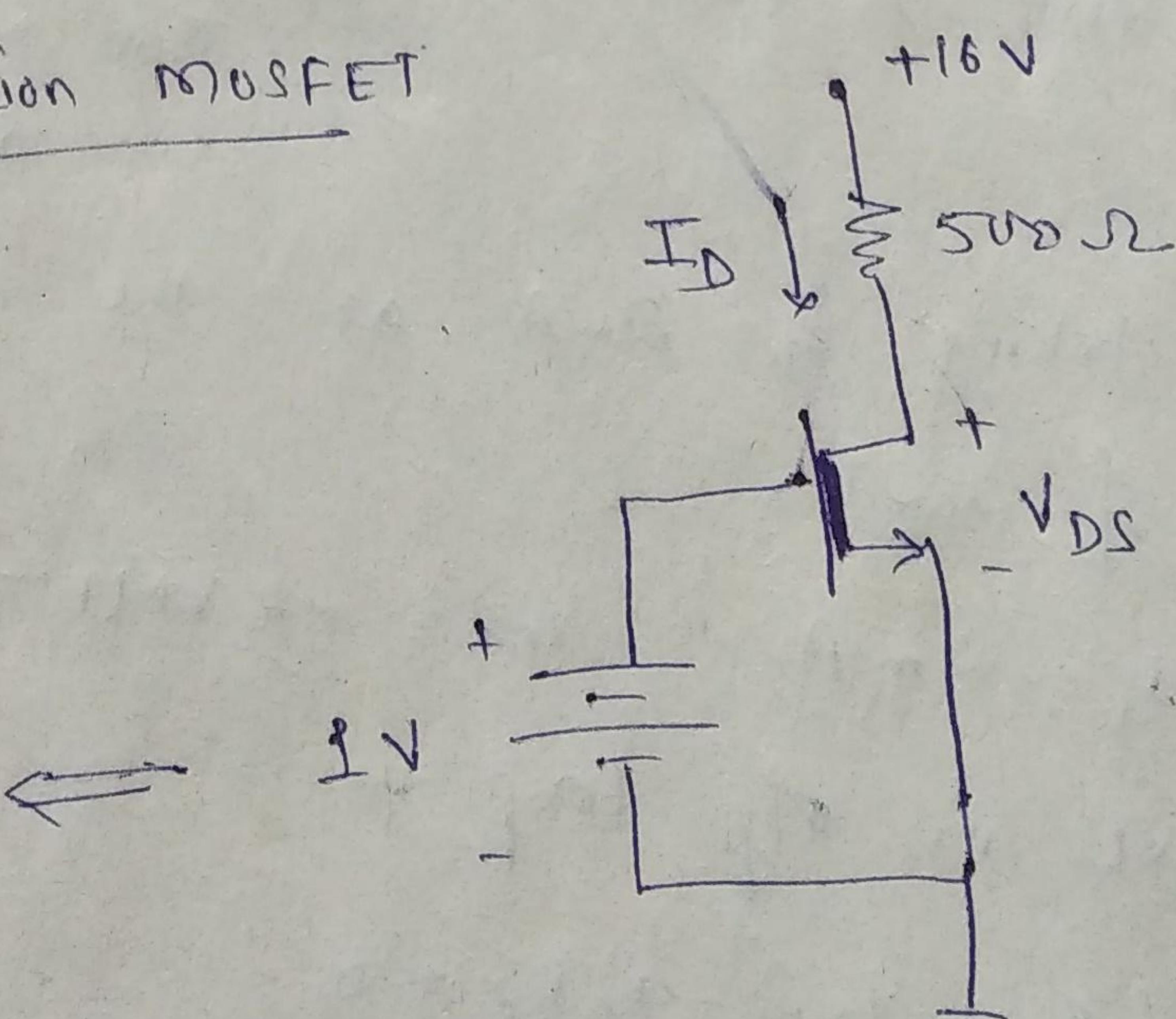

Writing KVL in top loop

$$+16 - i_D R_D - v_{DS} = 0$$

$$v_{DS} = 16 - i_D (500)$$

Assuming device is in active region, then

$$\begin{aligned} i_D &= I_{DSS} \left(1 - \frac{v_{GS}}{V_P}\right)^2 \\ &= (8 \times 10^{-3}) \left(1 - \frac{1}{-2}\right)^2 = 18 \text{ mA} \end{aligned}$$

$$\Rightarrow v_{DS} = 16 - (18)(500) = \underline{\underline{7 \text{ volt}}}$$

$$\begin{array}{c|c} v_{DS} & \frac{v_{GS} - V_P}{1 - (-2)} \\ \hline 7 & 3 \end{array}$$

$$\Rightarrow \boxed{v_{DS} > v_{GS} - V_P} \quad \leftarrow \text{condition for depletion MOS to be in active region}$$

⇒ MOSFET is in active region

⇒ ~~thus our assumption is validated.~~

So,

$$v_{GS} = 1 \text{ volt} \quad i_D = 18 \text{ mA} \quad v_{DS} = 7 \text{ volt}$$

$$\boxed{v_{DS} > v_{GS} - V_P \text{ and } (v_{GS} > V_P)} \quad \leftarrow \text{condition for depletion MOS to be in active region}$$

$$\boxed{v_{DS} < v_{GS} - V_P \text{ and } (v_{GS} > V_P)} \quad \leftarrow \text{condition for depletion MOS to be in ohmic region.}$$

If  $\boxed{v_{GS} < V_P}$  — device is in cut off.

→ if  $R_D$  is  $750 \Omega$

again assuming device is in active region then

$$i_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_p} \right)^2 = 18 \text{ mA}$$

$$V_{DS} = 16 - i_D (750) = 16 - 18 \times 10^{-3} \times 750 = 2.5 \text{ volt}$$

$$\left. \begin{array}{l} V_{DS} \\ 2.5 \end{array} \right\} \quad \left. \begin{array}{l} V_{GS} - V_p \\ 1 - (-2) = 3 \end{array} \right.$$

$\Rightarrow V_{DS} < V_{GS} - V_p$  ← condition for ohmic region  
But we assumed that device is in active region.

Thus our assumption is contradicted.

So let's start all over again, by assuming that device is in ohmic region. —

$$i_D = \underline{I_{DSS}} \left[ 2 \left( 1 - \frac{V_{GS}}{V_p} \right) \frac{V_{DS}}{(-V_p)} - \left( \frac{V_{DS}}{V_p} \right)^2 \right]$$

$$i_D = (8 \times 10^{-3}) \left[ 2 \left( 1 - \frac{1}{-2} \right) \frac{V_{DS}}{2} - \left( \frac{V_{DS}}{-2} \right)^2 \right]$$

Also  $i_D = \frac{16 - V_{DS}}{750}$

$$\therefore 8 \times 10^{-3} \left[ 2 \left( 1 - \frac{1}{-2} \right) \frac{V_{DS}}{2} - \left( \frac{V_{DS}}{-2} \right)^2 \right] = \frac{16 - V_{DS}}{750}$$

Here we get a quadratic equation -

$$3V_{DS}^2 - 20V_{DS} + 32 = 0$$

Solve -  $V_{DS_1} = \frac{8}{3} V$        $V_{DS_2} = 4 V$

$$\begin{array}{c|c} V_{DS} & \frac{V_{GS} - V_P}{3} \\ \hline 8/3 & \end{array}$$

$$\frac{8}{3} < 3$$

$$V_{DS} < V_{GS} - V_P$$

⇒ ohmic region  
consistent with the  
assumption ✓

$$\begin{array}{c|c} V_{DS} & \frac{V_{GS} - V_P}{3} \\ \hline 4 & \\ 4 & \end{array}$$

$$V_{DS} > V_{GS} - V_P$$

condit<sup>n</sup> for active region

contradict the assumpt<sup>n</sup>

$$i_D = \frac{16 - V_{DS}}{750} = \frac{16 - 8/3}{500}$$

$$= 17.8 \text{ mA}$$