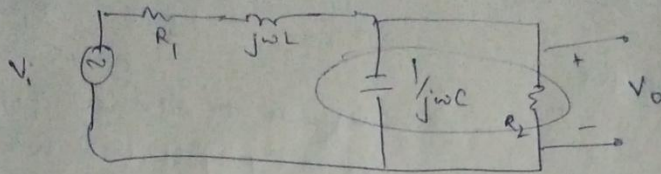


Tutorial 4

①




$$R_2 \parallel \frac{1}{j\omega C} = \frac{R_2 \times \frac{1}{j\omega C}}{R_2 + \frac{1}{j\omega C}}$$

$$= \frac{R_2 / j\omega C}{\frac{j\omega C R_2 + 1}{j\omega C}} = \frac{R_2}{1 + j\omega C R_2}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R} = \frac{R_2 + R_1}{R_1 R_2}$$

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

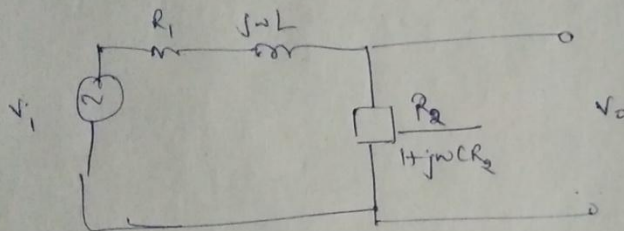

$$\frac{V_o}{V_i} = \frac{\frac{R_2}{1 + j\omega C R_2}}{R_1 + j\omega L + \frac{R_2}{1 + j\omega C R_2}}$$

$$= \frac{R_2 / (1 + j\omega C R_2)}{\frac{R_1(1 + j\omega C R_2) + j\omega L(1 + j\omega C R_2) + R_2}{1 + j\omega C R_2}}$$

$$= \frac{R_2}{R_1 + j\omega C R_2 R_1 + j\omega L + \cancel{j^2 \omega^2 L C R_2} + R_2}$$

$$= \frac{R_2}{R_1 + j\omega C R_2 R_1 + j\omega L - R_2 + R_2}$$


$$\Rightarrow \frac{V_o}{V_i} = \frac{R_2}{R_1 + j\omega L + j\omega C R_2 R_1}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\sqrt{LC} = \frac{1}{\omega}$$

$$LC = \frac{1}{\omega^2}$$

Q.2 (a)

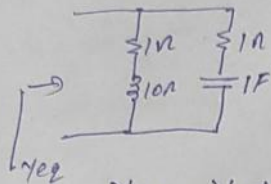

$$Y_{eq} = Y_1 + Y_2$$

$$Y_1 = \frac{1}{1+j10\omega} \times \frac{1-j10\omega}{1-j10\omega}$$

$$Y_1 = \frac{1-j10\omega}{1+100\omega^2}$$

$$Y_2 = \frac{1}{1+\frac{1}{j\omega \cdot 1}} = \frac{j\omega}{1+j\omega} \times \frac{1-j\omega}{1-j\omega} = \frac{\omega^2+j\omega}{1+\omega^2}$$

$$Y_{eq} = Y_1 + Y_2 = \frac{1}{1+100\omega^2} - \frac{j10\omega}{1+100\omega^2} + \frac{j\omega}{1+\omega^2} + \frac{\omega^2}{1+\omega^2}$$

$$Y_{eq} = \left(\frac{1}{1+100\omega^2} + \frac{\omega^2}{1+\omega^2} \right) + j \left(\frac{\omega}{1+\omega^2} - \frac{10\omega}{1+100\omega^2} \right)$$


for resonance frequency put imaginary term equal to zero

$$j \left(\frac{\omega}{1+\omega^2} - \frac{10\omega}{1+100\omega^2} \right) = 0$$

$$\frac{1}{1+\omega^2} = \frac{10}{1+100\omega^2}$$

$$\omega = \frac{1}{\sqrt{10}} \text{ rad/sec}$$

2(b)

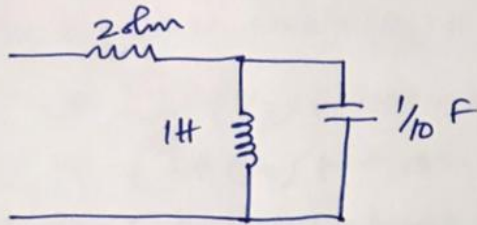

this is a tank circuit. resonance will occur when $X_L = X_C$

$$\Rightarrow SL = \frac{1}{SC}$$


$$\Rightarrow S^2 = \frac{1}{LC} \Rightarrow |\omega^2| = \frac{1}{LC}$$

$$\Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow \omega = \frac{1}{\sqrt{1 \times \frac{1}{10}}}$$


$$\Rightarrow \omega = \sqrt{10} \text{ rad.}$$

Sol-3

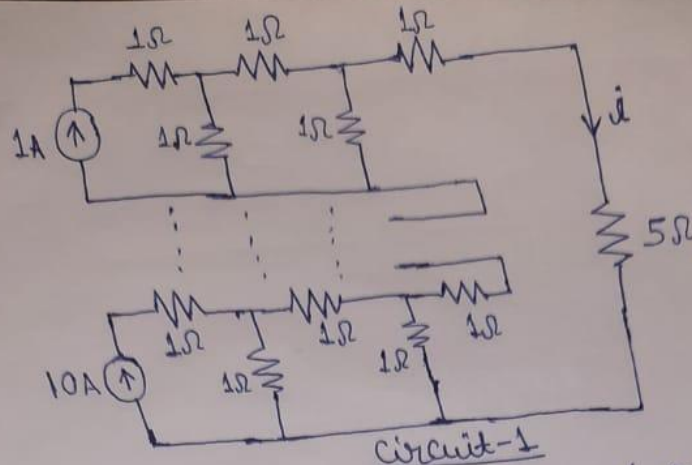


(a) Using Superposition, Keeping N th current source active and others to open circuit.

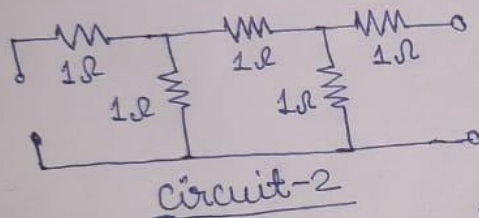(b) When the current source is open the equivalent Subcircuit look as follow:



$$\leftarrow R_{eq} = \frac{2 \times 1}{3} + 1 = \frac{5}{3} \Omega$$

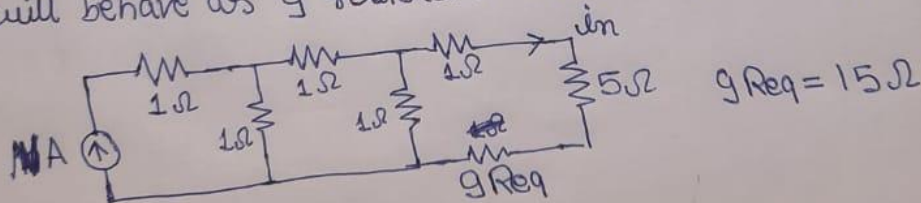(c) applying super-position ^{for} N th current source's contribution in i , ~~the~~ ~~other~~ subcircuits ~~will~~ will behave as 9 resistors in series of value $\frac{5}{3} \Omega$.



$$9R_{eq} = 15 \Omega$$

$$i_n = (1/65) A$$

Similarly, we can find i_1, i_2, \dots, i_{10}

$$i = i_1 + i_2 + \dots + i_{10} = \frac{1}{65} (1 + 2 + 3 + \dots + 10)$$

$$i = \frac{1}{65} \left[\frac{10 \times (10 + 1)}{2} \right] = \frac{11}{13} = 0.846 A$$


4

when $V_1 = 10 \text{ volt}$

$$i_1 = 2 \text{ A}$$


when $V_1 = 15 \text{ volt}$

$$V_2 = 11 \text{ V}$$

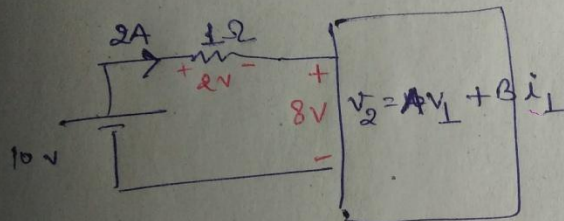

$$\Rightarrow V_2 = 10A + 2B$$

$$\Rightarrow 8 = 10A + 2B$$

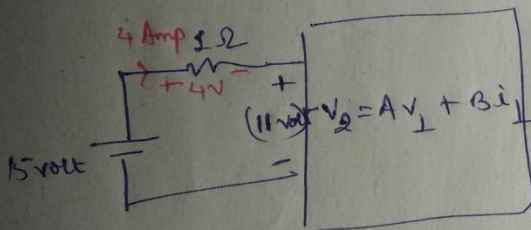

$$\Rightarrow 11 = 15A + 4B$$


$$8 = 10A + 2B$$

$$11 = 15A + 4B$$

\Rightarrow

$$A = 1 \text{ and } B = -1$$

5

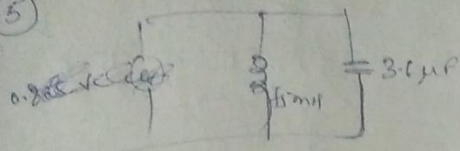

max. charge on capacitor = $2.9 \times 10^{-6} \text{ C}$
 \Rightarrow at this point capacitor is open
 \Rightarrow all current is flowing through inductor

$$Q = CV$$

$$2.9 \times 10^{-6} = 3.6 \times 10^{-6} V_{\text{max}}$$

$$\Rightarrow V_{\text{max}} = 0.805 \text{ volt}$$

~~Find Energy~~

at this point all energy is stored in capacitor

$$\text{energy} = \frac{1}{2} C V_{\text{max}}^2 = \frac{1}{2} \times 3.6 \times 10^{-6} \times (0.805)^2 = 1.16 \times 10^{-6}$$

~~Also~~ this same energy will be stored in capacitor, when current through inductor is maximum and voltage across capacitor is zero.

$$\text{energy} = \frac{1}{2} L i_{\text{max}}^2$$

$$\Rightarrow 1.16 \times 10^{-6} = \frac{1}{2} \times 75 \times 10^{-3} \times i_{\text{max}}^2$$

$$\Rightarrow i_{\text{max}}^2 = \frac{1.16 \times 10^{-6} \times 2}{75 \times 10^{-3}} = 0.0309 \times 10^{-3} = 30 \times 10^{-6} \text{ A}$$

$$i_{\text{max}} = \sqrt{30 \times 10^{-6}} \text{ A} = 5.477 \times 10^{-3} \text{ A} = 5.477 \text{ mA}$$

Sol-6

a) True: Resistor will dissipate the total energy (in form of electric and magnetic fields) in form of heat.

b) False: $Z = R + j\omega L - \frac{j}{\omega C} = R$ at $\omega_0 = \frac{1}{\sqrt{LC}}$

Phase is 0°

c) False: $X_C = \frac{1}{j\omega C} \Rightarrow \omega \uparrow \rightarrow X_C \downarrow$

d) True: Energy get stored in form of magnetic fields in inductor and electric fields in capacitor instead of getting dissipated.

e) False: $|Z| = \sqrt{R^2 + (X_L + X_C)^2} = R$ at $\omega_0 = \frac{1}{\sqrt{LC}}$
Current amplitude is maximum.

f) ~~False~~: $\Phi = \tan^{-1}\left(\frac{\omega L - \frac{1}{\omega C}}{R}\right)$: ~~depends on~~
True reactances

g) True: $Z = R + j\omega L - \frac{j}{\omega C}$: for ω , very high
 $(-\frac{j}{\omega C})$ $Z \approx j\omega L$

h) True: $|Z| = \sqrt{R^2 + (X_L + X_C)^2} = R = Z_{\min}$
at $\omega_0 = \frac{1}{\sqrt{LC}}$