
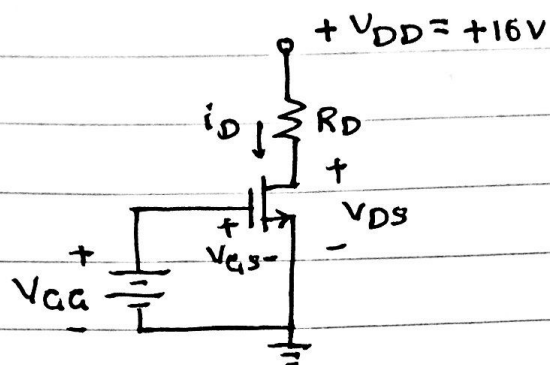


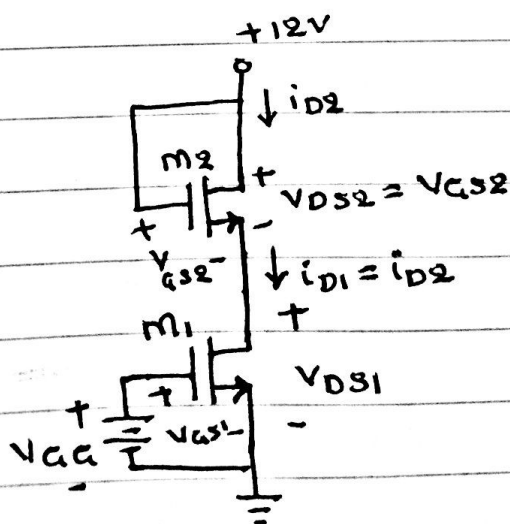
Q.1) For the circuit shown in the below figure, Suppose that $R_D = 250\Omega$ and the MOSFET has parameters $K = 0.25 \text{ mA/V}^2$ and $V_t = 2\text{V}$. Find V_{GS} such that $i_D = 4\text{mA}$



Q.2) For the circuit shown below, Suppose that both enhancement MOSFETs have $K = 0.25 \text{ mA/V}^2$ and $V_t = 2\text{V}$. When $V_{GS1} = 6\text{V}$, then M_1 operates in the active region. Find i_{D1} , i_{D2} , V_{DS1} , and V_{DS2} .



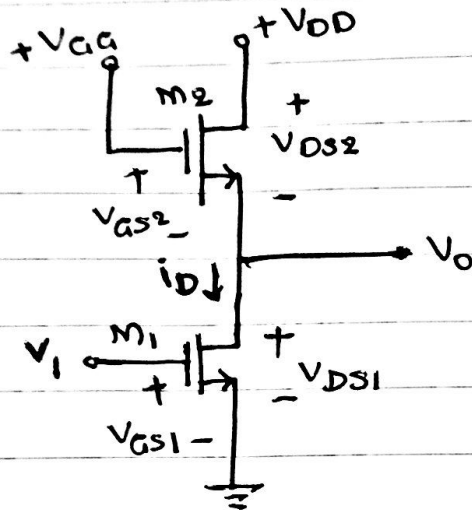Q.3) For the inverter given below figure, Suppose that $V_{GG} = 18V$, $V_{DD} = 12V$, and both MOSFETs have $V_T = 2V$. Given that $K_1 = 0.25 \text{ mA/V}^2$, analytically determine V_o for the case that $V_i = 12V$ and K_2 is (a) 0.25 mA/V^2 and (b) 0.05 mA/V^2 (M_1 operates in ohmic region)



Q.4) For the NMOS NOR gate given below, Suppose that $V_{DD} = 12V$, both enhancement MOSFETs have $V_T = 2V$ and $K = 0.25 \text{ mA/V}^2$, and the depletion MOSFET has $I_{DSS} = 4 \text{ mA}$ and $V_p = -4V$. Find V_o when $V_1 = V_2 = 12V$ (M_1 and M_2 are in ohmic region and M_3 is in the active region)

