
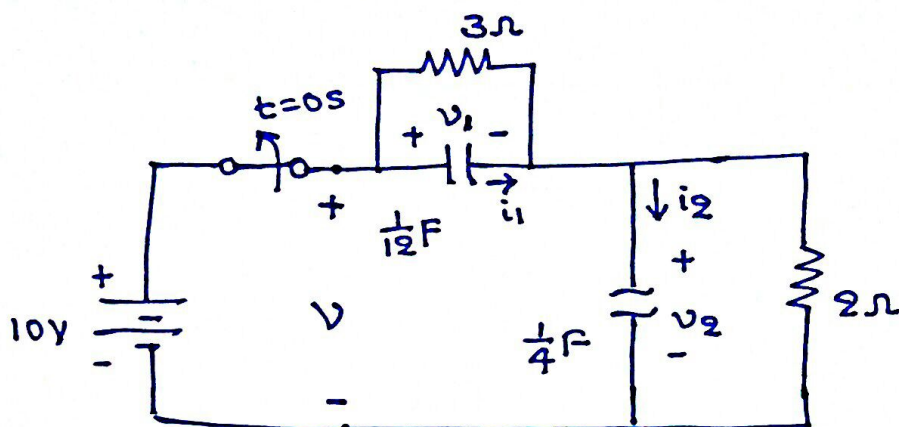


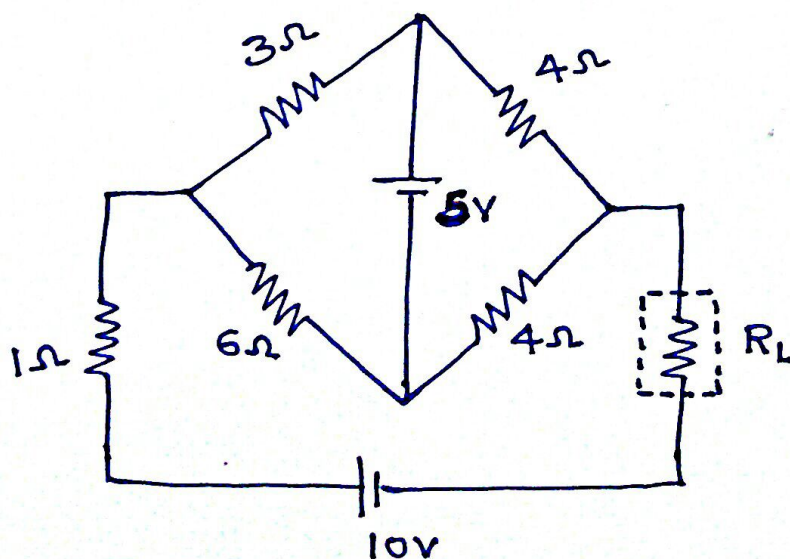1. Q) For the circuit shown below, the switch opens at time $t=0$ s. Find $v_1(t)$, $v_2(t)$, $i_1(t)$, $i_2(t)$ and $v(t)$ for all time.



2. Q) for the circuit shown in the below figure

- 1) find the R_L for maximum power dissipation
- 2) calculate the maximum power dissipated in R_L .



3.Q.4) For the circuit shown in figure below, suppose that $v(t)$ is described by the function given in Fig.(b). Sketch (a). $i(t)$, (b) $w_C(t)$, (c) $P_R(t)$, (d) $v_R(t)$ and (e) $v_S(t)$

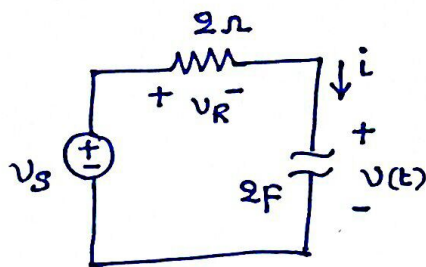


Fig.(a)


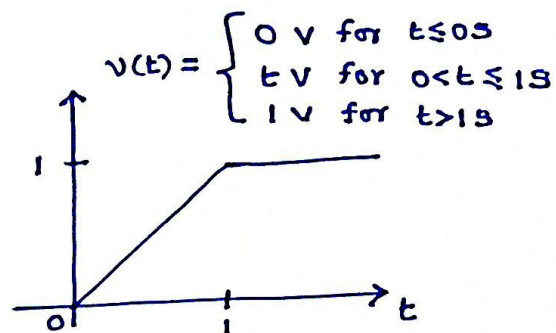


Fig.(b)

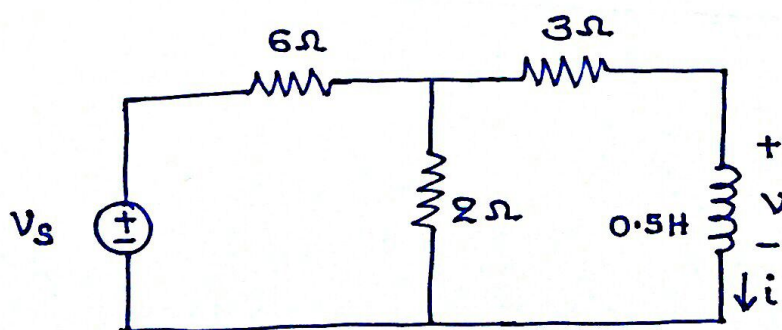4.Q) For the circuit shown below, suppose that $v_S(t) = 18 \text{ V}$ for $t < 0 \text{ s}$ and $v_S(t) = 0 \text{ V}$ for $t \geq 0 \text{ s}$. Write a differential equation in $i(t)$ for $t \geq 0 \text{ s}$. Find $i(t)$ and $v(t)$ for all time and sketch these functions.




5.Q) For the circuit shown in the below figure, the switch is

closed at $t = 0^+$ sec, ~~Find~~

(i) ~~$i(t)$~~ Find $i(t)$

(ii) plot $i(t)$

(iii) comment on the circuit response.

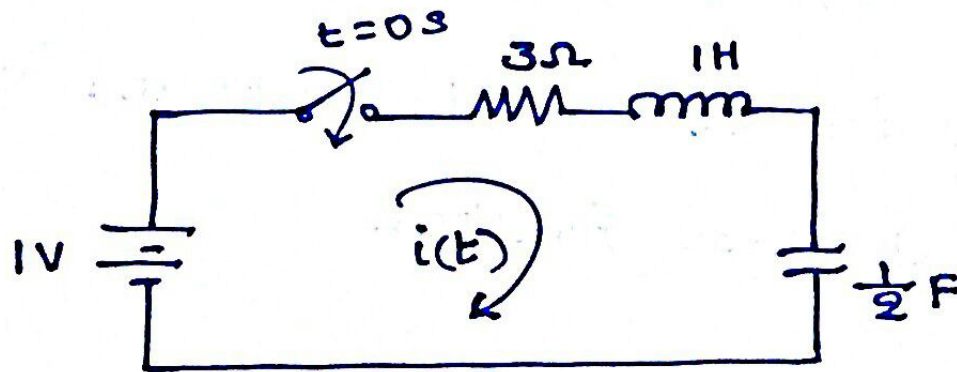

(iv) Find out the maximum voltage across the capacitor if $R = 1\text{ohm}$