
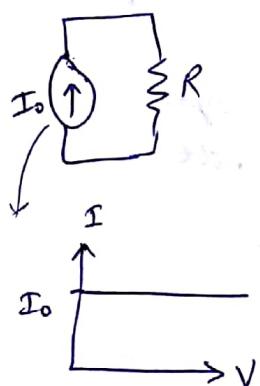

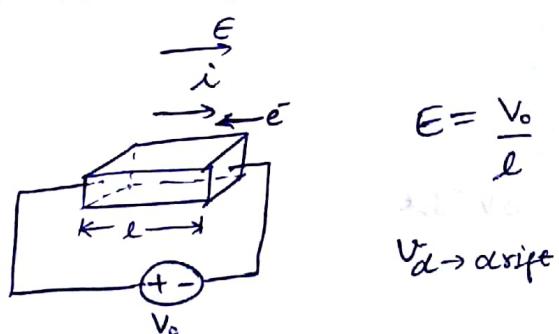
$$i = \frac{V_o}{R + R_{in}} \approx \frac{V_o}{R} \quad (R_{in} \ll R)$$



current source  $I_o$


$$(R_{in} \gg R)$$



$$E = \frac{V_o}{d}$$

$$F = (-e) E$$

$V_d \rightarrow$  drift

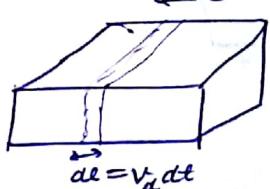

electron density =  $n$ .

$$n A V_d dt (-e)$$

$$i = \frac{Q}{dt}$$


$$\Rightarrow i = n e A V_d$$

current density :  $J = \frac{i}{A} = nev_a$ .

Resistivity  $\rho = \frac{E}{J}$  or  $J = \sigma E$ .

$$\Rightarrow \rho = \frac{V_o/l}{nev_a} \Rightarrow V_o = nev_a \rho l \Rightarrow \rho = \frac{V_o}{nev_a l} = \frac{E}{nev_a}$$
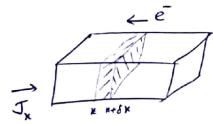
$$R = \frac{V_o}{i} = \frac{V_o}{JA} = \frac{El}{JA} = \frac{\rho l}{A} \Rightarrow R = \frac{\rho l}{A}$$



$\frac{J_x(x) dA}{(-e)} = \text{no. of es leaving the volume per unit time.}$

$\frac{J_x(x+\delta x) dA}{(-e)} = \text{no. of es entering the val./time}$

change in no. of es =  $(J_x(x+\delta x) - J_x(x)) \frac{dA}{(-e)} \delta t$


$$= \left( \frac{\partial J_x}{\partial x} \cdot \delta x \right) \frac{\delta y \delta z \cdot \delta t}{(-e)}$$

$$= \left( \frac{1}{-e} \right) \left( \frac{\partial J_x}{\partial x} + \frac{\partial J_y}{\partial y} + \frac{\partial J_z}{\partial z} \right) \cdot \delta V \cdot \delta t$$

$$\frac{\partial n(\vec{r}, t)}{\partial t} \delta V = \left( \frac{-1}{e} \right) (\vec{\nabla} \cdot \vec{J}) \cdot \delta V \cdot \delta t$$


$$\Rightarrow \frac{\partial n}{\partial t} = - \frac{\vec{\nabla} \cdot \vec{J}}{e} \Rightarrow \frac{\partial n}{\partial t} + \frac{1}{e} \vec{\nabla} \cdot \vec{J} = 0$$

continuity eqn.

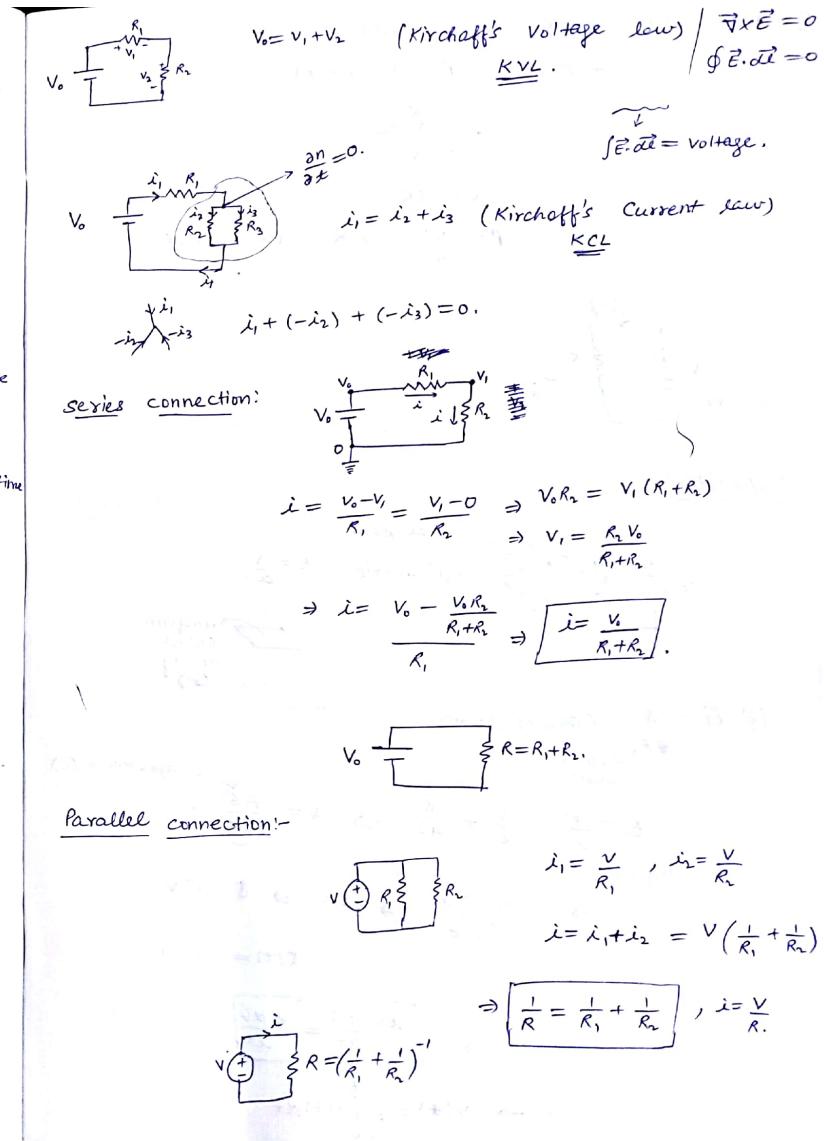


Instantaneous power :- (absorbed)

$$P = V(t) i(t)$$

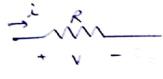


$$V = iR$$
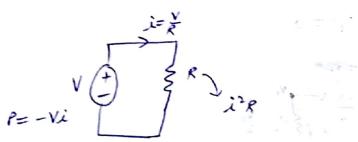
$$P = \frac{V^2}{R} = i^2 R = Vi = +ve.$$



Capacitor :-

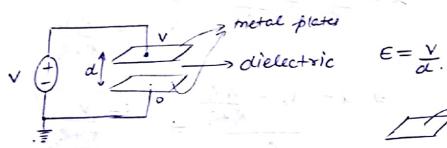

uniform charge density ( $\sigma$ )

$$\int \vec{E} \cdot d\vec{s} = \frac{Q}{\epsilon_0} \quad (\text{Gauss law})$$

$$E = \frac{\sigma}{\epsilon_0} = \frac{V}{d} = \frac{Q}{A\epsilon_0} \Rightarrow Q = \frac{A\epsilon_0}{d} \cdot V$$

$$V = \frac{Qd}{A\epsilon_0} \Rightarrow Q = CV \Rightarrow Q(t) = CV(t)$$


$$i = \frac{dQ}{dt} = C \frac{dV}{dt}$$

$$\Rightarrow V(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt .$$

$$V(t) = \frac{1}{C} \int_{-\infty}^{t_0} i(t) dt + \frac{1}{C} \int_{t_0}^t i(t) dt = \frac{1}{C} [V(t_0) + \int_{t_0}^t i(t) dt]$$

$$P_{abs}(t) = V(t) i(t)$$
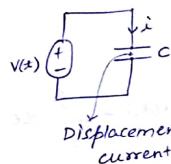
$$E.P = \int V i dt = \int C dV dt = \frac{1}{2} C V^2$$




$$i = C \frac{dV}{dt}$$

$$\frac{\partial \mathbf{H}}{\partial z} + \frac{1}{c} \nabla \cdot \vec{J} = 0 .$$

$$J_d = \epsilon \frac{\partial E}{\partial t}$$

Inductor :-

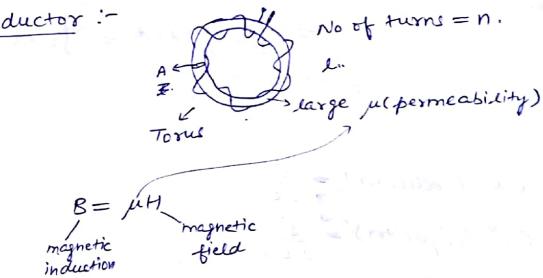

$$B = \mu H$$

$$\vec{J} \times \vec{H} = \vec{J}$$

$$\int H dl = i$$

$$\Rightarrow Hl = ni . \quad (n \text{ loops})$$

$$\Rightarrow H = \frac{ni}{l} \Rightarrow B = \frac{\mu ni}{l}$$

Magnetic flux  $\Phi = \int \vec{B} \cdot d\vec{s}$

$$= \mu_0 n i \cdot nA \Rightarrow \Phi = \frac{\mu_0 n^2 i}{l} \text{ Inductance (L)}$$

$$\Rightarrow \Phi = Li .$$

$$\Phi = L i \text{ (inductor)} \rightarrow v(t) = \frac{L di(t)}{dt}.$$

$$Q = C V \text{ (capacitor)} \rightarrow i(t) = C \frac{dv}{dt}.$$

$$V = \frac{d\phi}{dt} \quad (\vec{\nabla} \times \vec{E} = -\frac{\partial \vec{B}}{\partial t})$$

$$\hookrightarrow \int (\vec{\nabla} \times \vec{E}) \cdot d\vec{A} = \frac{\partial}{\partial t} \int \vec{B} \cdot d\vec{A}$$

$$\Rightarrow \int \vec{E} \cdot d\vec{A} = -\frac{\partial}{\partial t} \vec{B}.$$

$$i(t) = \frac{1}{L} \int_{-\infty}^t V dt = i(t_0) + \frac{1}{L} \int_{t_0}^t V dt$$

$$E = \int \vec{v} i d\ell$$

$$= \int (L \frac{d}{dx}) idx = \int L i dx$$

$$e = \frac{1}{2} L i^2$$

$$\epsilon = \frac{1}{2} L i^2 \text{ (inductor)} \rightarrow \frac{\partial^2}{2C}$$

$$E = \frac{1}{2} CV^2 \text{ (capacitor)} \xrightarrow{\Delta t} \frac{\phi^2}{2L}$$

SI units : C (farad)

L (Henry)

R (Ohm, Ω)


conductance,  $G = \frac{1}{R}$  (mho,  $\omega$ )

A circuit diagram consisting of a vertical voltage source  $V$  at the top. A horizontal line extends from its positive terminal to the left, then turns down and to the right, connecting to the bottom terminal of a capacitor  $C_1$ . The top terminal of  $C_1$  is connected to the leftmost terminal of an open terminal pair (OTP) labeled  $O$ . The rightmost terminal of the OTP is connected to the left terminal of a capacitor  $C_2$ . The right terminal of  $C_2$  is connected back to the common ground reference line at the bottom.

$$i_f = C_s \frac{d}{dt} (V - V_i)$$

$$i_2 = c_2 \frac{d}{dt} (V_t - e)$$
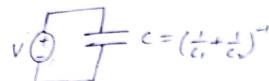
$$\frac{\dot{q}_1}{C_1} + \frac{\dot{q}_2}{C_2} = \frac{dV}{dt} \Rightarrow i \left( \frac{1}{C_1} + \frac{1}{C_2} \right) = \frac{dV}{dt}$$



$$i_1 = c_1 \frac{dV_0}{dt}, \quad i_2 = c_2 \frac{dV_0}{dt}$$

$$i = i_1 + i_2 = (C_1 + C_2) \frac{dV_0}{dt}.$$

$$\rightarrow \frac{1}{T} c_1 + c_2$$

$$V_i = \frac{L di}{dt}$$

$$V_{L1} = L_1 \frac{di}{dt}$$

$$V_{L_2} = L_2 \frac{di}{dt}$$

$$V = V_{L1} + V_{L2} = (L_1 + L_2) \frac{di}{dt}$$


$$L = L_1 + L_2 \quad .$$

$$V = L_1 \frac{di_1}{dt}$$


$$\frac{V}{L_1} + \frac{V}{L_2} = \frac{d(i_1 + i_2)}{dt} = \frac{di}{dt}$$

$$\Rightarrow \sqrt{\left(\frac{1}{L_1} + \frac{1}{L_2}\right)} = \frac{di}{dt} \rightarrow \frac{1}{L}$$

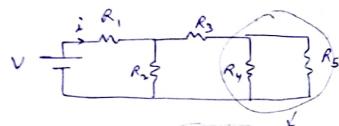
$$L = \left( \frac{1}{t_1} + \frac{1}{t_2} \right)^{-1},$$





series-parallel circuit

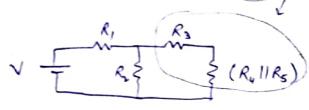
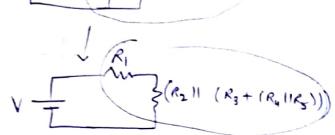
$$V \rightarrow V - (R_4 \parallel R_5) + R_3 + (R_4 \parallel R_5)$$



↓

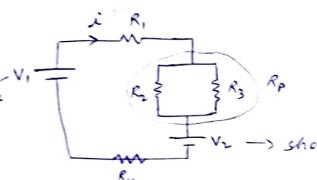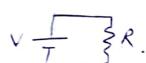


$$IR_1 + IR_p + V_2 + IR_4 = V_1 \quad \text{by shorting } V_1$$

$$\Rightarrow I = \frac{V_1 - V_2}{R_1 + R_p + R_4} = \frac{V_1}{R_1 + R_p + R_4} - \frac{V_2}{R_1 + R_p + R_4}. \quad \text{by shorting } V_2$$


Superposition.

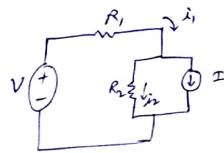- Keep one <sup>voltage</sup> source active and short all others & superpose.
- In case of current sources, open them (remove).



1) Open current source.

2) Short the voltage source.

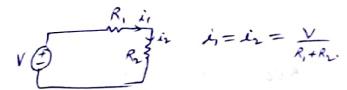

$$i_1 = \frac{IR_2}{R_1 + R_2}, \quad i_2 = -\frac{IR_1}{R_1 + R_2}$$

Superposition:


$$i_1 = \frac{V}{R_1 + R_2} + \frac{IR_2}{R_1 + R_2}, \quad i_2 = \frac{V}{R_1 + R_2} - \frac{IR_1}{R_1 + R_2}$$

$\frac{R_1}{R_2}$


$$P = i^2 R_1 = (i_1 + i_2)^2 R_1$$

$$= \underbrace{i_1^2 R_1}_{1st \ case} + \underbrace{i_2^2 R_1}_{2nd \ case} + 2i_1 i_2 R_1$$

No superposition  
for P.

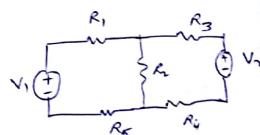


Node Voltages

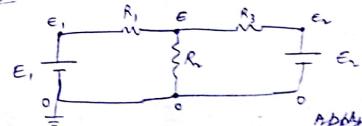

Apply KCL at nodes:
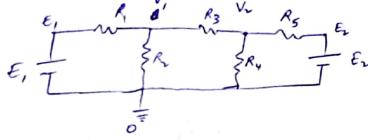
$$E \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = \frac{E_1}{R_1} + \frac{E_2}{R_2} \Leftrightarrow \frac{E - E_1}{R_1} + \frac{E - E_2}{R_2} + \frac{E - E_1}{R_3} = 0.$$



KCL at nodes:-

$$\frac{E_1 - V_1}{R_1} + \frac{0 - V_1}{R_2} + \frac{V_2 - V_1}{R_3} = 0 \quad \& \quad \frac{V_1 - V_2}{R_3} + \frac{0 - V_2}{R_4} + \frac{E_2 - V_2}{R_5} = 0.$$


$$\begin{aligned} G_{11} V_1 + G_{12} V_2 &= I_1 \\ G_{21} V_1 + G_{22} V_2 &= I_2 \end{aligned}$$

$$\begin{bmatrix} G_{11} & G_{12} \\ G_{21} & G_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Cramer's rule:

$$V_1 = \frac{\begin{vmatrix} I_1 & G_{12} \\ I_2 & G_{22} \end{vmatrix}}{D_G} \quad V_2 = \frac{\begin{vmatrix} G_{11} & I_1 \\ G_{12} & I_2 \end{vmatrix}}{D_G}$$
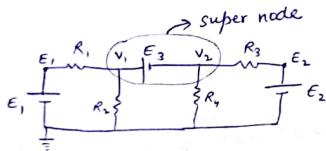
$$D_G = \begin{vmatrix} G_{11} & G_{12} \\ G_{21} & G_{22} \end{vmatrix} \quad V_n = \frac{\begin{vmatrix} G_{11} & I_1 \\ G_{12} & I_2 \end{vmatrix}}{D_G}$$



$$(i) - \frac{E_1 - V_1}{R_1} + \frac{0 - V_1}{R_2} + \frac{E_2 - V_2}{R_3} + \frac{0 - V_2}{R_4} = 0 \Rightarrow V_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) + V_2 \left( \frac{1}{R_3} + \frac{1}{R_4} \right) = \frac{E_1}{R_1} + \frac{E_2}{R_3}$$


$$(ii) - V_1 = V_2 + E_3.$$

Mesh currents:-




$$\text{KVL: } \begin{aligned} E_1 - R_1 I_1 + R_2 (I_1 + I_2) &= 0 \Rightarrow I_1 \underbrace{(R_1 + R_2)}_{R_{12}} + I_2 \underbrace{\frac{R_1}{R_2}}_{R_{21}} = E_1 \\ E_2 - R_3 I_2 + R_2 (I_1 + I_2) &= 0 \Rightarrow I_1 \underbrace{\frac{R_2}{R_3}}_{R_{13}} + I_2 \underbrace{(R_2 + R_3)}_{R_{22}} = E_2 \end{aligned}$$

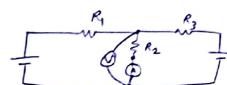- 1) Series-parallel
- 2) Superposition
- 3) Node method
- 4) Mesh method.




Thevenin's theorem:-
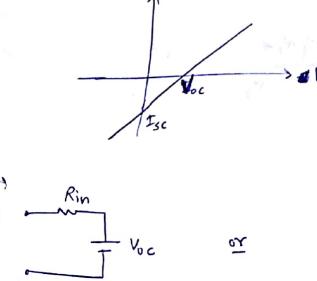
$$V = \frac{1}{R_1} E_{out} + \frac{1}{R_2} E_{in}$$



Norton's theorem



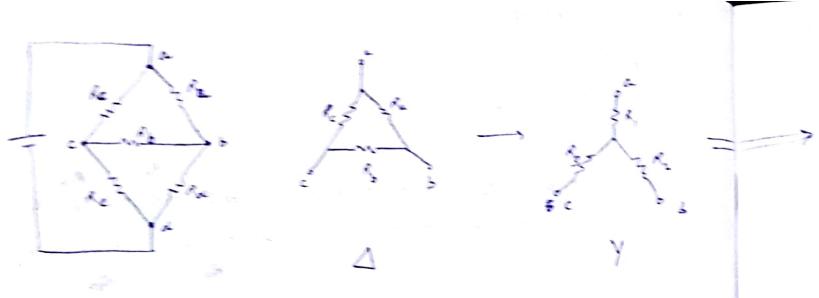

$$(R_{ab})_Y = (R_{ab})_{\Delta}$$

$$R_a + R_b = R_a \parallel (R_b + R_c) = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c}.$$

$$(R_{bc})_Y = (R_{bc})_{\Delta}$$

$$(R_{ac})_Y = (R_{ac})_{\Delta}.$$


Show

$$R_1 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_b}{R_a + R_b + R_c}$$
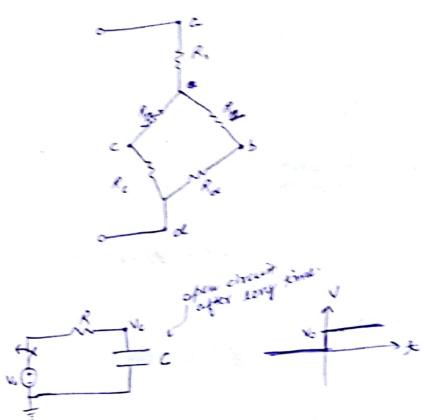
$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}.$$



$$\frac{V_o - V_c}{R} = \frac{C \frac{dV_c}{dt}}{RC}$$

$$\frac{dV_c}{dt} + \frac{V_c}{RC} = \frac{V_o}{RC}$$

$$V_c(t) = V_{c_h}^{(t)} + V_{c_p}^{(t)}$$

Homogeneous      Particular

$$\frac{dV_{c_h}}{dt} + \frac{V_{c_h}}{RC} = 0$$

$$\therefore V_{c_h}^{(t)} = Ae^{st} = Ae^{\frac{-t}{RC}}$$

$$AS e^{st} + \frac{Ae^{st}}{RC} = 0 \Rightarrow s = -\frac{1}{RC}.$$

$$\frac{dV_{c_p}}{dt} + \frac{V_p}{RC} = \frac{V_o}{RC} \Rightarrow [V_{c_p} = V_o]. \quad (\text{Assuming } V_{c_p} \text{ as constant}).$$

$$\Rightarrow [V_c(t) = Ae^{-\frac{t}{RC}} + V_o] \quad \begin{matrix} \text{use boundary} \\ \text{condition} \end{matrix}$$


At  $t=0$ ,  $V_C = 0$  (initially capacitor is not charged)

$$V_C(t=0) = 0$$

$$\Rightarrow A e^{-t/\tau} + V_0 = 0 \Rightarrow A = -V_0.$$

so,
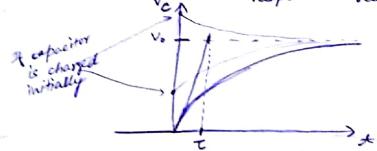
$$V_C(t) = V_0 \left(1 - e^{-t/\tau}\right).$$




$\tau = RC$  = time constant ( $\tau$ ).

$$e^{-5} \approx 0.0067$$



$$i(t) = \frac{V_0 - V_C(t)}{R} = \frac{V_0}{R} e^{-t/\tau}$$
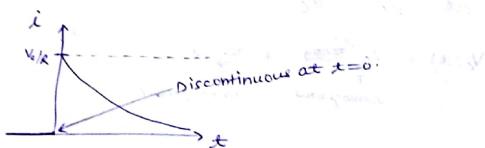
$$= \frac{C dV_C(t)}{dt} = \frac{V_0}{R} e^{-t/\tau}$$



At  $t=0^+$   $\Rightarrow$  Voltage drop across resistor  $= V_0$ .

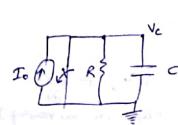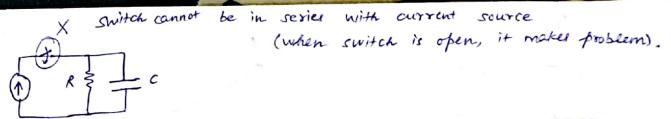$t=\infty \Rightarrow$  capacitor  $= V_0$ .



switch opened at  $t=0$ .

$$I_0 = \frac{V_0}{R} + C \frac{dV_C}{dt}$$

$$V_C(t) = V_{CH}(t) + V_{CP}$$

$$V_{CH}(t) = A e^{-t/\tau}$$




$$V_{CP}(t) = I_0 R$$

$$V_C(t) = A e^{-t/\tau} + I_0 R$$


$V_C = 0$  at  $t=0$   $\rightarrow$  Boundary condition:  $V_C(t)$

$$\Rightarrow V_C(t) = I_0 R \left(1 - e^{-t/\tau}\right)$$
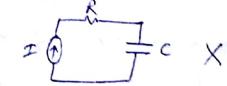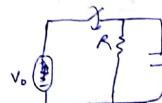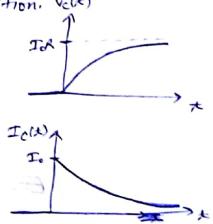
$$I_C(t) = C \frac{dV_C(t)}{dt} = I_0 e^{-t/\tau}$$



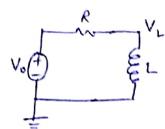(Current will keep going and  $V_C$  will increase to infinity)






$$I_L R + L \frac{dI_L}{dt} = V_0$$


$$I_L(t) = I_{LH}(t) + I_{LP}$$

$I_L = 0$  at  $t=0$  boundary condition
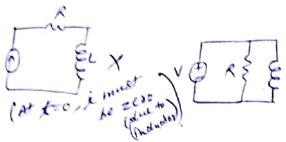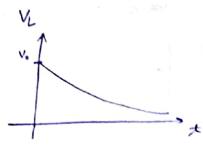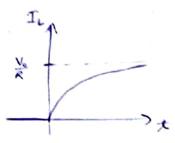
$$\Rightarrow \boxed{I_L = \frac{V_0}{R} \left(1 - e^{-\frac{t}{\tau}}\right)}, \quad (\tau = \frac{L}{R})$$



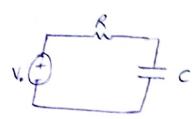(Across  $L$  is constn,  $V = \frac{L di}{dt}$   
it keeps on increasing)




$$\begin{aligned} \text{Power given by voltage source} &= \int_0^\infty i V_0 dt \\ &= \int_0^\infty i V_0 dt \\ &= \int_0^\infty \frac{V_0}{R} e^{-\frac{t}{RC}} dt \\ &= \frac{V_0^2}{R} \left[ -e^{-\frac{t}{RC}} \right]_0^\infty \\ &= C V_0^2 (1) \end{aligned}$$

$$\Rightarrow E = C V_0^2$$

$$\boxed{\text{Energy stored in capacitor} = \frac{1}{2} C V_0^2}$$

$$\text{Energy spent in resistor} = \frac{1}{2} C V_0^2$$
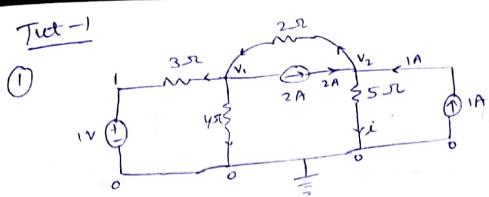
$$\begin{aligned} \int_0^\infty i^2(t) R dt &= \left( \frac{V_0}{R} \right)^2 R \int_0^\infty e^{-2t/RC} dt \\ &= \frac{1}{2} C V_0^2. \end{aligned}$$



$$2+1 = \frac{V_2}{5} + \frac{V_2 - V_1}{2}$$

$$\frac{V_2 - V_1}{2} = \frac{V_1}{4} + 2 + \frac{V_1 - 1}{3}$$

$$3 = \frac{V_2}{5} + \frac{V_2 - V_1}{2}$$

$$\frac{V_2 - V_1}{2} = \frac{7V_1}{12} + \frac{2V_1}{3} + \frac{5}{3}$$

$$6V_2 - 18V_1 = 7V_1 + 20$$

$$30 = 7V_2 + 7V_2 - 5V_1$$

$$6V_2 - 13V_1 = 20$$


$$7V_2 - 5V_1 = 30$$

$$(30 - 91)V_2 = 100 - 390$$

$$V_2 = \frac{350}{61}$$

$$\frac{280}{61 \times 5} = \frac{56}{61}$$



(2)

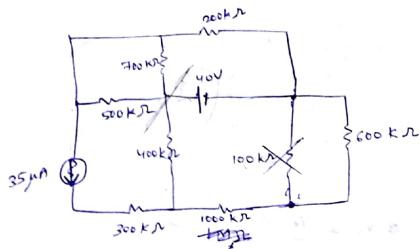

$$\text{open } \textcircled{1} \text{ & short } \textcircled{2}$$

$$R_{th} = 420 \text{ k}\Omega$$

$$1400 \times 600 = \frac{3}{12+90}$$

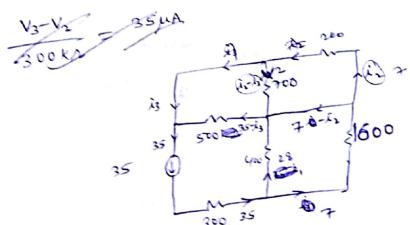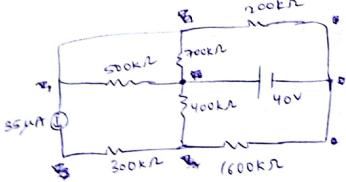

$$1600i_1 = 400(35 - i_1)$$


$$5i_1 = ?$$

$$200i_2 + 700(i_2 - i_3) = 0$$

$$9i_2 = 7i_3$$

$$200(i_2 - i_3) + 500(35 - i_3) = 0$$

$$7i_2 - 12i_3 + 35 \times 5 = 0$$

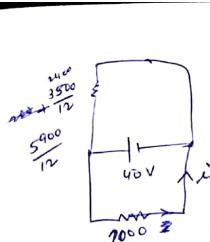

$$i = 0.0249 \text{ A.}$$

$$12V + \frac{7}{100000} \times 400 \times 10000 = 8V_{th}$$

$$\frac{42}{10} + 12 = 16.2 \text{ V}$$


$$2000 \times \frac{5900}{12}$$

$$\frac{400(3500)}{2000 + 5900}$$

$$\frac{400(3500)}{299}$$

$$\frac{400(3500)}{299} \times \frac{R}{AB} =$$

$$i_3 = \frac{1}{350}$$

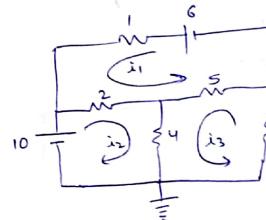

$$6 = i_1 + 2(i_1 + i_2) + 5(i_1 - i_3) + 2i_6$$

$$10 = i_1 + 2(i_1 + i_2) + 4(i_1 + i_3)$$

$$6i_3 + 5(i_3 - i_1) + 4(i_1 + i_3) = 0$$

$$26i_2 + 15i_3 = 50$$

$$38i_2 + 50i_3 = 50$$

$$18i_2 = 50$$

$$i_2 = \frac{50}{18}$$

$$10i_1 + 2i_2 - 5i_3 = 6$$

$$2i_1 + 6i_2 + 4i_3 = 10$$

$$5i_1 - 4i_2 - 15i_3 = 0$$

$$\frac{10i_1 + 2i_2 - 5i_3 = 6}{5i_1 - 4i_2 - 15i_3 = 0}$$

$$i_3 = \frac{11}{25}$$

$$i_1 = \frac{50}{18}$$

$$i_2 = \frac{50}{18}$$

$$i_1 = \frac{50}{18}$$

$$i_2 = \frac{50}{18}$$

$$i_3 = \frac{11}{25}$$

$$i_1 = \frac{50}{18}$$

$$i_2 = \frac{50}{18}$$

$$i_3 = \frac{11}{25}$$

$$i_1 = \frac{50}{18}$$

$$i_2 = \frac{50}{18}$$

$$i_3 = \frac{11}{25}$$


$$i_1 = \frac{50}{18}$$

$$i_2 = \frac{50}{18}$$

$$i_3 = \frac{11}{25}$$

$$i_1 = \frac{50}{18}$$

$$i_2 = \frac{50}{18}$$

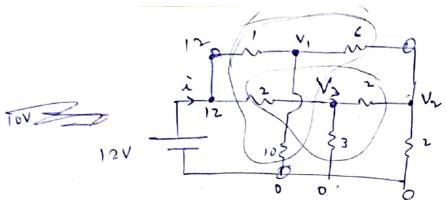

$$\frac{3(0 - V_1)}{1} + \frac{0 - 3V_1}{2} + \frac{5(V_2 - V_1)}{3} = 0.$$



$$\frac{3V_3 - 0}{2} + \frac{2V_3 - V_2}{3} + \frac{2V_3 - 0}{3} = 0.$$

$$\frac{3V_3}{2} + \frac{V_2 - V_1}{3} + \frac{3V_2}{3} = 0.$$

$$38V_1 - 5V_2 = 360.$$

$$7V_3 - 2V_2 = 36,$$

$$7V_2 - 3V_3 - V_1 = 0.$$

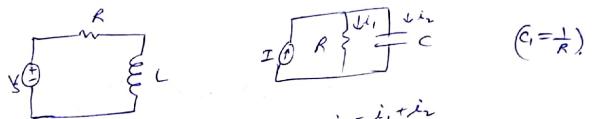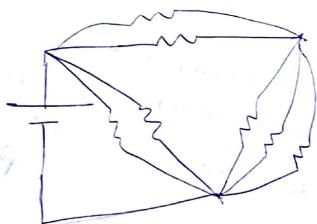

$$V_s = V_1 + V_R$$


$$V_s = RI + L \frac{di}{dt}$$

$$i_s = i_1 + i_2$$

$$i_s = C \frac{dv}{dt} + C \frac{dv}{dt} \rightarrow V_R.$$

$$\begin{aligned} x_1 &= V_1 + V_R \\ x_2 &= L \frac{di}{dt} \\ x_3 &= C \frac{dv}{dt} \end{aligned}$$



$$(C_1 = \frac{1}{R})$$

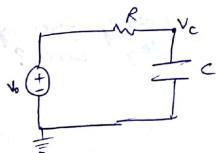

$$V_c(t) = V_o (1 - e^{-t/RC}) + V_i e^{-t/RC}$$

$$= V_o (1 - e^{-(t-T)/RC})$$

(time invariance)

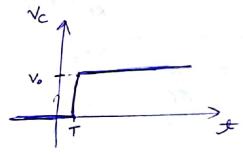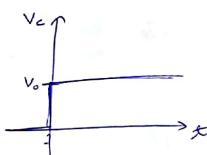


Discharging




$$t < T : V_c(t) = V_o (1 - e^{-t/RC})$$
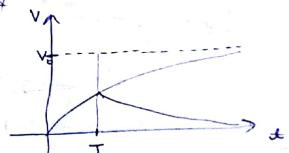
$$t > T : V_c(t) = V_c(T) e^{-\frac{(t-T)}{RC}} = V_o (1 - e^{-T/RC}) e^{-\frac{(t-T)}{RC}}$$



$$t \rightarrow T \quad e^{j\omega t} = \cos(\omega t) + j\sin(\omega t)$$
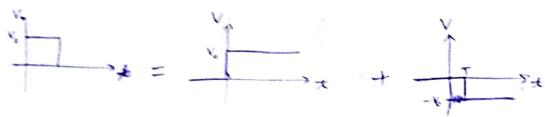
$$V_c(t) = V_0 (1 - e^{-T/\tau_C}) + (-V_0) (1 - e^{-(t-T)/\tau_C}).$$



Sources  $\begin{cases} T \rightarrow 0, V_0 \rightarrow \infty \\ \text{show that } V_0 T = K. \end{cases}$

$$\begin{aligned} V_c(t) &= V_0 (1 - e^{-T/\tau_C}) e^{-(t-T)/\tau_C} \\ &= e^{-T/\tau_C} = 1 - \left(\frac{T}{\tau_C}\right) + \left(\frac{T}{\tau_C}\right)^2 + \dots \end{aligned}$$

Energy given by  
Voltage source?

$$\begin{aligned} \underline{1 - e^{-T/\tau_C}} &= \frac{T}{\tau_C} - \left(\frac{T}{\tau_C}\right)^2 + \dots \\ \xrightarrow{\text{Influence response}} V_c(t) &= \frac{K}{RC} e^{-t/RC} - \frac{V_0 T}{RC} e^{-t/RC}. \end{aligned}$$

$$\begin{aligned} i_L \downarrow C &\quad \begin{cases} V_c \\ \text{---} \end{cases} \quad \begin{cases} L \downarrow i_L \\ \text{---} \end{cases} \quad \frac{KCL}{C} \\ C \frac{dV_c}{dt} + \frac{1}{L} \int_{-\infty}^t & \pm V_c(t') dt' = 0 \\ \boxed{\frac{d^2 V_c}{dt^2} + \frac{V_c(t)}{CL} = 0.} \end{aligned}$$

$$\text{Try: } V_c = A e^{mst}$$

$$\begin{aligned} s^2 + \frac{1}{LC} &= 0 \Rightarrow s = \pm \frac{1}{\sqrt{LC}}. \\ (\text{characteristic equation}) \quad \Rightarrow s &= \pm \frac{j}{\sqrt{LC}} \quad (j^2 = -1) \end{aligned}$$

$$V_c(t) = K_1 \cos(\omega_0 t) + K_2 \sin(\omega_0 t)$$

Need 2 boundary conditions

$$\left( \frac{\partial^2 V_c}{\partial t^2} + \frac{1}{LC} V_c = 0 \right)$$

$$V_c(t=0) = V_c(0) \Rightarrow K_1 = V_c(0)$$

$$i_L(t=0) = i_L(0) \Rightarrow R_i C V_c =$$

$$i_L(t) = -\frac{C dV_c}{dt} \approx -\frac{C \omega_0 V_c}{\tau_C} \approx -\frac{C \omega_0}{\tau_C} (-K_1 \cos(\omega_0 t) + K_2 \sin(\omega_0 t))$$

$$\Rightarrow i_L(0) = -K_2 C \omega_0.$$

$$\Rightarrow K_2 = -\frac{i_L(0)}{C \omega_0}.$$

$$\Rightarrow V_c(t) = V_c(0) \cos(\omega_0 t) - \frac{i_L(0)}{C \omega_0} \sin(\omega_0 t); \omega_0 = \frac{1}{\sqrt{LC}}$$

$$i_L(t) = \sqrt{\frac{C}{L}} V_c(0) \sin(\omega_0 t) - \frac{i_L(0)}{\omega_0} \cos(\omega_0 t).$$

$$\left[ a \cos k - b \sin k = \sqrt{a^2 + b^2} \cos(x+d); \tan d = \frac{b}{a} \right]$$

$$V_c(t) = \left[ V_c(0)^2 + \frac{1}{C} i_L(0)^2 \right]^{\frac{1}{2}} \cos \left( \omega_0 t + \tan^{-1} \left( \sqrt{\frac{i_L(0)}{V_c(0)}} \right) \right)$$



$$i_L(t) = \sqrt{\frac{C}{L}} \left[ \dots \right]^{\frac{1}{2}} \sin \left( \dots \right)$$

90° phase apart


$$\text{If } i_L(0) = 0$$

$$\Rightarrow V_c(t) = V_c(0) \cos(\omega_0 t)$$
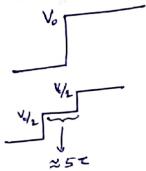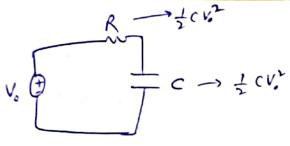
$$i_L(t) = \sqrt{\frac{C}{L}} V_c(0) \sin(\omega_0 t)$$


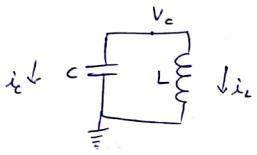
$$E_{dissipated} = \frac{1}{2} C \left(\frac{V_o}{2}\right)^2 + \frac{1}{2} C \left(\frac{V_o}{2}\right)^2 = \frac{1}{4} C V_o^2$$



$$\begin{aligned} \text{Energy stored} &= \frac{1}{2} C V_c(t) + \frac{1}{2} L i_L(t)^2 \\ &= \frac{1}{2} C \left(V_c(0) + \frac{L}{C} i_L(0)^2\right) \cos^2 \theta \\ &\quad + \frac{1}{2} L \left(\frac{C}{L}\right) \left(\dots\right) \sin^2 \theta \end{aligned}$$


$$E = \frac{1}{2} C V_c(0) + \frac{1}{2} L i_L(0)^2 \quad (\text{conserved})$$

$$\frac{1}{2} C V_c^2(\max) = \frac{1}{2} L i_L^2(\max) \Rightarrow \frac{V_c(\max)}{i_L(\max)} = \sqrt{\frac{L}{C}}. \quad (\text{characteristic impedance})$$

$$E(t) = \frac{1}{2} C V_c(t)^2 + \frac{1}{2} L i_L(t)^2$$

$$\begin{aligned} \frac{dE(t)}{dt} &= \left(C V_c \frac{dV_c(t)}{dt} + L i_L \frac{di_L(t)}{dt}\right) = \epsilon V_c (-\lambda_L) + V_c (\lambda_L) \\ i_c &= C \frac{dV_c}{dt} = -i_L \\ V_c &= L \frac{di_L}{dt} \end{aligned}$$

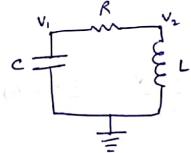$\Rightarrow E(t) = \text{constant}$   
Energy is conserved



$$\begin{aligned} \frac{dV_i}{dt} + \frac{V_i - V_o}{R} &= 0 \Rightarrow V_o = RC \frac{dV_i}{dt} + V_i \\ \frac{V_o - V_i}{R} + \frac{1}{L} \int_{-\infty}^t V_o(t') dt' &= 0 \end{aligned}$$

$$\frac{dV_i}{dt} + \frac{1}{L} \int_{-\infty}^t \left(RC \frac{dV_i}{dt'} + V_i\right) dt' = 0.$$

$$\frac{d^2V_i}{dt^2} + \frac{R}{L} \frac{dV_i}{dt} + \frac{1}{LC} V_i = 0.$$

$$\text{Try } V_i = A e^{st}$$

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0 \quad (\text{characteristic eqn.})$$

$$s = -\frac{(R/L) \pm \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}}{2} = -\alpha \pm \sqrt{\omega^2 - \alpha^2}. \quad \begin{matrix} S_1 \\ S_2 \end{matrix}$$

$$\text{Define } \alpha = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$V_i(t) = A_1 e^{S_1 t} + A_2 e^{S_2 t}$$

1)  $\alpha < \omega_0$  — underdamped dynamics

2)  $\alpha = \omega_0$  — critically damped

3)  $\alpha > \omega_0$  — overdamped

$$\text{Define } \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$V_i(t) = A_1 e^{-\alpha t} e^{j\omega_d t} + A_2 e^{-\alpha t} e^{-j\omega_d t}$$

$$= e^{-\alpha t} (K_1 \cos \omega_d t + K_2 \sin \omega_d t)$$


$$V_c(t=0) = V_c(0), \quad i_L(t=0) = 0.$$

$$k_1 = V_c(0)$$

$$\lambda_L = -c \frac{dV_c}{dt} \Rightarrow c(k_1 \alpha - k_2 \omega_d) = 0 \Rightarrow k_2 = \frac{ck_1 \alpha}{\omega_d} = \frac{\alpha}{\omega_d} V_c(0).$$

$$V_c(t) = V_c(0) \sqrt{1 + \left(\frac{\alpha}{\omega_d}\right)^2} e^{-\alpha t} \cos(\omega_d t + \phi)$$
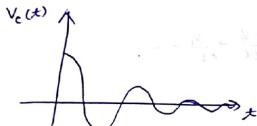
$$\lambda_L(t) = -e^{-\alpha t} \sin(\omega_d t).$$



Quality factor -

$$(1 \text{ dimensionless}) Q = \frac{c\omega_0}{2\alpha} = \frac{1}{R} \sqrt{\frac{L}{C}} \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad \alpha = \frac{R}{2L}$$

If  $\alpha$  small,  $Q$  large.  
( $R$  small)

$$T = \frac{2\pi}{\omega_d} \quad (\text{period of oscillation})$$

$Q$  oscillations =  $\frac{2\pi Q}{\omega_d}$

$$\text{Amplitude} \sim e^{-\frac{\pi Q}{\omega_d}} \approx e^{-\pi} = 4\%.$$

(If  $Q > 1, \omega_d \approx \omega_0$ ).

3)  $\alpha > \omega_0$  (overdamped)

$$\frac{R}{2} > \sqrt{\frac{L}{C}}$$



$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad [ \text{real} ] \quad -\text{ve}. \\ s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$V_c(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\lambda_L(t) = -c \frac{dV_c}{dt} = -c[s_1 A_1 e^{s_1 t} + s_2 A_2 e^{s_2 t}]$$

$$\text{At } t=0, V_c(0)=0 \\ \lambda_L(0)=0$$
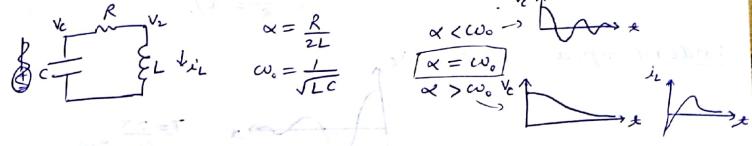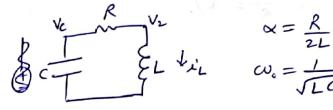
$$A_1 + A_2 = V_c(0), \quad s_1 A_1 + s_2 A_2 = 0 \Rightarrow A_1 = \frac{s_2 V_c(0)}{s_2 - s_1} = +ve \quad (s_1, s_2 < 0) \\ A_2 = \frac{s_1 V_c(0)}{s_1 - s_2} = -ve \quad (s_1 > s_2)$$



$$\alpha = \omega_0 \rightarrow s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -\alpha \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -\alpha \quad \left. \begin{array}{l} s_1 = s_2, \text{ only one independent solution.} \\ (\text{but should have 2}) \end{array} \right\}$$

$$\frac{d^2 V_c}{dt^2} + 2\alpha \frac{dV_c}{dt} + \omega^2 V_c = 0. \quad -e^{-\alpha t}, te^{-\alpha t}$$


$$V_c(t) = A_1 e^{-\alpha t} + A_2 t e^{-\alpha t} = e^{-\alpha t} (A_1 + A_2 t) \quad (A_1, A_2 \text{ constants})$$

$$\lambda_L = -c \frac{dV_c}{dt} = -c e^{-\alpha t} (A_1 \alpha - A_2 \alpha t + A_2)$$

$$V_c(0) = 0, \quad \lambda_L(t=0) = 0$$

$$A_1 = V_c(0) \quad \Rightarrow \quad -A_1 \alpha + A_2 = 0 \Rightarrow A_2 = A_1 \alpha$$
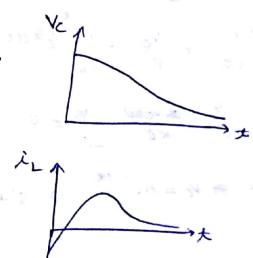
$$\Rightarrow V_c(t) = V_c(0) [1 + \alpha t] e^{-\alpha t}.$$



Energy Loss :-


$$E = \frac{1}{2} C (V_C(t))^2 + \frac{1}{2} L (i_L(t))^2.$$

$$\frac{dE}{dt} = C V_C \frac{dV_C}{dt} + L i_L \frac{di_L}{dt}, \quad i_L = \frac{V_C}{R}$$

$$\frac{dE}{dt} = -V_C i_L + V_L i_L = (V_L - V_C) i_L = -R i_L^2.$$

$$\left( \frac{V_C - V_L}{R} = i_L \right).$$

Underdamped case :-

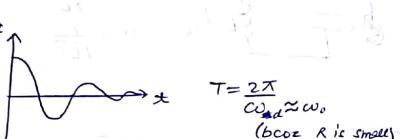


In one cycle:

$$\Delta E = R < i_L^2 > T,$$

$$\frac{E}{\Delta E} = \frac{L < i_L^2 >}{R T} = \frac{L \cdot \omega_0}{R \cdot 2\pi} = \frac{1}{R} \sqrt{\frac{L}{C}} \cdot \frac{1}{2\pi\theta}.$$
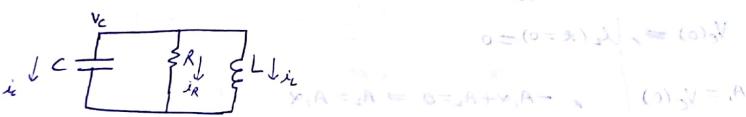
$$\Rightarrow Q = \frac{2\pi E}{\Delta E}.$$



$$\frac{d^2V_C}{dt^2} + \frac{V_C}{R} + \frac{1}{L} \int_{-\infty}^t V_C(t') dt' = 0.$$

$$\Rightarrow \frac{d^2V_C}{dt^2} + \frac{(dV_C/dt)}{RC} + \frac{V_C}{LC} = 0$$

$$\text{Assume } V_C = A e^{-st} \Rightarrow s^2 + \frac{s}{RC} + \frac{1}{LC} = 0 \quad (\text{characteristic eqn})$$

$$\alpha = \frac{1}{2RC}, \omega_0 = \frac{1}{\sqrt{LC}}, \quad (\alpha = \frac{R}{2L} \text{ in series case}).$$

$$s^2 + 2\alpha s + \omega_0^2 = 0 \Rightarrow s_1 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$


$\omega < \omega_0$

$\omega = \omega_0$

$\omega > \omega_0$

$Q \neq \frac{R}{2L}$
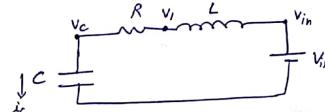
$$Q = R \sqrt{\frac{C}{L}} \quad (Q = \frac{1}{R} \sqrt{\frac{E}{C}} \text{ in series case}).$$



$$\frac{d^2V_C}{dt^2} + \frac{V_C - V_i}{R} = 0 \Rightarrow V_i = RC \frac{dV_C}{dt} + V_C.$$

$$\frac{V_i - V_C}{R} + \frac{1}{L} \int_{-\infty}^t (V_i - V_C) dt' = 0 \quad \leftarrow \text{Put } V_i.$$

$$\Rightarrow \frac{1}{R} \left( \frac{dV_i}{dt} - \frac{dV_C}{dt} \right) + \frac{1}{L} (V_i - V_C) = 0$$

$$\Rightarrow \frac{1}{R} \left( RC \frac{dV_C}{dt} + \frac{dV_C}{dt} - \frac{dV_C}{dt} \right) + \frac{1}{L} \left( RC \frac{dV_C}{dt} + V_C - V_{in} \right) = 0$$

$$\Rightarrow \frac{d^2V_C}{dt^2} + \frac{R}{L} \frac{dV_C}{dt} + \frac{V_C - V_{in}}{LC} = 0, \quad \frac{V_C - V_{in}}{LC} = \frac{V_{in}}{LC}$$


$$V_C(t) = V_{CH}(t) + V_{CP}(t)$$

Homogeneous

$$A_1 e^{st} + A_2 e^{-st}$$


$$s^2 + 2\alpha s + \omega_0^2 = 0.$$

$$V_C(0) = 0, \quad i_L(0) = 0$$

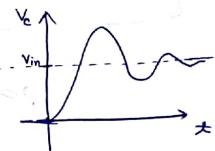

At  $t=0^+$  → voltage drop is across  $C$ .

$t=0^+ \rightarrow$  " "  $L$ .

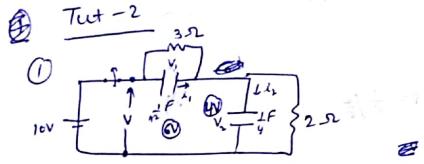

$$i_1 = -2e^{-t/0.5} \text{ Amperes}$$


$$v_1 = 6e^{-t/0.5} \text{ Volts}$$

$$v_2 = 4e^{-t/0.5} \text{ Volts}$$

$$i_2 = -2e^{-t/0.5} \text{ Amperes}$$

$$v = v_1 + v_2 = 6e^{-t/0.5}$$

Ques

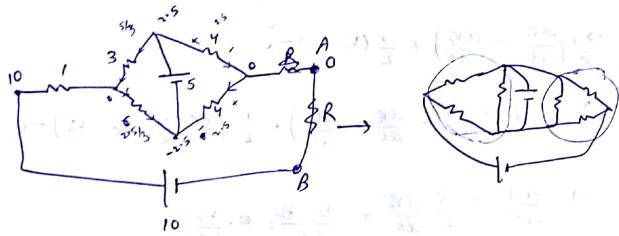

When  $R_L = R_{TH} \Rightarrow$  max. power dissipation

$$\Rightarrow R_{TH} = 5\Omega$$


$$V_{TH} = \frac{55}{6} V$$

$$P = \left( \frac{V_{TH}}{R_{TH} + R} \right)^2 R = \frac{V_{TH}^2}{4R}$$





Ques

$$i = \frac{dV}{dt} = 2A \quad \text{for } t \leq 1$$

$$= 0 \quad \text{for } t > 1$$

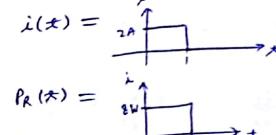

$$V_S =$$

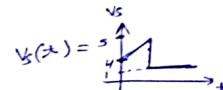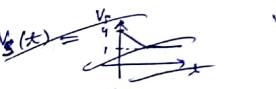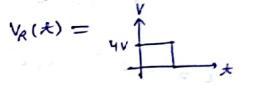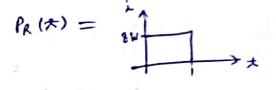


$$10V \quad 6\Omega \quad 1.5A \quad 3\Omega \quad 1A \quad 2\Omega \quad 0.5H$$

$$3\Omega \quad 0.5H \quad 1A$$

$$i(t) = I \cdot e^{-RNt}$$

$$i(t) = e^{-9t}$$

$$V(t) = L \frac{di}{dt} = -4e^{-9t}$$

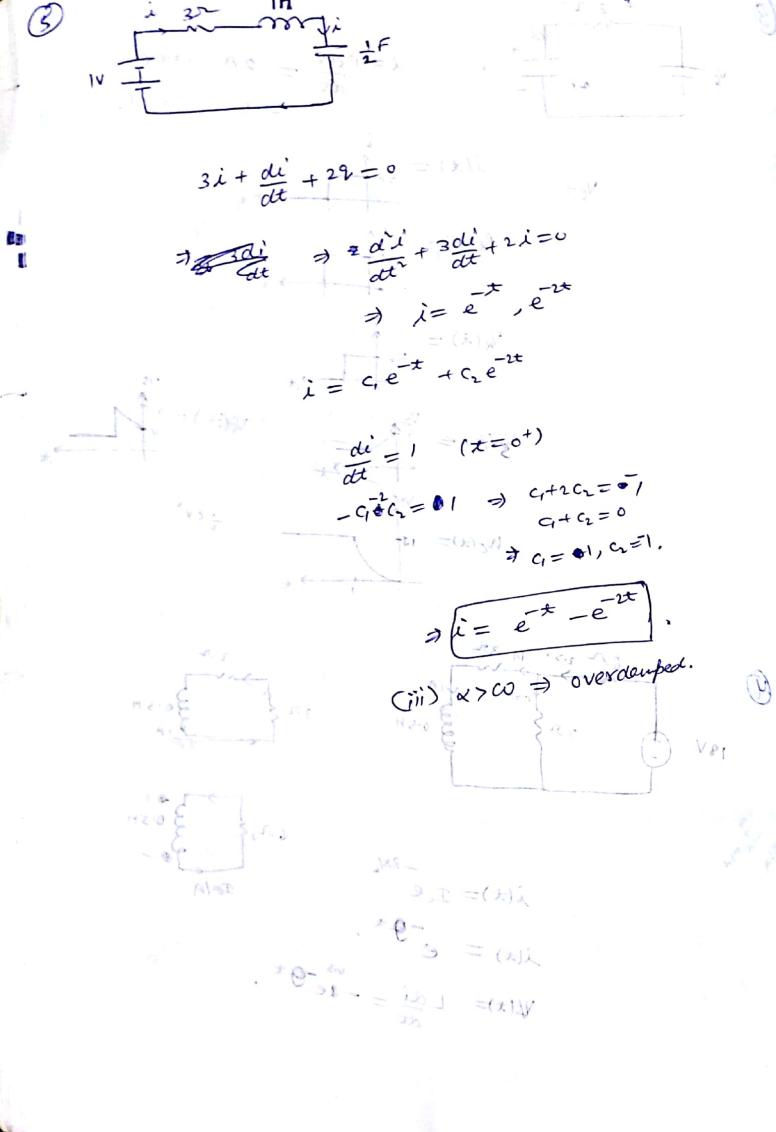

(iii)

$$\frac{V_{in} - V_C}{R} = C \frac{dV_C}{dt}$$

$$V_i(t) = V_i \cos(\omega t)$$

$$\omega: \text{angular frequency}$$

$$\text{Time period } T = 2\pi/\omega$$

$$t = \frac{1}{T} = \frac{\omega}{2\pi} \quad (\text{freq.})$$

$$V_C(t) = \frac{V_{CH}(t)}{R} + V_{CP}(t)$$

$$Ae^{-\frac{t}{RC}}$$

$$\tau = RC$$

$$\Rightarrow RC \frac{dV_C}{dt} + V_C = V_i \cos(\omega t)$$

Try:  $V_{CP}(t) = k_1 \cos(\omega t) + k_2 \sin(\omega t)$

$$\Rightarrow RCC \omega (-k_1 \sin \omega t + k_2 \cos \omega t) + (k_1 \cos \omega t + k_2 \sin \omega t) = V_i \cos \omega t$$

$$\Rightarrow k_2 = k_1 RCC \omega - \text{equating sine terms}$$

$$RCC \omega k_1 + k_1 = V_i - \text{equating cosine terms}$$

$$\Rightarrow k_1 = \frac{V_i}{1 + (RCC \omega)^2}, k_2 = \frac{V_i \omega}{1 + (RCC \omega)^2}$$

$$V_C(t) = \frac{V_i}{1 + (RCC \omega)^2} [\cos(\omega t) + (RCC \omega) \sin(\omega t)] + Ae^{-\frac{t}{RC}}$$

sinusoidal steady state

If  $V_{in} = V_i \sin \omega t = V_i \cos(\omega t \pm \pi/2)$

$$V_C(t) = \frac{V_i}{1 + (RCC \omega)^2} [\sin(\omega t) \mp RCC \omega \cos(\omega t)]$$

If  $V_{in} = \cos \omega t + k \sin \omega t$

$$V_C(t) = \text{Value to cosine} + \text{Value to sine}$$

$$V_C(t) = V_i \cos \omega t + f \sin \omega t = V_i e^{j\omega t}$$

(Euler's theorem)

$$V_o e^{j(\omega t + \phi)} = (V_o e^{j\phi}) e^{j\omega t}$$

$$V_{in} = V_i e^{j\omega t}$$

$$RC \frac{dV_c}{dt} + V_c = V_{in}$$

$$\text{Try } V_c = V_0 e^{j\omega t}$$

$$RC V_i e^{j\omega t} - (j\omega) V_0 e^{j\omega t} + V_0 e^{j\omega t} = V_{in} \Rightarrow V_i e^{j\omega t} = V_{in}$$

$$RC V_i e^{j\omega t} + V_f = V_i$$

$$V_i = \frac{V_i}{RC\omega j + 1} = \frac{V_i (RC\omega j)}{1 - (RC\omega)^2}$$

$$V_i = \frac{V_i}{1 - (RC\omega)^2} - j \frac{RC\omega V_i}{1 - (RC\omega)^2}$$

$$V_{in} = V_i (\cos \omega t + j \sin \omega t)$$

$$\text{If } V_{in} = V_i \cos \omega t = \text{real part} = \operatorname{Re}(V_i e^{j\omega t})$$

$$= \frac{V_i}{1 - (RC\omega)^2}$$

$$V_{in} = V_i \sin \omega t = \text{imaginary part} = \operatorname{Imag}(V_i e^{j\omega t})$$

$$V_{in} = \frac{V_i e^{j\omega t}}{\operatorname{Re}(V_i e^{j\omega t})}, V_{out} = \frac{V_i e^{j\omega t}}{\operatorname{Re}(V_i e^{j\omega t})} \cdot \frac{j\omega}{(j\omega)^2 + 1} = j\omega V$$

$$\text{If } V_{in} = \cos(\omega t) \Rightarrow V_i = 1$$

$$\text{If } V_{in} = \sin(\omega t) \Rightarrow V_i = -j$$

$$V_{in} = \cos(\omega t + \phi) \Rightarrow V_i = \cos(\omega t + \phi)$$

$$V_{in} = V_i (\cos \omega t + j \sin \omega t) = V_i e^{j\omega t}$$



$$v_i = a + jb = \sqrt{a^2 + b^2} e^{j\theta} \quad \theta = \tan^{-1}(b/a)$$

$$\text{Resistance: } i(t) = \operatorname{Re}[I e^{j\omega t}]$$

$$i(t) = I e^{j\omega t} = I e^{j\theta}$$

$$V(t) = \operatorname{Re}[V e^{j\omega t}]$$

$$V(t) = i(t) R \Rightarrow V_i \cos(\omega t + \theta) = RI \cos(\omega t + \theta)$$

$$\Rightarrow V_i = RI, \theta = 0$$

$$\Rightarrow \frac{V}{I} = R$$

Capacitor:-

$$i(t) = I e^{j\omega t} = (I_i e^{j\theta}) e^{j\omega t} \quad \left. \begin{array}{l} i(t) = I_i \cos(\omega t + \theta) \\ V(t) = V_i e^{j\theta} e^{j\omega t} \end{array} \right\} V(t) = V_i \cos(\omega t + \theta)$$


$$V(t) = V_i e^{j\theta} e^{j\omega t} = (V_i e^{j\theta}) e^{j\omega t} \quad \left. \begin{array}{l} V(t) = V_i \cos(\omega t + \theta) \\ I_i, V_i \rightarrow +ve \end{array} \right\}$$

⇒

$$i(t) = C \frac{dV_c}{dt} \Rightarrow I_i \cos(\omega t + \theta) = C V_i \cos(\omega t + \theta) = C V_i \cos(\frac{\pi}{2} + \omega t + \theta)$$

$$\Rightarrow I_i = C V_i \cos(\frac{\pi}{2} + \omega t + \theta)$$
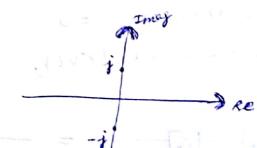
$$\frac{V}{I} = \frac{V_i e^{j\theta}}{I_i e^{j\theta}} = \frac{1}{C \cos(\frac{\pi}{2} + \omega t + \theta)} = \frac{1}{j\omega C}$$



Inductor:-


$$V = L \frac{di}{dt} \Rightarrow \frac{V}{I} = j\omega L \quad \left. \begin{array}{l} I = I e^{j\omega t} \\ V = V e^{j\theta} = L I (j\omega) e^{j\omega t} \end{array} \right\} \frac{V}{I} = j\omega L$$

$$\frac{\bar{V}}{\bar{I}} = \text{complex impedance} = z_1 + z_2$$

$z = R$  - resistor

$$z = \frac{1}{j\omega C} - \text{capacitor}$$

$$z = j\omega L - \text{inductor}$$

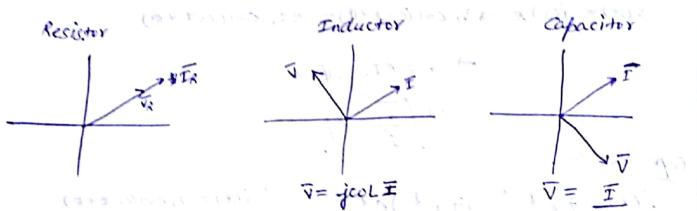

$$\begin{aligned} \bar{I} &= \text{real part of } \bar{I} \\ \bar{I} &= I_0 \cos(\omega t) \Rightarrow \bar{I} = I_0 e^{j\omega t} \\ V &= \omega(j\omega L) \bar{I} = e^{j\omega t} \\ &= I_0 j\omega L \cos(\omega t) \\ &= -I_0 j\omega L \sin(\omega t). \end{aligned}$$



$$V_1(x) + V_2(x) + V_3(x) = 0$$

$$V_1 + V_2 + \dots = 0 \quad (\text{KVL}).$$

$$\bar{V}_{z_1} = \bar{I} z_1, \quad \bar{V}_{z_2} = \bar{I} z_2 \quad \bar{V}_z = \bar{I}(z_1 + z_2)$$

$$\bar{I}_1 + \bar{I}_2 + \bar{I}_3 + \bar{I}_4 = 0 \quad (\text{KCL}).$$

$$\begin{aligned} \bar{I}_{z_1} &= \frac{\bar{V}}{z_1}, \quad \bar{I}_{z_2} = \frac{\bar{V}}{z_2} \\ \bar{I} &= \bar{I}_{z_1} + \bar{I}_{z_2} = \bar{V} \left( \frac{1}{z_1} + \frac{1}{z_2} \right) \Rightarrow \frac{1}{z} = \frac{1}{z_1} + \frac{1}{z_2}. \end{aligned}$$

$$\bar{I}_{z_1} = \frac{\bar{V}}{z_1}, \quad \bar{I}_{z_2} = \frac{\bar{V}}{z_2}$$

$$\bar{I} = \bar{I}_{z_1} + \bar{I}_{z_2} = \bar{V} \left( \frac{1}{z_1} + \frac{1}{z_2} \right) \Rightarrow \frac{1}{z} = \frac{1}{z_1} + \frac{1}{z_2}$$

$$\bar{I} = \bar{I}_{z_1} + \bar{I}_{z_2}$$

$$\frac{1}{z} = \frac{1}{z_1} + \frac{1}{z_2} \Rightarrow \frac{1}{z} = \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2}$$

$$\frac{1}{z} = \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} \Rightarrow \frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow C = C_1 + C_2$$

$$\frac{1}{C} = \frac{1}{z} = j\omega C_1 + j\omega C_2 = j\omega(C_1 + C_2)$$

$$\frac{1}{C} = \frac{1}{z} = j\omega C_1 + j\omega C_2 \Rightarrow C = C_1 + C_2$$

$$\bar{V}_s \xrightarrow{R} \frac{1}{j\omega C} \Rightarrow z = R + \frac{1}{j\omega C} = \frac{1 + j\omega RC}{j\omega C}$$

$$\bar{I} = \frac{\bar{V}_s}{z} = \frac{\bar{V}_s j\omega C}{1 + j\omega RC} = \frac{\bar{V}_s (j\omega C)(1 - j\omega RC)}{1 + \omega^2 R^2 C^2}$$

$$R = 1 \Omega, \omega C = 1 \Omega$$


$$z = 1 + \frac{1}{j} = (1 - j) \Omega$$

$$\bar{I} = \frac{\bar{V}_s}{1 - j} = \frac{\bar{V}_s (1 + j)}{2} \Rightarrow \bar{V}_s = \bar{I} (1 - j)$$

$$\bar{V}_s = (\sqrt{2} \bar{I}) \left( \frac{1 - j}{\sqrt{2}} \right) e^{-j\pi/4}$$


$$\bar{V}_s = (\sqrt{2} \bar{I}) \left( \frac{1 - j}{\sqrt{2}} \right) e^{-j\pi/4}$$
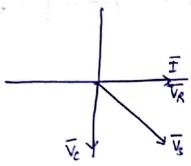
$$\bar{V}_c = \bar{I} Z_c = \bar{I} \frac{1}{j\omega C} = -j\bar{I}$$



$$\bar{V}_c + \bar{V}_s = \bar{V}_s$$

Thevenin's theorem:-

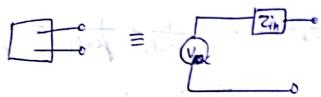

Find out  $V_{oc}$ .

$$Z = \frac{1}{j\omega C} + j\omega L + R \\ = j(\omega L - \frac{1}{\omega C}) + R.$$

$$\bar{V}_{oc} = \frac{\bar{V}_{in}}{Z} \cdot (j\omega L + R).$$

$$Z_{in} = \frac{1}{j\omega C} \parallel (R + j\omega L).$$

Power:-

$$i(t) = I \cos(\omega t + \phi) \rightarrow \bar{I} = I e^{j\phi}$$

$$\cos x \cos \beta = \frac{1}{2} [\cos(x-\beta) + \cos(x+\beta)]$$

$$\text{If } V(t) i(t) = VI \cos(\omega t + \phi) \cos(\omega t + \theta)$$

$$P(t) = VI \cdot \frac{1}{2} [\cos(\phi-\theta) + \cos(\omega t + \theta + \phi)].$$

$$\langle P(t) \rangle = \frac{1}{2} VI \cos(\phi - \theta), = \frac{1}{2} \operatorname{Re}(V \bar{I}^*) = \frac{1}{2} \operatorname{Re}(V^* \bar{I})$$


Pavg

$I^*$  → conjugate


$$\phi = 0 \Rightarrow P_{avg} = \frac{1}{2} VI$$

$$\phi = 90^\circ \Rightarrow P_{avg} = 0$$
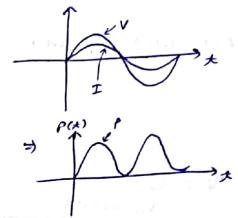
$$\phi = -90^\circ \Rightarrow P_{avg} = 0$$




$$P_{avg} = \frac{1}{2} |I| \operatorname{Re}(z) = \frac{1}{2} \frac{|V|^2}{\operatorname{Re}(z)}.$$

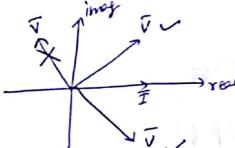

$\bar{V}$  &  $\bar{I}$  angle can be at max  $90^\circ$ .

Maximum Power transfer:-

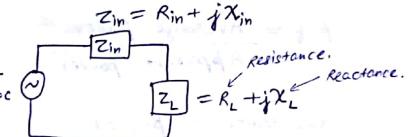

$$\bar{I} = \frac{\bar{V}_{oc}}{Z_{in} + Z_L}$$

$$\bar{V}_L = \frac{\bar{V}_{oc}}{Z_{in} + Z_L} \cdot Z_L$$

$$P_L = \frac{1}{2} \operatorname{Re}(\bar{V}_L \bar{I}^*) = \frac{1}{2} \operatorname{Re}\left(\frac{|\bar{V}_{oc}|^2}{(Z_{in} + Z_L)(Z_{in}^* + Z_L^*)}\right)$$

$$= \frac{1}{2} |\bar{V}_{oc}|^2 \frac{R_L}{(R_{in} + R_L)^2 + (X_{in} + X_L)^2} \rightarrow 0 \text{ for max. power}$$

$$\frac{\partial}{\partial R_L} \left( \frac{R_L}{(R_{in}+R_L)^2} \right) = 0 \Rightarrow \frac{2(R_{in}+R_L) \cdot R_L - (R_{in}+R_L)^2}{(R_{in}+R_L)^4} = 0$$

$$\Rightarrow R_{in} = R_L$$

For max. power along  $Z_L$ :  $R_L = R_{in}$

$$Z_L = Z_{in}^*$$

$$V = V_o = V_o \cos \omega t$$

$$\text{RMS value: } \sqrt{\frac{1}{T} \int_0^T V_o^2 \cos^2 \omega t dt} = \sqrt{\frac{1}{2} V_o^2 T} = V_o / \sqrt{2}$$

$$P_{avg} = \frac{1}{2} V I \cos(\theta)$$

$$= V_e I_e \cos(\theta)$$

Apparent power

$$\text{p.f.} = \frac{\text{Average power}}{\text{Apparent power}}$$



$$\theta = \text{p.f. angle.}$$

Resistance - p.f. = 1

Inductor/capacitor - p.f. = 0.


$\theta > 0$  - Inductive load (lagging)

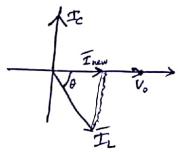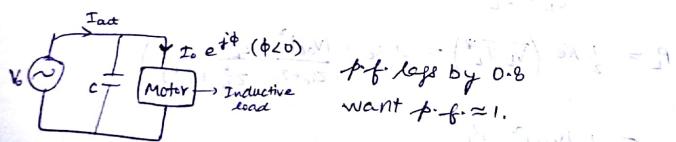$\theta < 0$  - capacitive load (leading)



$|I_{out}|$  less

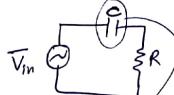Power through motor remains same but  $I_{out}$  decreases. We can reduce power loss in transmission wires. ( $I \downarrow, I^2 R \downarrow$ ).





$$I = \frac{V_{in}}{R + \frac{1}{j\omega C}}$$

$$V_R = \pm \frac{V_{in}}{R + \frac{1}{j\omega C}} \cdot R$$

$$H(\omega) = \frac{V_R}{V_{in}} = \frac{R}{1 + \frac{1}{j\omega RC}} = \frac{j\omega RC}{1 + j\omega RC}$$
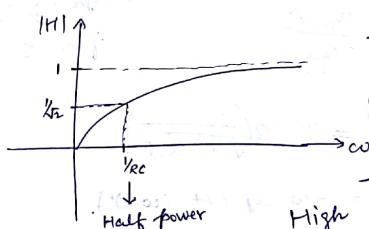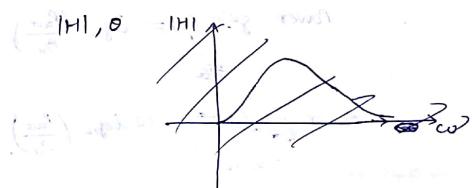
$$\Rightarrow H(\omega) = \frac{j\omega RC (1 - j\omega RC)}{(1 + j\omega RC)^2} = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}} e^{j\omega RC}$$




High pass filter  
(co large passes)


$$V_o = \left(\frac{1}{j\omega C}\right) \cdot V_{in}$$

$$H = \frac{1}{1+j\omega RC} = \left(\frac{V_o}{V_{in}}\right)$$
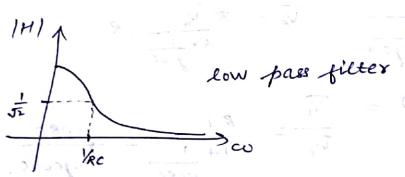
$$\tan \theta = \frac{Im}{Re} = -\omega RC.$$



$$|H| = \left|\frac{V_o}{V_{in}}\right| = \text{Voltage gain}$$

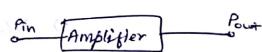

$$\text{Power gain (B)} = \log_{10} \left( \frac{P_{out}}{P_{in}} \right)$$

see

$$\text{Power gain (dB)} = 10 \log_{10} \left( \frac{P_{out}}{P_{in}} \right)$$

decibel

$$P_{in} = \frac{|V_{in}|^2}{2R_{in}}, P_{out} = \frac{|V_{out}|^2}{2R_{out}}$$


load

$$= 20 \log_{10} \left( \frac{|V_{out}|}{|V_{in}|} \right)$$

if  $R_{in} = R_{out}$ .

$$\text{gain (dB)} = 20 \log \left| \frac{V_o}{V_{in}} \right| = 20 \log \left( \frac{1}{\sqrt{1+(\omega RC)^2}} \right)$$

$$= -10 \log (1 + (\omega RC)^2).$$

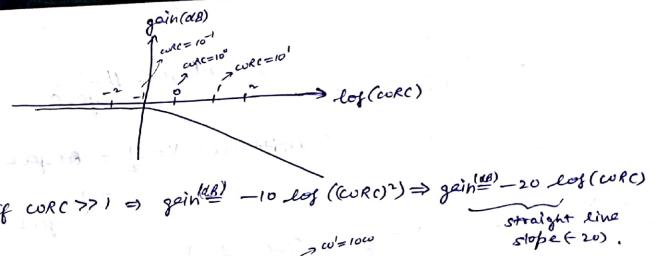

If  $\omega RC \gg 1 \Rightarrow \text{gain} = -10 \log ((\omega RC)^2) \Rightarrow \text{gain} = -20 \log (\omega RC)$

slope =  $-20 \text{ dB/decade}$   
decade: freq. change by factor of 10.

$$\text{If } \omega' = 10 \omega \\ \text{gain}' = -20 \log (10 \omega) \\ = -20 - 20 \log (\omega) = -20 + \text{gain}.$$

$$\text{slope} = 6.02 \text{ dB/octave}$$

$$\text{gain}' = -20 \log (2\omega) \\ = -20 \log^2 - 20 \log \omega = -6.02 + \text{gain}.$$

Tut-3

$$\textcircled{1} \quad V_e = 220 \text{ V}, f = 60 \text{ Hz}, I_e = 20 \text{ A}, \cos \theta = 0.75 \text{ (lagging)}$$

$$\textcircled{2} \quad P_{avg} = V_e I_e \cos \theta = 220 \times 20 \times 0.75 = 3300 \text{ W.}$$

$$\textcircled{3} \quad \text{reactive part} = V_e I_e \sin \theta$$

$$P_{avg} = \frac{V_e^2}{R_{eff}} \text{ Re} \left( \frac{1}{z} \right), \quad P_{avg} = \frac{V_e^2}{R_{eff}} \text{ Re} \left( \frac{1}{z} \right).$$

$$P_{avg} = \frac{V_e^2}{R_{eff}} \text{ Re} \left( \frac{1}{z} \right), \quad \frac{\text{Im}(z)}{\text{Re}(z)} = \sin \theta$$

$$\Rightarrow \text{Im}(z) = \text{Re}(z) \sin \theta \\ \Rightarrow V_e^2 \sin \theta = \frac{P_{avg}}{\text{Re}(z)}$$


$$\text{Im}(z) = 0 \Rightarrow \text{Im} \left( \frac{1}{z_1} + \frac{1}{z_2} \right) = 0$$

$$\Rightarrow j\omega C + \frac{1}{jL + R + j\omega C} = 0$$

$$\omega C \left( \frac{-jL\omega - j\omega^2 C + 1}{R + j\omega C} \right) = 0$$

$$\omega C \left( \frac{-jL\omega - j\omega^2 C + 1}{R + j\omega C} \right) = 0$$
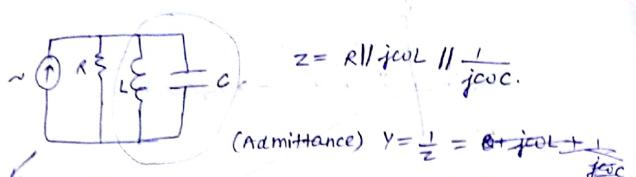
$$\omega C \left( \frac{-jL\omega - j\omega^2 C + 1}{R + j\omega C} \right) = 0$$



$$Z = R \parallel j\omega L \parallel \frac{1}{j\omega C}$$



$$(Admittance) Y = \frac{1}{Z} = \frac{1}{R} + j\omega L + \frac{1}{j\omega C}$$

$$Q = R \sqrt{\frac{C}{L}}$$

$$Y = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$

$$\bar{V} = \frac{\bar{I}}{Y}$$
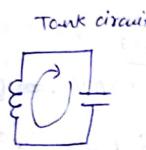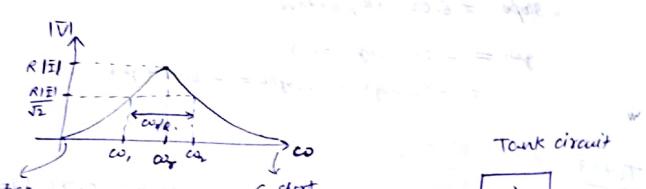
$$At \omega = \omega_r, \omega_r = \frac{1}{\sqrt{LC}}, \text{ resistance}$$



$Z = \infty$  at  $\omega = \omega_r$ .

$$Y = \frac{1}{R} \oplus \left( 1 + jR \left( \frac{\omega_r}{\omega} - \frac{1}{\omega \omega_r} \right) \right)$$

Need  $R \left( \omega_r - \frac{1}{\omega_r} \right) = \pm 1$ , for  $M = \frac{\sqrt{2}}{R}$  (half-power points)

$$R \left( \omega_r - \frac{1}{\omega_r} \right) = +1 \Rightarrow \omega_r^2 RLC - \omega_r L C - R = 0.$$

$$\Rightarrow \omega_r = \frac{\omega_r + \sqrt{\omega_r^2 + 4R^2 C^2}}{2RLC}$$


$$\Rightarrow \omega_r = \frac{1}{2RC} \pm \sqrt{\frac{1}{(2RC)^2} + \frac{1}{LC}}$$

$$\frac{\omega_r}{Q} = \frac{1}{\sqrt{LC}} \cdot \sqrt{\frac{L}{C}} \cdot \frac{1}{R} = \frac{1}{R C}$$

$$\omega = \frac{\omega_r}{2Q} \oplus \omega_r \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \Rightarrow \omega_2 = \frac{\omega_r}{2Q} + \omega_r \sqrt{\left(\frac{1}{2Q}\right)^2 + 1}$$

$$\omega_1 = -\frac{\omega_r}{2Q} + \omega_r \sqrt{\left(\frac{1}{2Q}\right)^2 + 1}$$

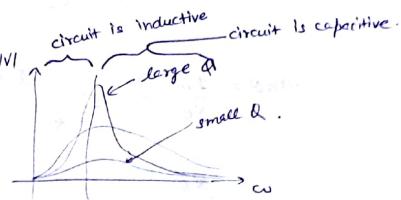
$$BW = \omega_2 - \omega_1 = \frac{\omega_r}{Q}$$



$Q = \frac{\omega_r}{B.W.}$  = selectivity of circuit.

$$At \omega = \omega_r, I_L = \frac{V}{Z_L} = \frac{IR}{j\omega_r L}, \omega_r = \frac{1}{\sqrt{LC}}$$


$$|I_L| = |I| R \sqrt{\frac{C}{L}} = Q |I|$$

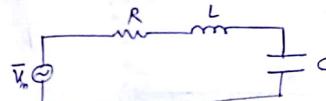

$$Z = R + j\omega L + \frac{1}{j\omega C}, I = \frac{\bar{V}_{in}}{Z}, \bar{V}_R = \frac{\bar{V}_{in}}{Z} \cdot R$$

$$\Rightarrow \bar{V}_R = \frac{\bar{V}_{in} \cdot R}{R + j(\omega L - \frac{1}{\omega C})}$$
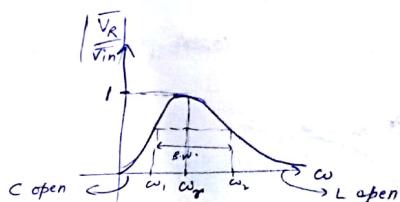
$$At \omega = \omega_R = \frac{1}{\sqrt{LC}}$$



$$BW = \omega_2 - \omega_1 = \omega_r/Q$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$



$$H = \frac{V_R}{V_{in}} = \frac{R}{R + j(\omega L - \frac{1}{\omega C})}$$

$$= \frac{R(R - j(\omega L - \frac{1}{\omega C}))}{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$\tan \theta = \frac{Im}{Re} = \frac{\frac{1}{\omega C} - \omega L}{R}$$

$$\text{If } \omega \rightarrow 0 \Rightarrow \tan \theta = \frac{1}{\omega R C}$$
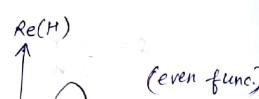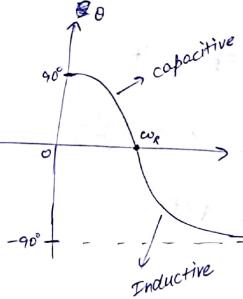
$$\omega \rightarrow \infty \Rightarrow \tan \theta = -\frac{\omega L}{R}$$




$$Re(H) = \frac{R^2}{R^2 + (\omega L - \frac{1}{\omega C})^2}$$


$$Im(H) = \frac{R \omega (\frac{1}{\omega C} - \omega L)}{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

Inductive


(odd func)

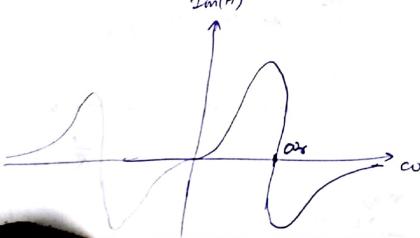
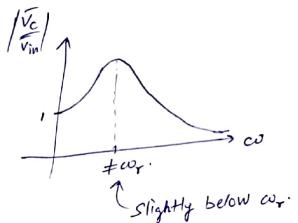
$$H' = \frac{V_C}{V_{in}} = \frac{\frac{1}{j\omega C}}{R + j(\omega L - \frac{1}{\omega C})}$$



$$\text{at } \omega_0 = \omega_r \\ |H'| = Q.$$

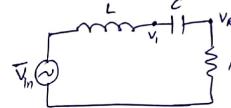

$$\bar{I} = \frac{\bar{V}_{in}}{R + j(L\omega - \frac{1}{\omega C})}$$

$$\bar{V}_R = \bar{I}R = \bar{V}_{in} \cdot \frac{R}{R + j(\omega L - \frac{1}{\omega C})}$$

$$\frac{V_R}{R} + C \frac{d}{dt} (V_R - V_i) = 0 \quad \text{(i)}$$

$$\frac{1}{L} \int_{-\infty}^t (V_t - V_{in}) dt' + C \frac{d}{dt} (V_i - V_R) = 0 \quad \underbrace{V_R / R}_{V_R / R}$$

$$\Rightarrow \frac{1}{L} (V_i - V_{in}) + \cancel{\frac{dV_R}{dt}} = 0 + \frac{1}{R} \frac{d}{dt} (V_R) = 0.$$

$$\Rightarrow \frac{1}{L} \frac{dV_i}{dt} + \cancel{\frac{1}{R} \frac{d^2 V_R}{dt^2}} = 0 \quad \text{use } \frac{dV_{in}}{dt} = \frac{V_R}{RC} + \frac{dV_R}{dt}. \quad \text{diff.}$$

$$\frac{dV_R}{dt^2} + \frac{R}{L} \frac{dV_R}{dt} + \frac{1}{LC} V_R = \frac{R}{L} \frac{dV_{in}}{dt}.$$

Assume:  $e^{j\omega t}$ .


$$(-\omega^2 + \frac{R}{L}j\omega + \frac{1}{LC}) V_R = \frac{R}{L} j\omega V_{in}$$

$$V_R = \left( \frac{j\omega R}{L} \right) V_{in} \cdot \frac{1}{-\omega^2 + \frac{R}{L}j\omega + \frac{1}{LC}} = \frac{R V_{in}}{\cancel{+j\omega L + R + \frac{1}{j\omega C}}} \quad \text{H}(\omega)$$

$$e^{st} s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \quad (\text{if } V_{in} = 0)$$

$$s = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}}{2}$$

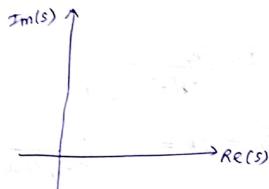
$$H(s) = \frac{\left(\frac{SR}{L}\right)}{(s-s_1)(s-s_2)}$$



$$\delta(x) = \frac{1}{2\pi} \int_{-\infty}^{\infty} e^{j\omega t} d\omega \quad (\text{Fourier transform})$$

$$H(t) = \frac{1}{2\pi} \int H(\omega) e^{j\omega t} d\omega$$
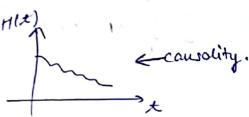
$$H(\omega) = \int_{-\infty}^{\infty} H(t) e^{-j\omega t} dt$$




$$\frac{dV_o}{dt} = -\omega^2 V_o$$

$$\sqrt{V_o^2 + V_o'^2} = \sqrt{V_o^2 + \omega^2 V_o^2} = \sqrt{1 + \omega^2} V_o$$



$$V_o = V_o \sqrt{1 + \omega^2} \cos(\omega t + \phi)$$

Op. Amp. (Operational amplifier):

Active element


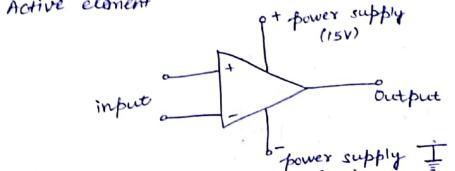


$$V_o = A(V_+ - V_-) \quad (10^5)$$

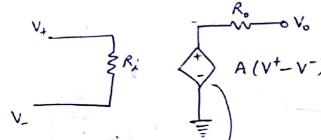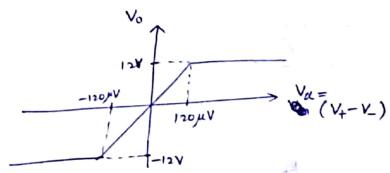

Voltage controlled  
Dependent voltage source
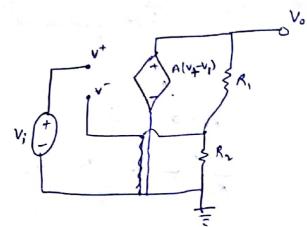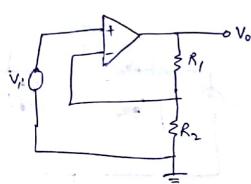
$$\begin{cases} R_i \approx 2M\Omega & \rightarrow \text{almost open.} \\ R_f \approx 75\Omega & \rightarrow \text{almost short.} \\ A \approx 10^5 & \end{cases}$$



$$V_o = \frac{AV_+}{1 + AR_2} \quad (1 + AR_2 \gg 1)$$


$$\begin{aligned} V_+ &= V_+ - (1) \\ \frac{V_- + V_o - V_o}{R_2} &= 0 - (ii) \\ V_- &= \frac{R_2 V_o}{R_1 + R_2}, \quad V_o = A(V_+ - V_-) - (iii) \end{aligned}$$

$$A \text{ is very large} \Rightarrow V_o = \frac{AV_i}{1 + AR_i} = \frac{V_i}{R_i + R_2}$$

$$\Rightarrow V_o = \left( \frac{R_1 + R_2}{R_2} \right) V_i$$

$$\Rightarrow \boxed{V_o = \left( 1 + \frac{R_1}{R_2} \right) V_i}$$

$$\text{Gain} = 1 + \frac{R_1}{R_2}$$

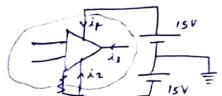


B

$$R_{in} \rightarrow \infty$$

$$R_o \rightarrow 0$$

$$A \rightarrow \infty$$

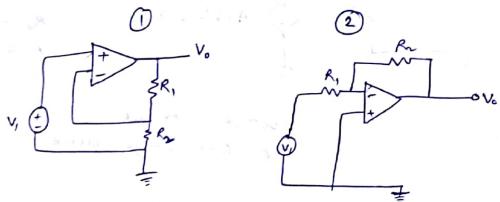

(-ve feedback)


$$V_+ = 0 \quad \text{(i)}$$

$$\frac{V_i - V_-}{R_1} = \frac{V_- - V_o}{R_2} \quad \text{(ii)}$$

$$V_o = A(V_+ - V_-) \quad \text{(iii)}$$


$$\Rightarrow V_o = \frac{-AR_2/(R_1 + R_2)}{1 + \left( \frac{AR_1}{R_1 + R_2} \right)} \Rightarrow \boxed{V_o = -\frac{R_2}{R_1} V_i}$$
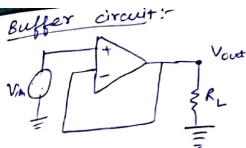
$$\begin{matrix} R_1 \\ R_2 \\ R_{in} \\ R_{out} \end{matrix}$$



$$V_{out} = V_{in}$$

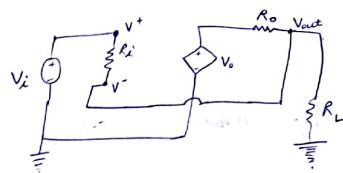$V_{in}$  does not supply any current. All current comes from power source.



$$V_o = A(V^+ - V^-)$$

$$\frac{V_{out}}{R_L} + \frac{V_{out} - V_o}{R_o} + \frac{V^+ - V^-}{R_i} = 0$$

$$V_o = A(V^+ - V^-), \quad V^+ = V_i, \quad V^- = V_{out}$$

$$V_{out} \left( \frac{1}{R_L} + \frac{1+A}{R_o} + \frac{1}{R_i} \right) = V_{in} \left( \frac{1}{R_i} + \frac{A}{R_o} \right)$$

$$\boxed{V_{out} = V_{in} \frac{(R_o + A R_i) R_L}{R_i R_o + R_L R_i (1+A) + R_L R_o}}$$

$$\frac{R_o + A R_i}{R_i R_o + R_L R_i (1+A) + R_L R_o} = \frac{1}{R_{TH} + R_L}$$

$$R_{TH}(R_o + A R_i) = R_o P_o + R_i P_L$$

$$R_{TH} = R_i(R_o + A R_i)$$

$$R_{TH} = \frac{R_o + R_i}{1 + A}$$


$$\rightarrow A \rightarrow \infty \Rightarrow V_{out} = \frac{A R_i R_L}{R_i R_o + A R_i} V_{in} \Rightarrow \boxed{V_{out} = V_{in}}$$

$$i = \frac{V_{in} - V_{out}}{R_i}$$


$$V_{out} \approx \frac{A}{1+A} V_{in}$$

$$V_{in} - V_{out} = \frac{1}{1+A} V_{in}, \quad \Rightarrow i = \frac{1}{1+A} \frac{V_{in}}{R_i}$$

$$\Rightarrow R_{in} = A R_i$$

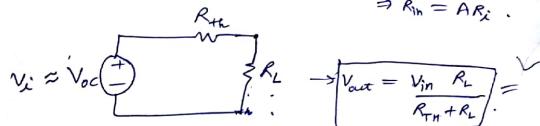
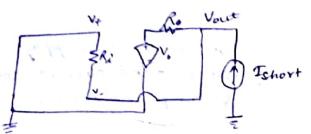
$$\boxed{V_{out} = \frac{V_{in} R_L}{R_{TH} + R_L}}$$



$$\Rightarrow \frac{V_{out} - V_+}{R_i} + \frac{V_{out} - V_o}{R_o} = I$$




$$V_o = A(V_+ - V_-) = A(0 - V_-) = -AV_{out}$$

$$\Rightarrow \frac{V_{out}}{R_i} + \frac{V_{act} + AV_{out}}{R_o} = I$$

$$\Rightarrow I = V_{out} \left( \frac{1}{R_i} + \frac{1+A}{R_o} \right)$$

$$R_{TH} = \frac{V_{out}}{I_{short}}$$
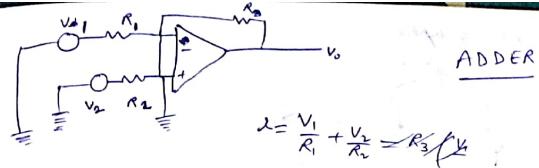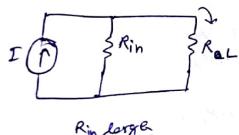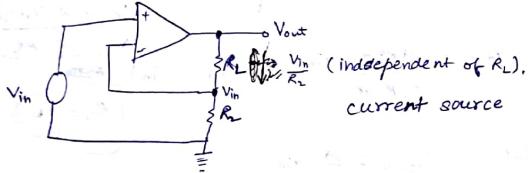
$$\Rightarrow R_{TH} = \frac{R_o R_i}{R_o + R_i(1+A)} \approx \frac{R_o}{A}$$




$$I = \frac{V_1}{R_1} + \frac{V_2}{R_2} = R_3^{-1}$$

$$V_o = -R_3 \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

If  $R_1 = R_2$

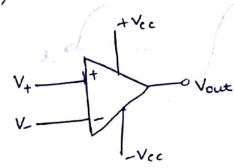
$$\Rightarrow V_o = -\frac{R_3}{R_1} (V_1 + V_2)$$



$V_+ > V_-$ ,  $V_{out} = V_{cc}$ .

$V_+ < V_-$ ,  $V_{out} = -V_{cc}$ .

### Schmitt trigger

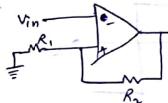


Assume  $V_{out} = +V_{cc}$ .

$$\Rightarrow V_+ = BV_{cc} \quad (B = \frac{R_1}{R_1 + R_2})$$

$\Rightarrow$  If  $V_{in} < BV_{cc}$  (OK)

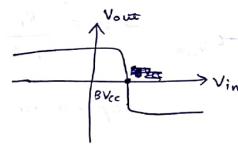
If  $V_{in} > BV_{cc}$ ,  $V_{out} = -V_{cc}$ .






Assume  $V_{out} = -V_{cc} \Rightarrow V_+ = -BV_{cc}$

If  $V_{in} < -BV_{cc} \Rightarrow V_{out} = +V_{cc}$ .

$V_{in} > -BV_{cc} \Rightarrow$  (OK)

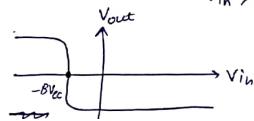

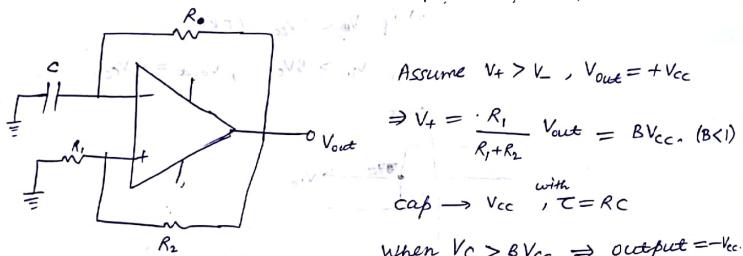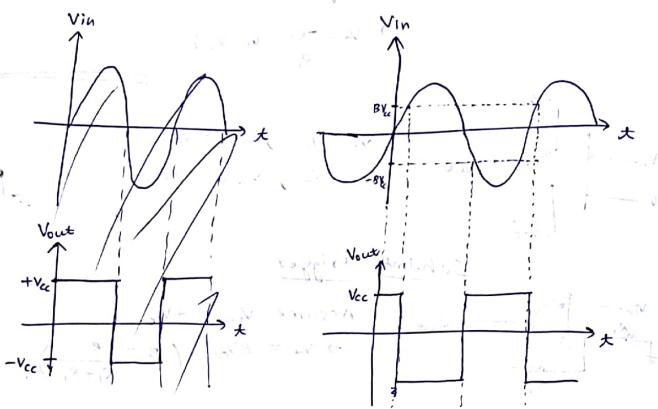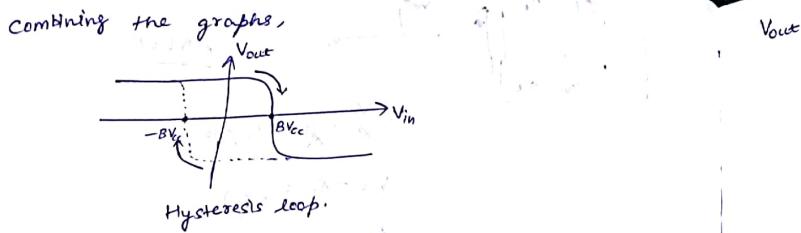

A stable device  
(oscillator).

$T = ?$

$$V_c = V_-(t) = V_{cc} + A e^{-t/Rc}$$

$$At t=0, V_-(0) = V_{cc} + A = -BV_{cc}$$

$$\Rightarrow A = -(1+B)V_{cc}$$

$$V_L(t) = V_{cc} - (1+B)V_{cc} e^{-t/Rc}$$

$$V_-(t) = V_{cc} - (1+B)V_{cc} e^{-t/Rc} = BV_{cc}$$

$$\Rightarrow V_{cc} - (1+B)V_{cc} e^{-T/RC} = BV_{cc}$$

$$\Rightarrow e^{-T/RC} = \frac{(1-B)}{1+B}$$


$$\Rightarrow T = 2RC \ln\left(\frac{1+B}{1-B}\right) B = \frac{R}{R_1 + R_2}$$

$$\frac{V_{out} - V_c}{R} = i = \frac{CdV_c}{dt}$$


$$-\frac{dt}{RC} = \ln(V_{out} - V_c)$$

$$V_{out} = V_c + A e^{-t/Rc}$$

## Op-amp

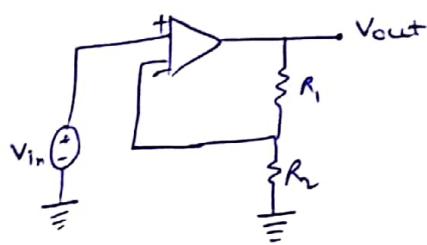

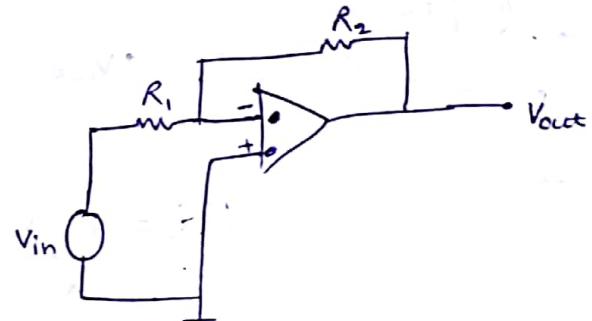
$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$



$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

Input current = 0.


Virtual short b/w  $V_+$  &  $V_-$ .

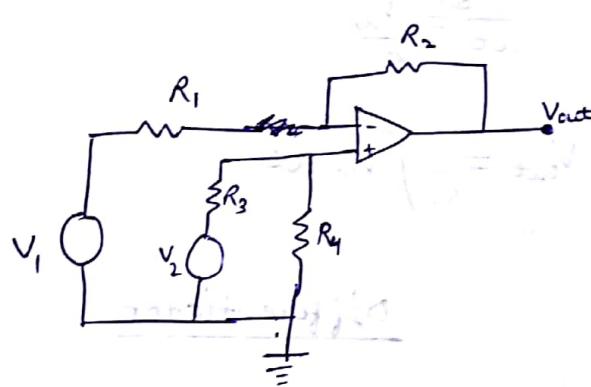

Put  $V_2 = 0$

$$V_{out,1} = -\frac{R_2}{R_1} V_1$$

Put  $V_1 = 0$

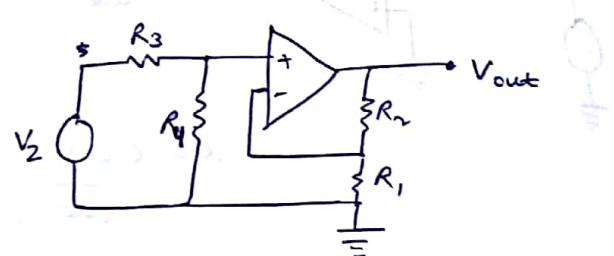


$$V_{out,2} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_2$$

Let  $R_3 = R_1$ ,  $R_4 = R_2$

$$V_{out,2} = \frac{R_2}{R_1} V_2$$

$$V_{out} = V_{out,1} + V_{out,2}$$
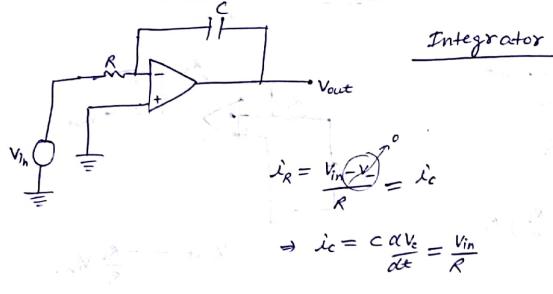
$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$




Integrator

$$V_C = -V_{out}$$


$$\Rightarrow -C \frac{dV_{out}}{dt} = \frac{V_{in}}{R}$$
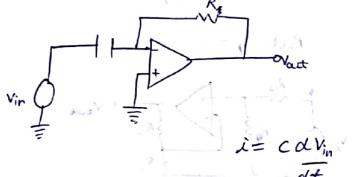
$$\Rightarrow V_{out} = -\frac{1}{RC} \int V_{in} dt$$



Differentiator
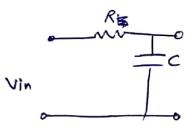
$$V_{out} = -Ri = -RC \frac{dV_{in}}{dt}$$




Low-pass filter

$$V_{out} = \frac{V_{in}}{R + \frac{1}{j\omega C}}$$

$$\Rightarrow V_{out} = \frac{V_{in}}{1 + j(\omega/\omega_0)} = \frac{V_{in}}{1 + j(\omega/\omega_0)}$$
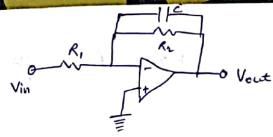
$$\omega_0 = \frac{1}{RC} = \text{cutoff freq.}$$




Low-pass filter

$$V_{out} = -\frac{Z_2}{Z_1} \cdot V_{in} = -\left( \frac{R_2 || \frac{1}{j\omega C}}{R_1} \right) \cdot V_{in}$$

$$= -\frac{1}{R_1} \left( \frac{\frac{1}{j\omega C}}{R_2 + \frac{1}{j\omega C}} \right) V_{in}$$
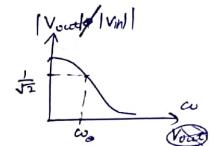
$$\Rightarrow V_{out} = -\frac{R_2}{R_1} \left( \frac{1}{1 + j(\omega/\omega_0)} \right) V_{in}, \quad \omega_0 = \frac{1}{R_2 C} = \text{cutoff freq.}$$




High-pass filter

$$V_{out} = \frac{V_{in}}{R + \frac{1}{j\omega C}} = \frac{V_{in}}{1 + \frac{1}{j\omega RC}}$$

$$\Rightarrow V_{out} = \frac{V_{in}}{1 - j(\omega/\omega_0)}, \quad \omega_0 = \frac{1}{RC}$$

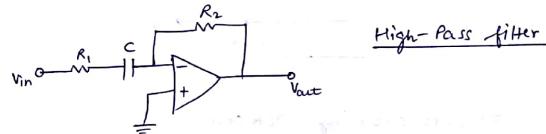
$$\Rightarrow V_{out} = \frac{j(\omega/\omega_0)}{1 + j(\omega/\omega_0)} \cdot V_{in}$$



High-Pass filter

$$V_{out} = -\frac{Z_2}{Z_1} V_{in} = -\frac{R_2}{R_1 + \frac{1}{j\omega C}} \cdot V_{in} = -\frac{R_2}{R_1} \left( \frac{j\omega C R_1}{1 + j\omega C R_1} \right)$$
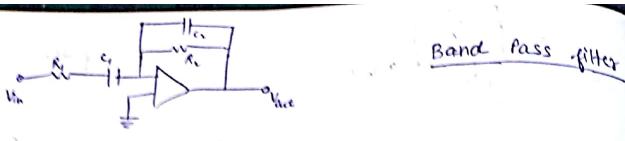
$$\Rightarrow \omega_0 = \frac{1}{R_1 C}$$




$$V_{out} = -\frac{R_2}{R_1} V_{in} = \frac{(R_2 || \frac{1}{j\omega C_2})}{(R_1 + \frac{1}{j\omega C_1})} V_{in}$$

$$V_{out} = -\frac{R_2}{R_1} \frac{\frac{1}{j\omega C_2}}{\left(\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2}\right) \left(R_1 + \frac{1}{j\omega C_1}\right)} V_{in}$$


$$\Rightarrow V_{out} = \frac{-R_2 \cdot j\omega C_2}{(1 + j\omega C_1 R_1)(1 + j\omega C_2 R_1)} V_{in} = -\frac{R_2}{R_1} \left[ \frac{-j\omega C_2 R_1}{(1 + j\omega C_1 R_1)(1 + j\omega C_2 R_1)} \right] V_{in}$$

Assume  $R_2 > R_1$ ,  $C_{1L} = \frac{1}{R_1 C_1}$  &  $C_{2H} = \frac{1}{R_2 C_2}$ .


### Comparator

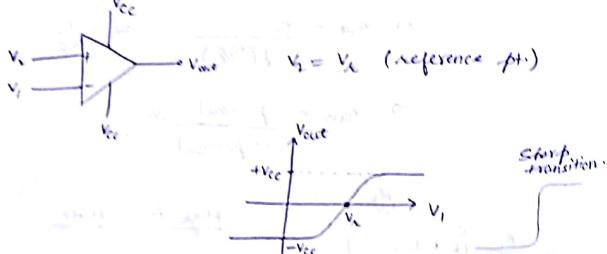

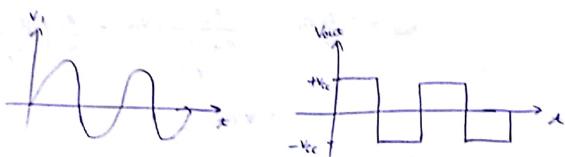If  $V_i = 0 \Rightarrow$  Zero crossing detector



### Band Pass filter

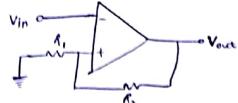


(+ve feedback)

Assume  $V_{out} = +V_{cc}$ .

$$\Rightarrow V_+ = \left( \frac{R_1}{R_1 + R_2} \right) V_{cc} = B V_{cc}.$$

If  $V_{in} < B V_{cc} \Rightarrow$  OK

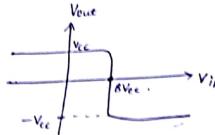If  $V_{in} > B V_{cc} \Rightarrow$  Output should be -ve.





Assume  $V_{out} = -V_{cc} \Rightarrow V_+ = -V_{cc}$ .

$$\Rightarrow V_+ = \left( \frac{R_1}{R_1 + R_2} \right) (-V_{cc})$$

$$\Rightarrow V_f = -B V_{cc}$$

If  $V_{in} > B V_{cc} \Rightarrow$  OK

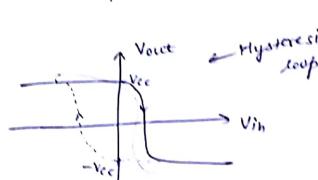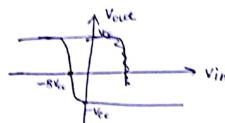If  $V_{in} < -B V_{cc} \Rightarrow$  Output = +ve.




### Semi-conductors

Metals -  
Insulators -

Metal: Cu - (2s electrons)

(Ar)  $3d^{10} 4s^1$

Free electron

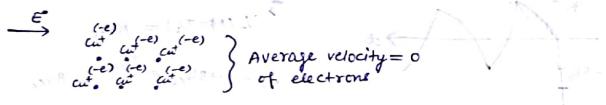

$$\frac{dp}{dt} = -eE + \bar{p} = \bar{p} = \text{avg. momentum.}$$

Time constant.

momentum lost  
due to collision, etc.

Steady state  $\Rightarrow \frac{dp}{dt} = 0$ .

$$\Rightarrow \boxed{\bar{p} = -eE\tau}$$

$$v_d = -\frac{eE\tau}{m} \Rightarrow |\frac{v_d}{E}| = \frac{e\tau}{m} = \mu \text{ (mobility)}$$

Current density :-

$J = (\text{charge density}) \times \text{velocity}$

$$J = -nev_d$$

$n = \text{density}$

$$J = \left( \frac{ne\tau}{m} \right) E \quad | \quad J = \sigma E$$

conductivity =  $\sigma$ .


$$\sigma = ne\mu.$$

Units :-

$$\mu = \frac{m \cdot m}{V} = m^2/Vs. \quad \text{common unit} = cm^2/Vs.$$

$$\sigma = \frac{1}{\Omega m} \quad f = \frac{1}{\sigma} = \Omega m. \quad (\Omega cm).$$
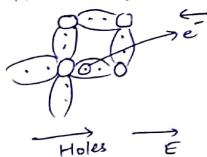
$$\rho = 10^{-4} - 10^{-6} \Omega \text{cm} \text{ (metals).}$$



Si (Ne)  $3s^2 3p^2$ .  
Ge (Ar)  $3s^2 3p^2$ .

$$\text{density of conduction } \bar{e} = n = 1.5 \times 10^{10} / \text{cm}^3 \text{ (Si)} \rightarrow n_i = 1.5 \times 10^{10} / \text{cm}^3$$

$$= 2.6 \times 10^{13} / \text{cm}^3 \text{ (Ge)}$$

$$\text{density of Si} = 5 \times 10^{23} / \text{cm}^3 \text{ (Si)} \quad 2 \times 10^{23} / \text{cm}^3 \text{ (Ge)?}$$

$$J = nqeE$$

$$= nq\mu_n E + p q\mu_p E$$

↓  
density  
of  $e^-$ .

↓  
Density  
of  $h^+$ .

$$\Rightarrow \sigma = \underbrace{q(n\mu_n + p\mu_p)}_{\sigma} E$$

$$\boxed{n=p}$$

Bipolar conductivity

$$\text{Law of mass action} \Rightarrow n \cdot p = n_i^2.$$

$$\underbrace{N_D + p}_{\substack{+ve \\ \text{charge}}} = \underbrace{n + N_A}_{\substack{-ve \\ \text{charge}}}$$

$N_D$ : Donor donates  $e^-$   
becomes truly charged.

Assume n-type semiconductor:

$$N_A = 0$$

$$\Rightarrow N_D + p = n$$

$$p = \frac{n_i^2}{n} \Rightarrow n \cdot N_D + \frac{n_i^2}{n} = n.$$

$$\Rightarrow n^2 - N_D n - n_i^2 = 0$$

$$\Rightarrow n = \frac{N_D + \sqrt{N_D^2 + 4n_i^2}}{2}$$

$$\Rightarrow n = \frac{N_D + \sqrt{N_D^2 + 4n_i^2}}{2}$$

$N_D \gg n_i$

$$n = N_D \quad \boxed{\rho \approx \frac{n_i^2}{N_D}}$$

### P-type semiconductor:-

$$\begin{array}{ll} N_D = 0 & N_A > n_i \\ \Rightarrow \boxed{\rho \approx N_A} & \boxed{n = n_i} \end{array}$$

$N_D = 10^5 / \text{cm}^3, N_A = 0$  in Si semiconductor

( $n_i = 1.5 \times 10^{10} / \text{cm}^3$ )

$n \approx 10^{15} / \text{cm}^3$

( $p_{Si} = 5 \times 10^{12} / \text{cm}^3$ )

$$\rho \approx \frac{(1.5 \times 10^{10})^2}{10^{15}} \Rightarrow \rho \approx 2.25 \times 10^5 / \text{cm}^3.$$

$$\sigma = q(n\mu_n + p\mu_p) \approx q\mu_n$$

$\approx qN_D$  ( $\sigma$  increased by  $10^5$  times)

$$\begin{array}{c} \rightarrow E \\ \leftarrow e^- \\ \rightarrow \text{+ve} \\ \leftarrow \text{+ve} \end{array}$$

$$J = J_n + J_p \quad \boxed{J_n = q\mu_n nE}$$

$$+ qD_n \frac{\partial n}{\partial x}$$



$$J_p = q\mu_p E + -qD_p \frac{\partial p}{\partial x}$$

drift

diffusion

$$[J_n + J_p] + qD_p \frac{\partial p}{\partial x} = 0$$
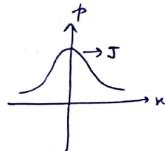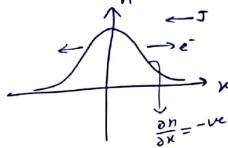
$$[J_n + J_p] + qD_p \frac{\partial p}{\partial x} = 0$$



$$\frac{D_n}{\mu_n} = \frac{D_p}{\mu_p} = \frac{k_B T}{q} \quad \text{--- Einstein relation.}$$

$$\frac{k_B T}{q} = V_T \quad (\text{Thermal voltage}). \quad = 0.026V \quad \text{at } 300K.$$

### Graded semiconductors:-

Net hole current = 0.

"---electron" = 0.

$$p\mu_p qE - qD_p \frac{\partial p}{\partial x} = 0$$

$$E = \frac{D_p}{\mu_p p} \frac{\partial p}{\partial x} \Rightarrow -\frac{\partial V}{\partial x} = \frac{V_T}{p} \frac{\partial p}{\partial x}$$

$$\Rightarrow -\frac{\partial V}{\partial x} = \frac{D_p}{\mu_p p}$$


$$\Rightarrow \int_{x_1}^{x_2} -\frac{\partial V}{\partial x} dx = \int_{x_1}^{x_2} \frac{V_T}{p} \frac{\partial p}{\partial x} dx$$

$$\Rightarrow V_2 - V_1 = V_T \ln(\frac{p_1}{p_2})$$

$$\Rightarrow \frac{p_1}{p_2} = e^{(V_2 - V_1) V_T}$$

$$\begin{cases} p_1 = p_2 e^{V_2/V_T} \\ n_1 = n_2 e^{-V_1/V_T} \end{cases} \quad (V_{21} = V_2 - V_1)$$


$$(n_1 p_1 = n_2 p_2).$$

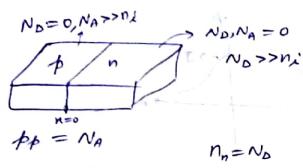


$$V_o = V_T \ln \left( \frac{P_p}{P_n} \right) = V_T \ln \left( \frac{n_p}{n_n} \right)$$

$$= V_T \ln \left( \frac{N_A}{(N_D^2/N_A)} \right) = 2V_T \ln \left( \frac{N_A}{N_D} \right)$$
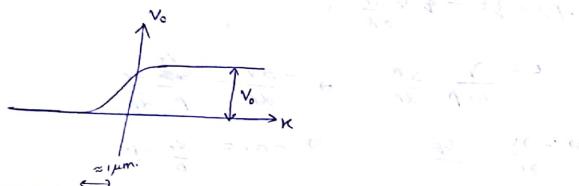
$$= V_T \ln \left( \frac{N_A}{(n_i^2/n_i)} \right) = V_T \ln \left( \frac{N_A N_D}{n_i^2} \right).$$



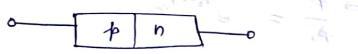
$p$   $n$   $e^-$  diffuses from  $n$  to  $p$  creating holes(+ve) in  $n$ .



$(N_D - x = N_A)$



Diode  
(passive)

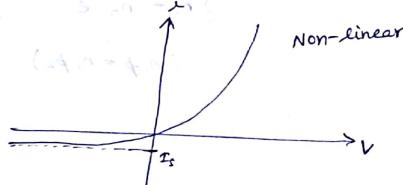


$$i = I_s (e^{V_o/V_T} - 1)$$

$N = [1, 2]$ .


$V_T$ : thermal voltage
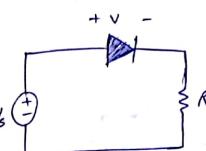
$$V_T = \frac{k_B T}{q} \approx 0.026 \text{ mV (300K)}$$



$$i = I_s (e^{V_o/V_T} - 1)$$
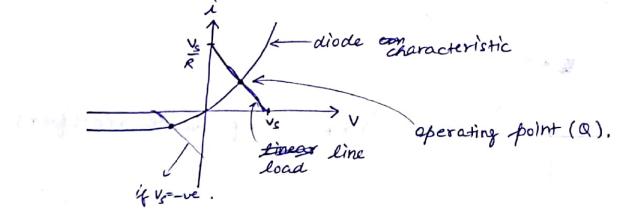
$$V_s = V + iR \Rightarrow i = \frac{V_s - V}{R}$$




Forward bias (low resistance),  
Reverse bias (high resistance).

Ideal diode:-




$$V < 0 \Rightarrow i = 0.$$

$$V > 0 \Rightarrow i = \infty.$$

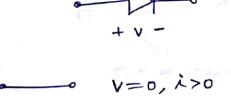

$$V = 0, i > 0$$

$$V \neq 0, i = 0, V \leq 0.$$

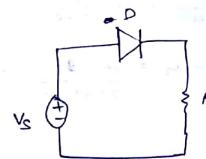


Assume D is ON.



$$i = \frac{V_s}{R} > 0$$

$\Rightarrow$  assumption OK.

Assume D is off

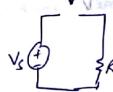
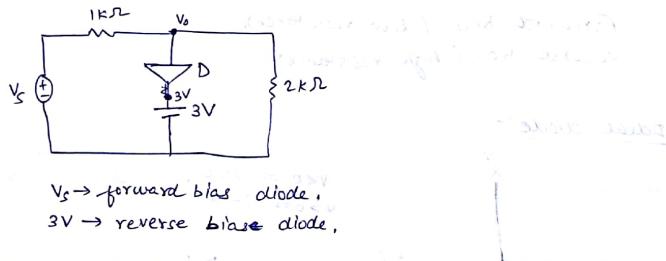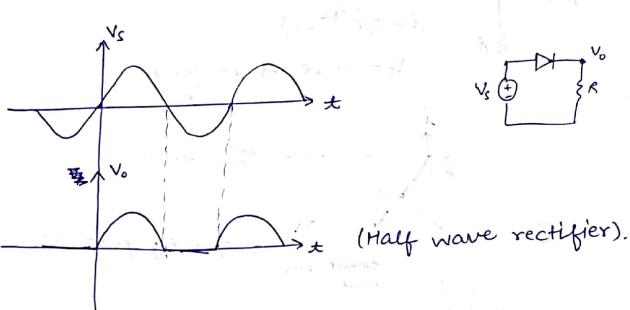
$$V = V_s > 0 \quad (V \text{ should be } \leq 0), \\ \Rightarrow \text{assumption wrong.}$$




Assume D is ON  $\Rightarrow$

i must be +ve

$$\Rightarrow V_s > 4.5V.$$

$$V_o = 3V.$$

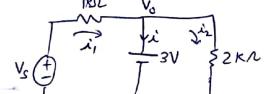

$$i_1 = \frac{V_o - 3}{1000}, \quad i_2 = \frac{3}{2000}$$


$$i = i_1 - i_2 = \frac{2V_o - 9}{2000} = \frac{V_o - 4.5}{1000}$$

Assume D is OFF:-

$$V_o < 3V \\ \Rightarrow \frac{2V_s}{3} < 3 \\ \Rightarrow V_s < 4.5V.$$

$$V_o = \frac{2V_s}{3}$$

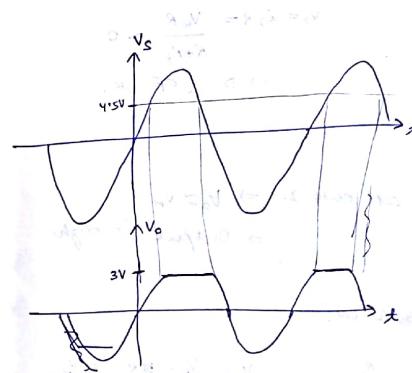
$$V_o = \begin{cases} \frac{2V_s}{3} & V_s \leq 4.5V \\ 3V, & V_s > 4.5V \end{cases}$$



Logic circuits:-

Low voltage = 0  
High voltage = 1

= 1  
= 0

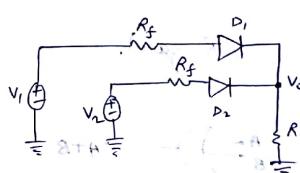


## Log Logic Circuits

$$1) V_1 = 0, V_2 = 0 \Rightarrow V_o = 0$$

$$2) V_1 = 0, V_2 = +V_H \Rightarrow D_2 = ON$$

Assume  $D_1 = OFF$

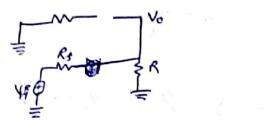

$i_2 > 0 \Rightarrow D_2$  ON. OK.

$$V_o = i_2 R = \frac{V_H R}{R + R_f} > 0$$

$\Rightarrow D_1$  OFF OK.

If  $R \gg R_f$


$$\Rightarrow V_o \approx V_H$$

$\Rightarrow$  Output is High

$$3) V_1 = V_H, V_2 = 0 \Rightarrow \text{same as case 2.} \Rightarrow V_o \approx V_H$$

$\Rightarrow$  Output is High
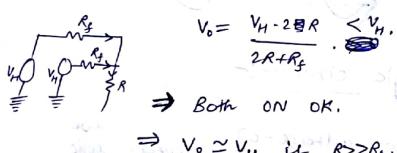
$$4) V_1 = V_H, V_2 = V_H \Rightarrow \text{Assume both ON.}$$



$$V_o = \frac{V_H - 2 \cdot R \cdot V_H}{2R + R_f} \leq V_H$$




$\Rightarrow$  Both ON OK.

$\Rightarrow V_o \approx V_H$  if  $R \gg R_f$ .

## Truth Table

$V_1$	$V_2$	$V_o$
0	0	0
1	0	1
0	1	1
1	1	1

(OR gate).

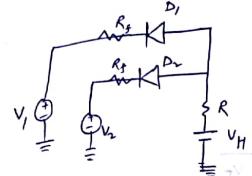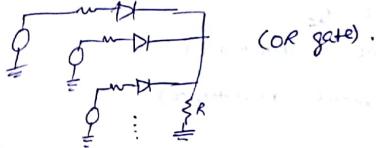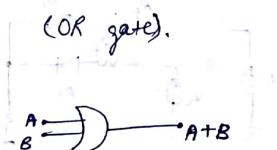

$$1) V_1 = 0, V_2 = 0 \Rightarrow \text{Both diodes ON.}$$

$$V_o = \frac{V_H R_f}{R_f + R} \quad R \gg R_f \Rightarrow V_o \approx 0.$$

$$2) V_1 = 0, V_2 = V_H \Rightarrow \text{Assume } D_1 \text{ ON, } D_2 \text{ OFF.}$$



$$\Rightarrow V_o = \frac{V_H R_f}{R_f + R} \quad R \gg R_f \Rightarrow V_o \approx 0.$$

$$3) V_1 = V_H, V_2 = 0 \Rightarrow \text{same as case 2.} \Rightarrow V_o \approx 0. \quad D_1 \text{ OFF, } D_2 \text{ ON.}$$

$$4) V_1 = V_H, V_2 = V_H \Rightarrow \text{Both OFF} \Rightarrow V_o \approx V_H.$$

$V_1$	$V_2$	$V_o$
0	0	0
0	1	0
1	0	0
1	1	1

(And gate)

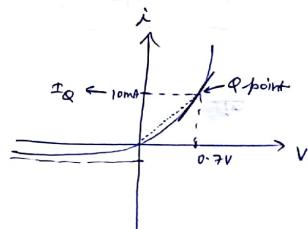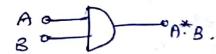

$$d.c. \text{ Resistance } R = \frac{0.7 \text{ V}}{10 \text{ mA}} = 70 \Omega.$$

$$a.c. \text{ resistance } V = 0.7 \text{ V} + V_{a.c.}, \quad I = 10 \text{ mA} + I_{a.c.}$$

$$g = \frac{i_{ac}}{V_{ac}} = \text{(incremental conductance)}$$

$$r = \frac{1}{g} = \frac{V_{ac}}{i_{ac}} \cdot \text{(incremental resistance)}$$



$$g = \frac{di}{dV}, r = \frac{dV}{di}$$

$$i = I_s (e^{\frac{V}{nV_T}} - 1)$$




$$\frac{di}{dV} = \frac{I_s}{nV_T} e^{\frac{V}{nV_T}} = I_s e^{\frac{V}{nV_T}} \cdot \frac{1}{nV_T}$$

$$k = \frac{qIE}{V_T}$$


$$k = \frac{nV_T}{I_s}$$

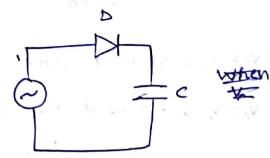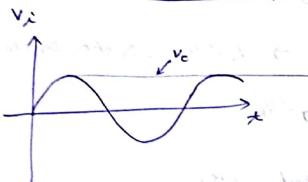

Peak Detector.

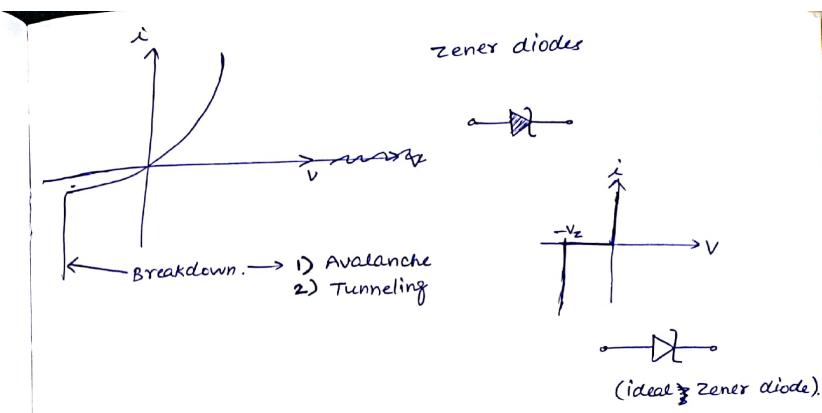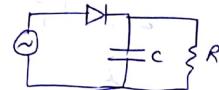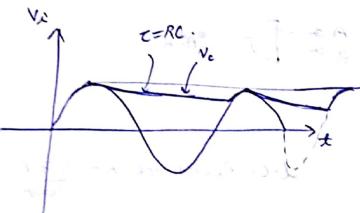

(ideal zener diode)

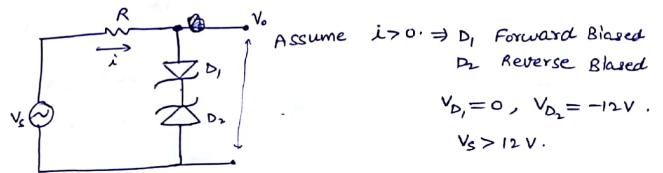

$$V_s = 24 \sin \omega t$$

$$V_Z = 12 \text{ V}$$

Assume  $i > 0 \Rightarrow D_1$  Forward Biased  
 $D_2$  Reverse Biased


$$V_{D_1} = 0, V_{D_2} = -12 \text{ V}$$

$$V_s > 12 \text{ V}$$

Assume  $i < 0 \Rightarrow D_1$  Reverse,  $D_2$  Forward  
 $V_{D_1} = -12 \text{ V}, V_{D_2} = 0 \text{ V}$   
 $V_s < -12 \text{ V}$


Assume  $i = 0 \Rightarrow$  Assume  $V_s = 7 \text{ V}$ .
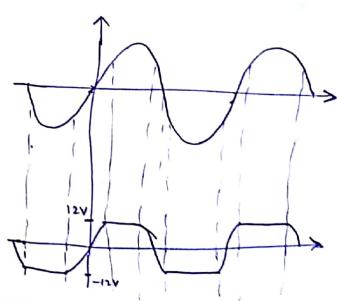
$$V_R = 0, V_o = V_s, V_f = 7 \text{ V}$$





Voltage limiter.

## Bipolar Junction Transistor (BJT)

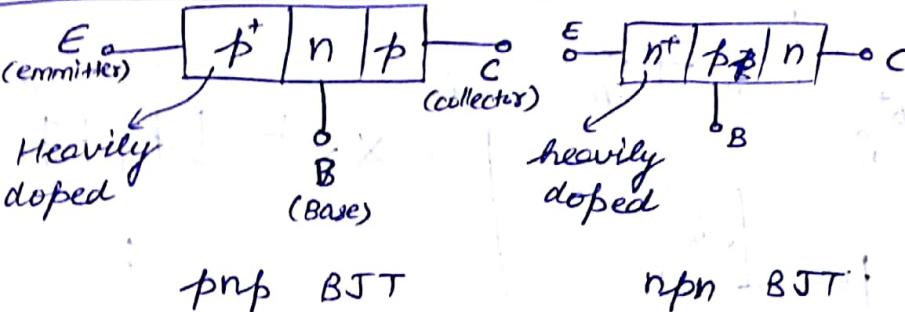

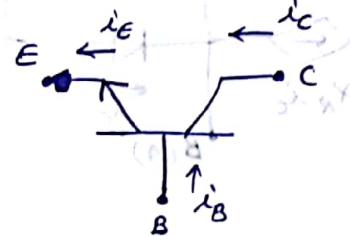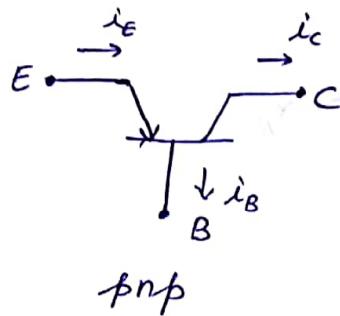emitter doping > base doping > collector doping



$$i_E = i_B + i_C$$

$$V_{EB} + V_{BC} + V_{CE} = 0.$$

E-B junction

FB

FB

R<sub>B</sub>

R<sub>B</sub>

~~C-B~~ junction

FB

RB

FB

RB

Mode


Saturation

Active


Reverse-Active


(Inverted)

Cut-off

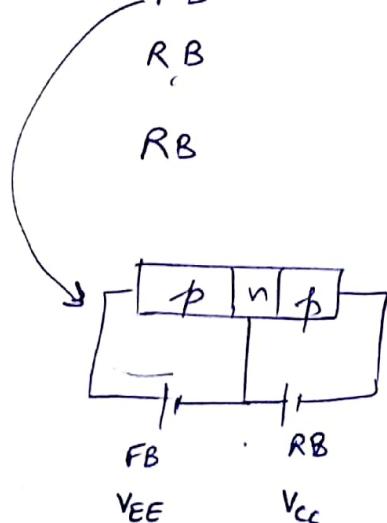

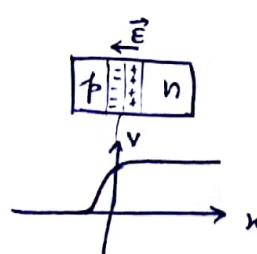Active mode : amplifier  
sat., cut-off : logic




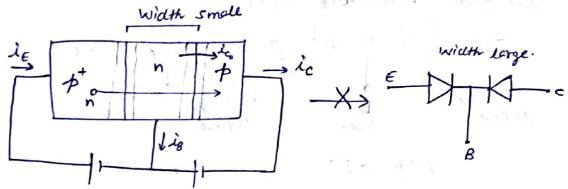

$$i_E = i_B + i_C$$

$$\Rightarrow i_B = i_E \left( \frac{1}{\alpha} \right)$$
~~$$\Rightarrow i_C = \left( \frac{\alpha}{1-\alpha} \right) i_B$$~~

$$\Rightarrow i_C = \beta i_B$$

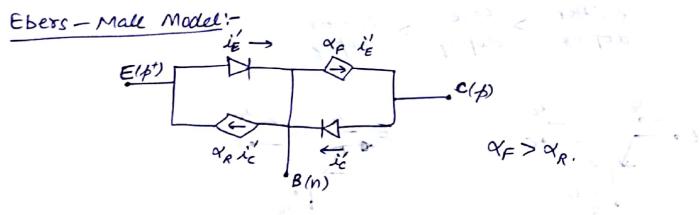

$$i'_E = I_{ES} (e^{V_{BE}/V_T} - 1)$$

$$i'_C = I_{CS} (e^{V_{CE}/V_T} - 1)$$

$$i_E = I'_E - \alpha_R i'_C = I_{ES} (e^{V_{BE}/V_T} - 1) - \alpha_R I_{CS} (e^{V_{CB}/V_T} - 1)$$

$$i_C = \alpha_F i'_E - \cancel{i'_C} = \alpha_F I_{ES} (e^{V_{BE}/V_T} - 1) - I_{CS} (e^{V_{CB}/V_T} - 1)$$

$$i_B = i_E - i_C$$


Assume active mode,

$$e^{\frac{V_{BE}}{V_T}} - 1 = \frac{i_E}{I_{ES}} - \alpha_R I_{CS}$$



$$i_C = \alpha_F I_{ES} \left( \frac{i_E - \alpha_R I_{CS}}{I_{ES}} \right) + I_{CS}$$

$$= \alpha_F i_E + I_{CS} (1 - \alpha_F \alpha_R)$$


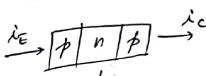
$$i_C = \alpha i_E + i_{C_0} \Rightarrow i_C = \alpha i_E$$





Circuit configuration:

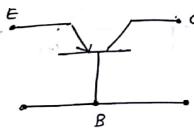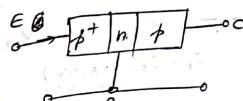

Common base configuration

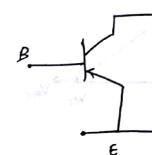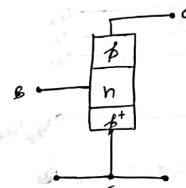


Common emitter configuration

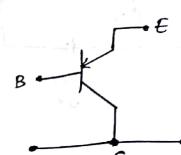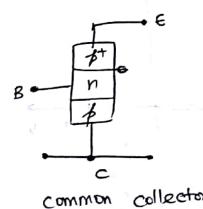

Common collector

Common Base :-

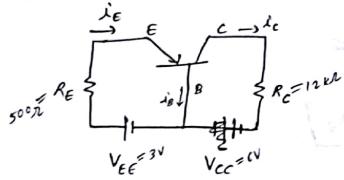


Input side

$$V_{EE} = i_E R_E + V_{EB} \text{ (load line)}$$




Output side

$$V_{CC} = i_C R_C + V_{BC}$$

Input side  $\rightarrow$

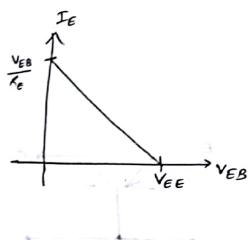

Output side  $\rightarrow$

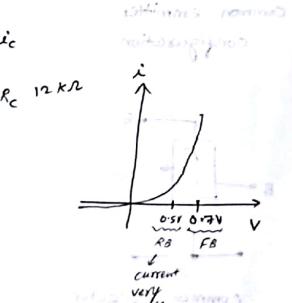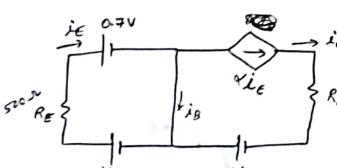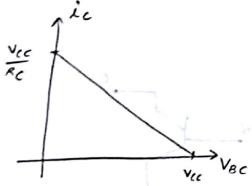

$$I_C \neq I_C(V_{CB})$$

$$V_{CB} - V_{CE} + i_E R_E = 0$$

$$0.7 - 3 + 500 i_E = 0 \Rightarrow i_E = 4.6 \text{ mA}$$


$$V_{CB} - R_C i_C + 6 = 0$$

$$i_C = \alpha i_E \approx i_E$$



$$\Rightarrow V_{CB} - 12000 \times 4.6 \times 10^{-3} + 6 = 0$$

$\Rightarrow V_{CB} = -0.48 \text{ V}$ . (Assumption OK). (Reverse biased).


Common Emitter :- (npn BJT)

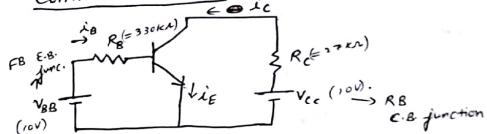

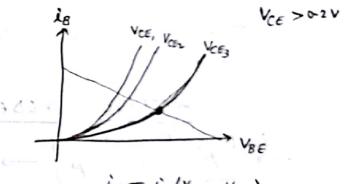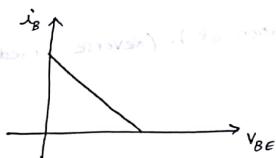
$$\text{Input} \rightarrow V_{BB} = i_B R_B + V_{BE}$$



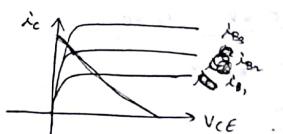
$$\text{Output} \rightarrow V_{CC} = i_C R_C + V_{CE}$$



$$i_C = i_C(V_{CE}, i_B)$$

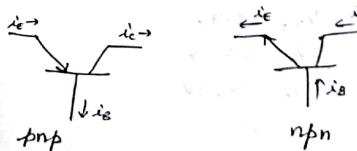

Assume active mode:-

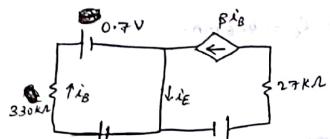


$$i_B = \frac{10 - 0.7}{330 \times 10^3} = 2.82 \mu A.$$

$$i_C = \beta i_B = 2.82 \text{ mA.}$$



$$V_{CE} = (-2.7 \times 10^3) i_C + 10 = 2.39 \text{ V.}$$
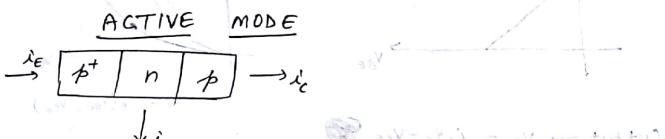
$$\Rightarrow V_{BE} = V_{BE} - V_{CE} \\ = 0.7V - 2.39V \\ \Rightarrow V_{BC} = -1.69 \text{ V} \quad (\text{Assumption OK}). \quad (\text{Reverse biased}).$$





$$V_{EB} = 0.7V, V_{CB} < 0.5V, i_B > 0$$
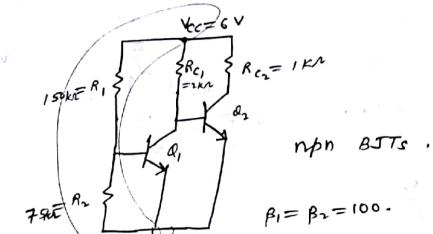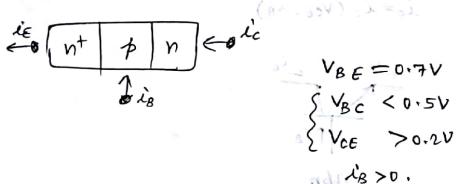
$$V_{EC} = V_{EB} + V_{BC} = V_{EB} - V_{CB} \\ \Rightarrow V_{EC} > 0.2V.$$



$$\beta_1 = \beta_2 = 100.$$


Assume both Active.

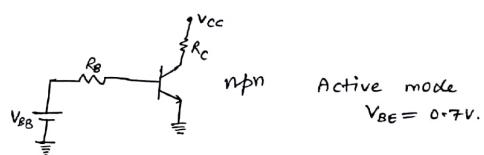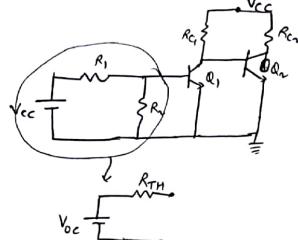

Active mode  
V<sub>BE</sub> = 0.7V.

Cut-off mode


Both junctions R.B.  $i_B = 0 = i_C$ .

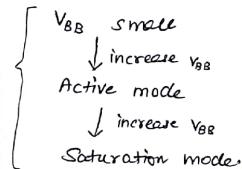


Saturation mode :-

$$V_{BE}(\text{sat}) = 0.8V$$

$$V_{CE}(\text{sat}) = 0.2V$$

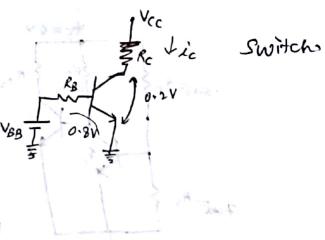
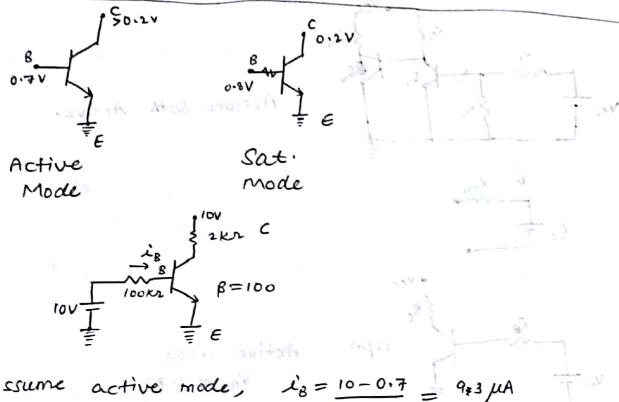
$$\text{Check: } i_B > \frac{i_C}{\beta}$$



$$\text{Assume active mode, } i_B = \frac{10 - 0.7}{100k\Omega} = 9.3 \mu A$$

$$i_C = \beta i_B = 9.3 \text{ mA.}$$

$$V_{CE} = 10 - i_C R_C \\ = 10 - 9.3 \times 2k\Omega \\ = -8.6V.$$

$V_{CE}$  must be  $> 0.2V$  for active mode.


$\Rightarrow$  Incorrect assumption.

Assume saturation mode,

$$i_B = \frac{10 - 0.8}{100k\Omega} = 9.2 \mu A \quad i_C = \frac{10 - 0.2}{2k\Omega} = 4.9 \text{ mA.}$$

~~assume 9.2 mA.~~
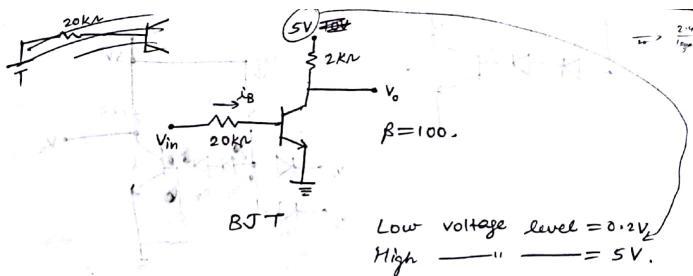
$$\beta i_B = 9.2 \text{ mA} > i_C \Rightarrow \text{Correct.}$$



1)  $V_{in}$  is small  $V_{in} = 0.2V$ .

Both reverse biased

$\Rightarrow Q = 0$  cut-off mode

$$\Rightarrow V_o = 5V.$$

2)  $V_{in} = 5V$ .

Assume  $Q = 0N$ . (saturation).


$$i_B = \frac{5 - 0.8}{20k\Omega} = 0.21 \text{ mA}$$

$$i_C = \frac{5 - 0.2}{2k\Omega} = 2.4 \text{ mA}$$

$$\beta i_B = 0.21 \times 100 = 21 > \frac{2.4}{i_C} \text{ mA} \Rightarrow \beta i_B > i_C \Rightarrow \text{Correct.}$$


$$V_o = 5 - 2k\Omega \times 2.4 \text{ mA}$$



$$\Rightarrow V_o = 0.2V.$$

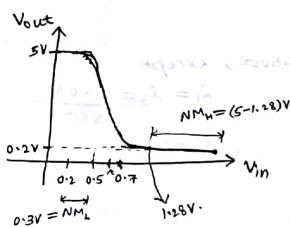

Need  $i_B > \frac{i_C}{\beta}$  for sat. mode'
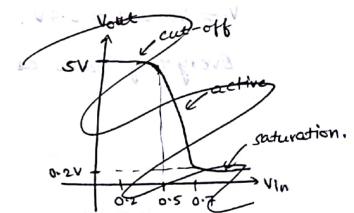
$$\frac{V_{in} - 0.8}{20k\Omega} > \frac{5 - 0.2}{2k\Omega \times 100} \Rightarrow V_{in} > 1.28V.$$



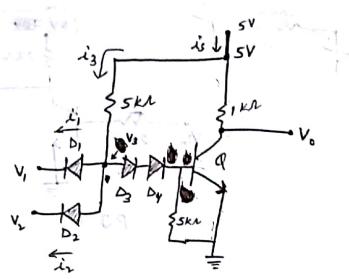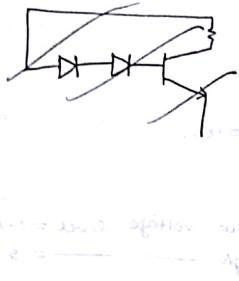

$$1) V_1 = V_2 = 0.2V$$

Assume  $D_1, D_2$  ON.

$$\Rightarrow V_3 = 0.2 + 0.7 = 0.9V$$

Assume  $D_3, D_4$  OFF

$$i_3 = \frac{5 - 0.9}{5k\Omega} \quad (i_1 = i_2 = \frac{i_3}{2} = +ve. \quad (D_1, D_2 \text{ ON} \text{ correct}).)$$

$$i_8 = 0, V_{BE} = 0.$$

$\varphi = \text{OFF}$


$$V_o = 5V.$$

$$2) V_1 = 0.1V, V_2 = 5V.$$

Assume  $D_1$  ON,  $D_2$  OFF.

$$V_3 = V_1 + 0.7 = 0.9V.$$

Everything same as above, except

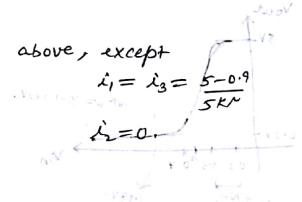

$$3) V_1 = 5V, V_2 = 0.2V \Rightarrow \text{same as above}$$

$$i_1 = 0 \\ i_2 = i_3 \\ \therefore V_o = 5V.$$

$$4) V_1 = 5V, V_2 = 5V.$$

$D_1, D_2$  OFF.  $i_1 = i_2 = 0.$


Assume  $D_3, D_4$  ON.

Assume  $\varphi = \text{ON}$  (sat.)

$$V_3 = 0.7 + 0.7 + 0.8 = 2.2V.$$

$$i_3 = \frac{5 - 2.2}{5k\Omega} = \frac{2.8}{5k\Omega} = 0.56 \text{ mA}. \quad i_8 = i_3 - \frac{0.8}{5k\Omega} = 0.56 - \frac{0.16}{5k\Omega} = 0.4 \text{ mA}.$$
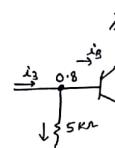
$$i_C = \frac{5 - 0.2}{1k\Omega} = 4.8 \text{ mA}.$$



$$\Rightarrow i_B = 0.4 \text{ mA}.$$

$$\text{If } \beta = 100 \Rightarrow \beta i_B = 40 \text{ mA} > i_C$$

$\Rightarrow$  Correct assumption.

$$\frac{\beta}{\beta} \left[ \frac{i_C}{i_B} = 12 \right] \text{ if } \beta > 12 \Rightarrow \text{correct assumption.}$$

$$V_o = 0.2V.$$

$V_1$	$V_2$	$V_o$	AND	NAND Gate
0	0	1	0	
1	0	1	0	
0	1	1	0	
1	1	0	1	



Power dissipation :-

$$\text{Case 4)} i_8 = i_3 + i_C = 0.56 + 4.8 = 5.36 \text{ mA}.$$

$$\text{Power} = V_i i = 5 \times 5.36 = 26.8 \text{ mW}.$$

$$\text{Cases 1, 2, 3)} i_8 = i_3 + i_C = i_3 = 0.82 \text{ mA}.$$
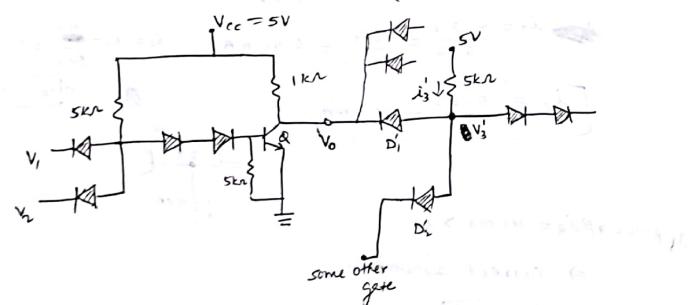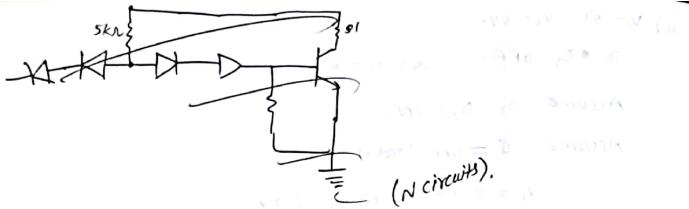
$$\text{Power} = V_i i = 5 \times 0.82 = 4.1 \text{ mW}.$$



If  $V_1 = 5V, V_2 = 5V$

$$V_o = 0.2V$$

$Q$  in saturation.

$$\Rightarrow D_1 \text{ is ON. } \Rightarrow V_3' = 0.2 + 0.7 = 0.9V.$$

$$I_3' = \frac{5 - 0.9}{5k\Omega} = 0.82 \text{ mA.}$$

$$I_B = \frac{5 - 0.2}{1k\Omega} = 0.8 \text{ mA.} \quad \text{(worst case if all current flows through } D_1).$$

$$I_B = 0.4 \text{ mA. (calculated last time).}$$

$$\text{Need: } \beta I_B \geq I_B$$

$$\Rightarrow \beta(0.4) \geq (4.8 + N \times 0.82)$$

$$\text{Let } \beta = 40$$

$$\Rightarrow 16 \geq 4.8 + N \times 0.82 \Rightarrow N \leq \frac{11.2}{0.82} \Rightarrow N \leq 13.7.$$

$\Rightarrow [N = 13]$ , at max.



$\Rightarrow \text{Fan out} = 13.$

## FET (Field Effect Transistors)

Unipolar (majority carriers)


Voltage controlled  
(electric field)

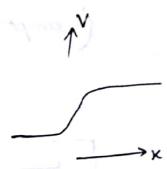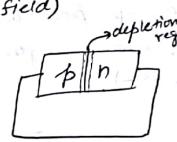- 1) JFET - Junction FET
- 2) MOSFET - Metal Oxide Semiconductor FET.




Depletion regions increase in reverse bias.

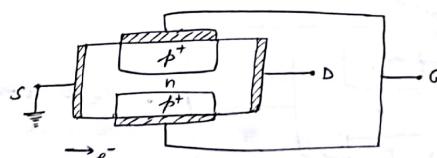can control the depletion region by Voltage.




Source, Drain, Gate. (n-channel JFET)

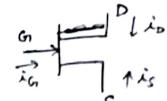



Apply  $V_{DS} \geq 0$ .

Everything grounded  $\Rightarrow$

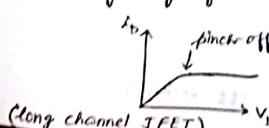



(long channel JFET)

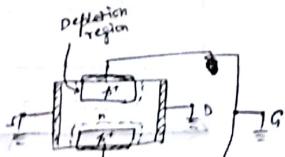

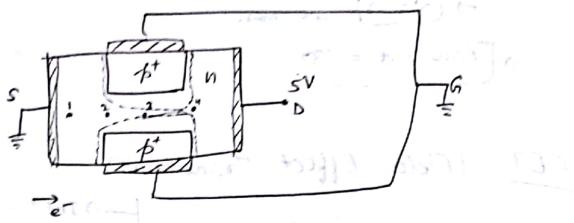


pinch-off  $\rightarrow$  when the depletion regions touch.

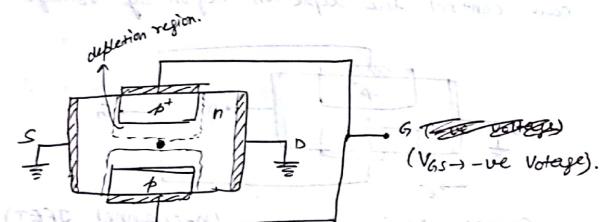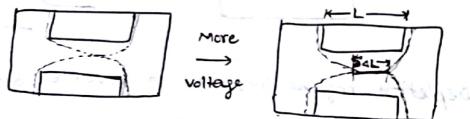(Assumption: length of pinch-off is much less than total length ( $\Delta L \ll L$ )).



If  $V_{GS} \rightarrow +ve$   
then forward biased diodes

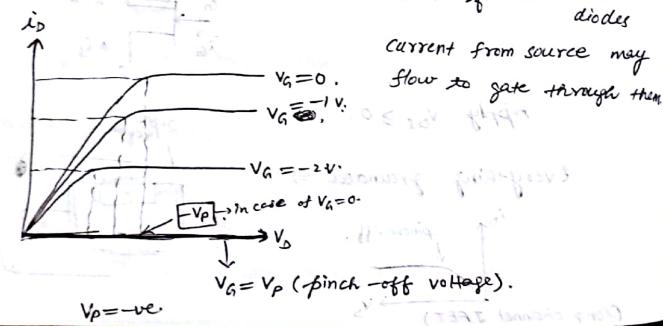current from source may flow to gate through them




$$V_{D, \text{sat.}} = V_G - V_p.$$

$$\rightarrow i_D = I_{DSS} \left[ 2 \left( 1 - \frac{V_{GS}}{V_p} \right) \frac{V_{DS}}{-V_p} - \left( \frac{V_{DS}}{V_p} \right)^2 \right]$$

$i_D = i_{D, \text{sat}}$  (saturation/active).

If  $V_{DS}$  is small (compared to  $V_p$ ),
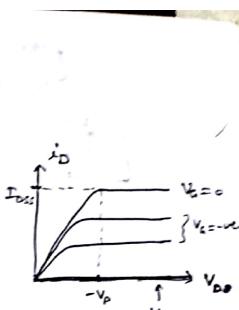
$$R = \frac{V_{DS}}{i_D} = \frac{V_p^2}{2 I_{DSS} (V_{GS} - V_p)}$$





$$I_{DSS} = I_{D, \text{sat}} (V_G = 0)$$

$$\frac{\partial i_D}{\partial V_D} = I_{DSS} \left[ 2 \left( \frac{V_{GS} - V_p}{V_p^2} \right) - \frac{2 V_{DS}}{V_p^2} \right]$$


$$\Rightarrow V_{DS} = V_{GS} - V_p \quad | \quad = V_{D, \text{sat.}}$$

$$i_{D, \text{sat.}} = I_{DSS} \left[ 2 \left( \frac{V_{GS} - V_p}{V_p} \right)^2 - \left( \frac{V_{GS} - V_p}{V_p} \right)^2 \right]$$

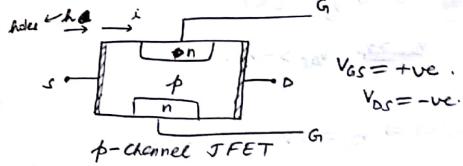
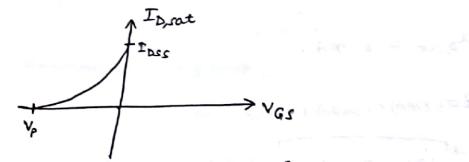
$$\Rightarrow i_{D, \text{sat.}} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_p} \right)^2.$$



JFET - Depletion Type device

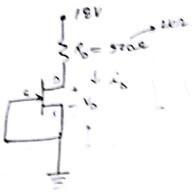

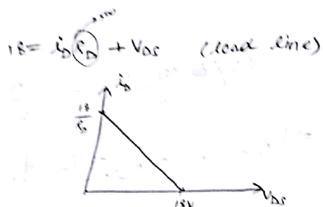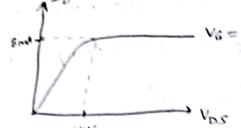Given:  $I_{DS} = 8 \text{ mA}$   
 $V_P = -4 \text{ V}$



Assume JFET in active mode,

$$I_{Dsat} = I_{DS} \left(1 - \frac{V_{DS}}{V_P}\right)^2 = 8 \left(1 - \frac{0}{-4}\right)^2$$

$$\Rightarrow I_{Dsat} = 8 \text{ mA.}$$

$$18 = (8 \text{ mA}) \times (500 \Omega) + V_{DS}$$

$$\Rightarrow V_{DS} = 14 \text{ V.} \quad (10 \text{ k})$$

$$\cancel{V_{DS} > V_P.}$$

$$\text{If } R_o = 2 \text{ k} \Rightarrow V_{DS} = 2 \text{ V}, \quad V_{DS} > -V_P.$$

wrong assumption.

Assume ohmic mode, using main eqn.


$$I_D = (8 \times 10^{-3}) \left[ 2 \left(1 - \frac{0}{-4}\right) \frac{V_{DS}}{500} - \left(\frac{V_{DS}}{500}\right)^2 \right]$$

$$\Rightarrow \frac{18 - V_{DS}}{2 \times 500} = \frac{8 \times 10^{-3}}{500} \left( \frac{V_{DS}}{2} - \frac{V_{DS}^2}{1000} \right)$$

$$\Rightarrow 72 - 4V_{DS} = 8V_{DS} - V_{DS}^2 \Rightarrow V_{DS}^2 - 12V_{DS} + 72 = 0$$

$$\Rightarrow V_{DS} = 3, 6. \quad (V_{DS} < 4 \text{ V}).$$

### MOSFET

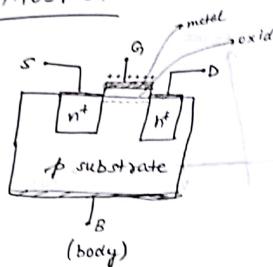

n-channel mosfet (NMOS)




$$V_G = 0$$

Apply +ve  $V_G$ .

large  $+V_G$ , surface inversion.

$$V_G > V_t$$

threshold voltage

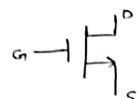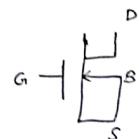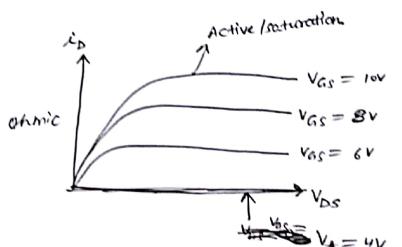

enhancement



MOSFET  $\rightarrow$  Enhancement Mode.

$$* \lambda_D = k [2(v_{GS} - V_T) v_{DS} - v_{DS}^2]$$




$$\frac{dI_D}{dV_{DS}} = k (2(v_{GS} - V_T) - 2v_{DS})$$

$$\Rightarrow [V_{DS} = v_{GS} - V_T] = V_{D, \text{sat}}$$

$$\lambda_D \ll (v_{GS} - V_T)^2$$

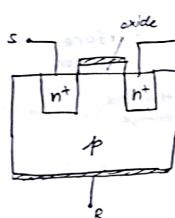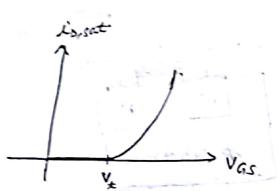


Depletion MOSFET

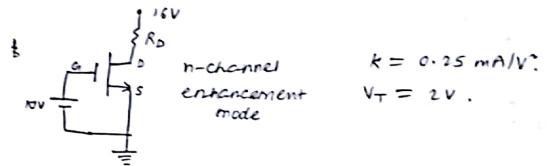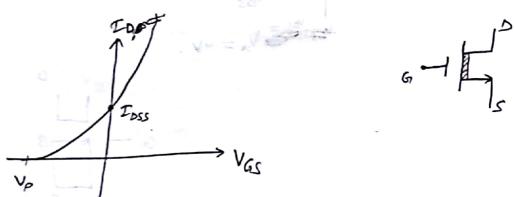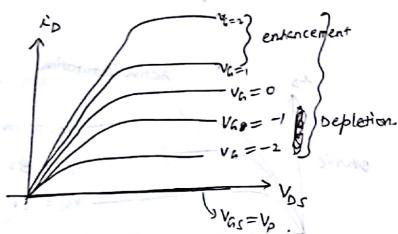

$$k = 0.25 \text{ mA/V}^2$$

$$V_T = 2V$$

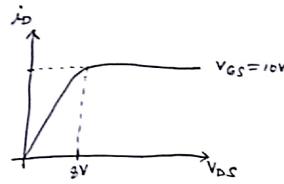


$$V_{D, \text{sat}} = V_{GS} - V_T = 10 - 2 = 8V$$

$$\begin{aligned} I_{D, \text{sat}} &= k (10 - 2)^2 = k (v_{GS} - V_T)^2 \\ &= 0.25 \times 64 \text{ mA} \\ \Rightarrow I_{D, \text{sat}} &= 16 \text{ mA} \end{aligned}$$

Load line,

$$16 = V_{DS} + \lambda_D R_D$$

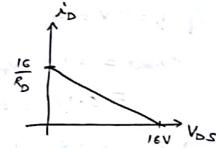

$$\text{Let } R_D = 250\Omega$$

Assume active (saturation)  $\Rightarrow I_D = I_{D, \text{sat}} = 16 \text{ mA}$

$$16 = V_{DS} + 16 \text{ mA} \times 250\Omega$$

$$\Rightarrow V_{DS} = 12V$$

$V_{DS} > 8V \Rightarrow$  Assumption OK


$$\text{Let } R_D = 1k\Omega$$

Assume active (sat.)  $\Rightarrow V_{DS} = 0V < 8V \Rightarrow$  WRONG Assumption.


Assume ohmic mode  $\Rightarrow I_D = k [2(v_{GS} - V_T) v_{DS} - v_{DS}^2] \quad (i)$

$$16 = V_{DS} + \lambda_D R_D \quad (ii)$$
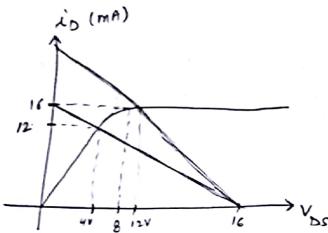
$$\begin{aligned} \text{(ohmic mode)} \Rightarrow & V_{DS} = 4V \text{ or } 12V \Rightarrow V_{DS} = 4V; \lambda_D = 12 \text{ mA} \end{aligned}$$



$$1) R_D = 250 \Omega$$

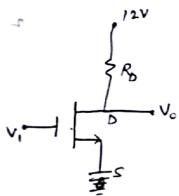

$$V_x = 2V$$

$$K = 0.25 \text{ mA/V}^2$$

$$R_D = 1k\Omega$$


If  $V_i = 12V = V_{GS}$

$$I_{D,sat} = K(V_{GS} - V_T)^2$$

$$= 0.25(12-2)^2 \text{ mA}$$

$$\Rightarrow I_{D,sat} = 25 \text{ mA.}$$
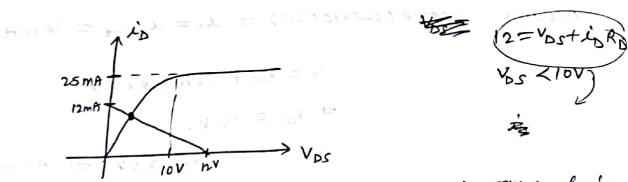
$$V_{D,sat} = V_{GS} - V_T = 12 - 2 = 10V.$$




Assumption wrong  $\Rightarrow$  assume ohmic & solve.

If  $V_i = 12V$  (high)


$$V_o = \text{low} \approx 2V, I_D = \frac{12-2}{1k\Omega} = 10 \text{ mA.}$$

If  $V_i = 2V$  (low)

$$\Rightarrow V_o = 12V.$$

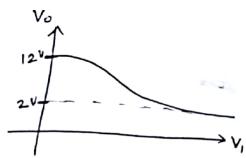
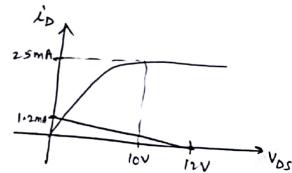
$$\text{If } R_D = 10k\Omega, I_D = V_{DS} + I_D R_D$$



(better inverter)


Replace  $R_D$  by MOSFET.



n-channel enhancement

$$V_{D,sat} = V_{GS} - V_T = V_{DS} - V_T$$

$$\Rightarrow \text{Always active.}$$

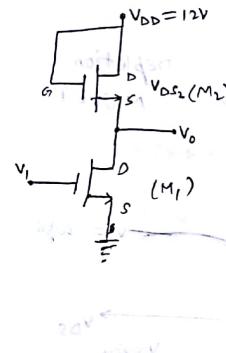






$$V_x = 2V$$

$$K = 0.25 \text{ mA/V}^2$$

$$M_2: I_D = I_{D,sat} = k_2(V_{GS} - V_T)^2$$

$$= k_2(V_{DD} - V_{DS} - V_T)^2$$
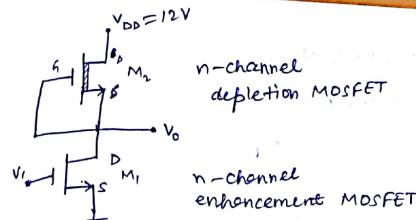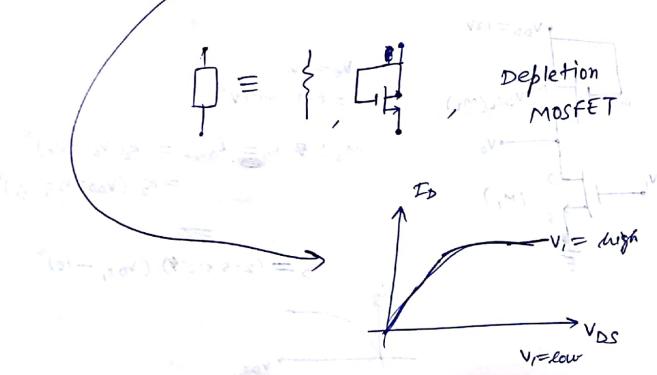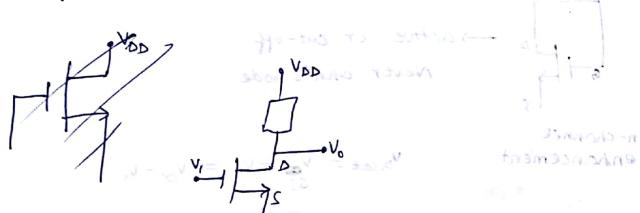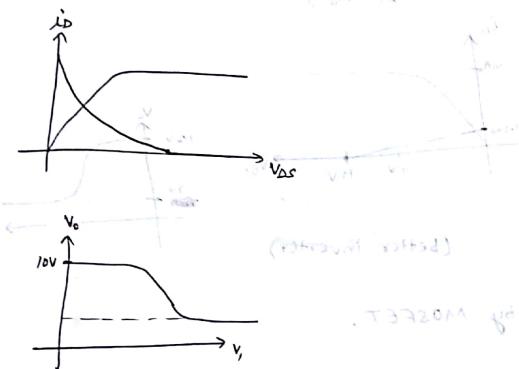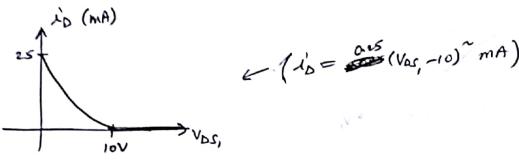
$$I_D = (2.5 \times 10^{-4})(V_{DS} - 10)^2$$




$$M_1: k = 0.25 \text{ mA/V}^2$$

$$V_G = 2V$$

$$M_2: I_{DSS} = 4 \text{ mA}$$

$$V_P = -4V$$

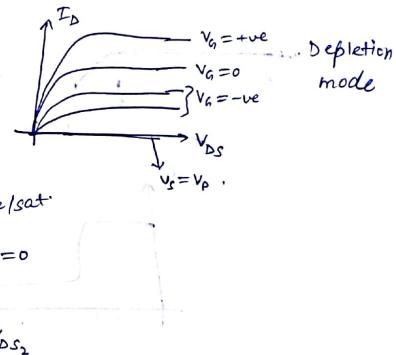

Assume M<sub>2</sub> in ohmic

$$I_D = I_{DSS} \left[ 2 \left( \frac{V_{DS_2} - V_p}{V_p} \right) V_{DS_2} - \left( \frac{V_{DS_2}}{V_p} \right)^2 \right]$$

$$= 4 \left[ 2 \times \frac{V_{DS_2}}{(4)^2} - \frac{(V_{DS_2})^2}{(4)^2} \right] \quad V_p = -4V$$

$$V_{DS_2} = V_{DD} - V_{DS_1}$$




$$I_D = -(2.5 \times 10^{-4}) (V_{DS_2}^2 - 16V_{DS_2} + 48)$$

$$\text{Need: } V_{DS_2} = V_{DD} - V_{DS_1} \leq 4V$$

$$\Rightarrow V_{DS_1} \geq 12 - 4 \Rightarrow V_{DS_1} \geq 8V$$

If  $V_{DS1} < 8V \Rightarrow M_2$  : sat. / active

$$i_D = 4 \text{ mA}$$

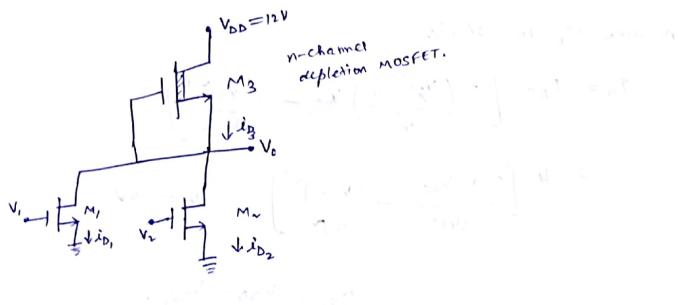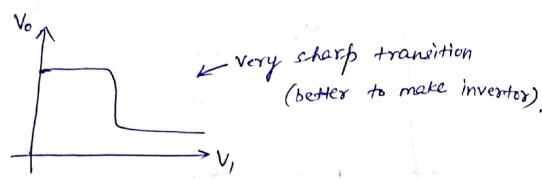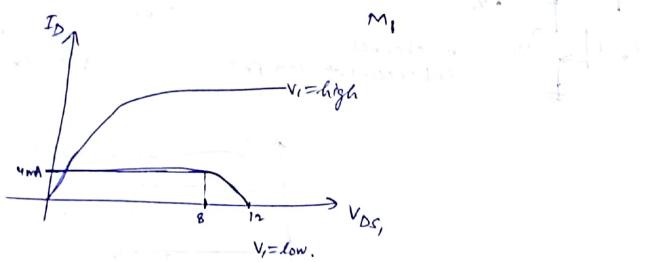

1)  $V_1 = 0, V_2 = 0 \Rightarrow M_1 = M_2 = \text{OFF}$

$$\Rightarrow i_{D3} = 0.$$

$$\Rightarrow V_0 = V_{DD} = 12V.$$

2)  $V_1 = 0, V_2 = V_{DD}$

$M_1 = \text{OFF} \Rightarrow \text{same as inverter}$

$V_0 = \text{low.}$

3)  $V_1 = 0, V_{DD}, V_2 = 0$

$M_2 = \text{OFF} \Rightarrow \text{same as inverter}$

$V_0 = \text{low}$


4)  $V_1 = V_{DD}, V_2 = V_{DD}$

$M_1, M_2 = \text{ON}$

$V_0 = \text{low.}$

$V_1$	$V_2$	$V_0$
0	0	1
1	0	0
0	1	0
1	1	0

NOR

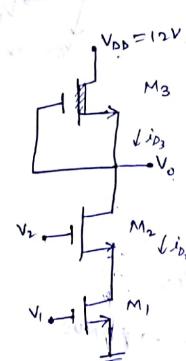

If  $V_1 = 0, V_2 = 0 \Rightarrow M_1 = \text{OFF} \Rightarrow i_D = 0$

$$\Rightarrow V_0 = V_{DD}.$$

- 1)  $V_1 = 0, V_2 = 0 \Rightarrow V_0 = \text{high.}$  Find out state of  $M_2$ ?
- 2)  $V_1 = 0, V_2 = V_{DD} \Rightarrow V_0 = V_{DD}.$  Find out state of  $M_2$ ?

$V_1, V_2, V_0$

0 0 1 }  $i_D = 0$

1 0 1 }  $i_D = 0$ ,  $\Rightarrow$  saturation

0 1 1 }  $i_D = 0$

1 1 0 }  $i_D = 0$ ,  $\Rightarrow$  saturation







NAND.

3)  $V_1 = V_{DD}, V_2 = 0 \Rightarrow M_1 = \text{ON}, M_2 = \text{OFF}$

$$\Rightarrow i_D = 0 \Rightarrow V_0 = V_{DD}.$$

4)  $V_1 = \text{high}, M_1 = \text{ON}, M_2 = \text{ON} \Rightarrow V_0 = \text{small.}$


CMOS  
↓  
complementary

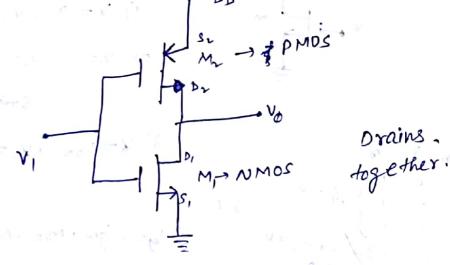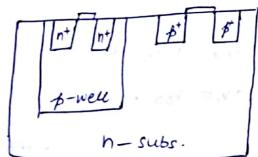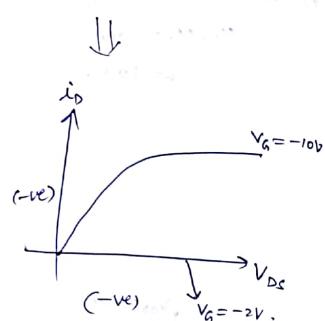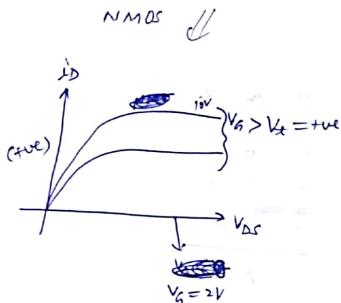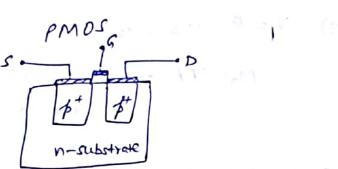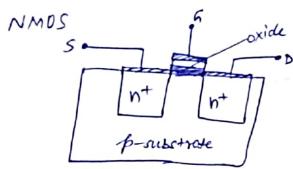

1)  $V_1 = 0 \Rightarrow M_1 = \text{OFF} \Rightarrow i_D = 0$   
 $M_2 = \text{ON}$  ( $V_{GS2} = V_1 - V_{SD} = -V_{DD}$ ).  
 $\Rightarrow V_o = \text{high}$ . ( $V_{DS} = 0$  if  $i_D = 0$ )

2)  $V_1 = V_{DD} \Rightarrow M_1 = \text{ON}$   
 $M_2 = \text{OFF}$  ( $V_{GS2} = V_1 - V_{SD} = 0$ ).  
 $\Rightarrow i_D = 0$ .  
 $\Rightarrow V_{DS1} = 0 \Rightarrow V_o = 0$ .

CMOS NAND GATE :-

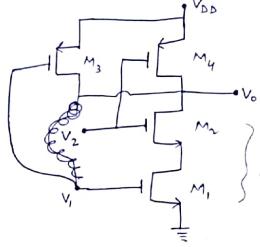

If  $V_1 = 0 \Rightarrow M_1 = \text{OFF} \Rightarrow i_D = 0$ .  
 $M_3 = \text{ON}$ .  
 $V_G = V_{DD}$ .  
 $\boxed{M_3 \Rightarrow V_{GS} = V_0 - V_{SD} = -V_{DD} \equiv 0}$

1)  $V_1 = 0, V_2 = 0 \Rightarrow V_o = V_{DD}, M_1 = \text{OFF}, M_2 = \text{OFF}, M_3 = \text{ON}, M_4 = \text{ON}$

2)  $V_1 = 0, V_2 = V_{DD} \Rightarrow V_o = V_{DD}, M_1 = \text{OFF}, M_2 = \text{ON}, M_3 = \text{ON}, M_4 = \text{OFF}$ .  
Assume  $M_2$  ON.

$\Rightarrow V_{DS2} = 0$

$$\Rightarrow V_{DS2} = V_0 - V_{DS2} = V_{DD}$$

$$\Rightarrow V_{GS2} = V_2 - V_{DS2} = 0 \quad (X)$$

Assume  $M_2$  OFF.

3)  $V_1 = V_{DD}, V_2 = 0 \Rightarrow M_1 = \text{ON}, M_3 = \text{OFF}, M_4 = \text{ON}$ .

$M_2 = \text{OFF}$ .  
 $\boxed{\text{but } i_D = 0 \Rightarrow V_{DS2} = 0}$   
 $\Rightarrow V_o = V_{DD}$ .

4)  $V_i = V_{DD}$ ,  $V_o = V_{DD}$ .  $\Rightarrow M_1 = ON$ ;  $M_3, M_4 = OFF$   
 $\Rightarrow I_D = 0$   $\leftarrow$  run off

$$M_2: V_{GS_2} = V_2 - V_{DS_2} = V_{DD} - V_{DS_2}$$



$M_1$  ON but no current  $\Rightarrow V_{DS_2} = 0 \Rightarrow V_{GS_2} = V_{DD}$   
 $\Rightarrow M_2 = ON$ .

$M_2$  ON but no current  $\Rightarrow V_{DS_2} = 0 \Rightarrow V_o = 0$ .

$V_i$	$V_o$	$V_o$
0	0	1
1	0	1
0	1	1
1	1	0


$\Rightarrow$  NAND Gate.

### CMOS NOR GATE :- HW

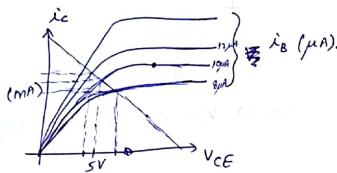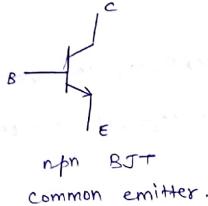

$$\frac{I_c}{I_B} = \beta = 100 \Rightarrow \frac{\Delta I_c}{\Delta I_B} = 100.$$

(active) current amplification


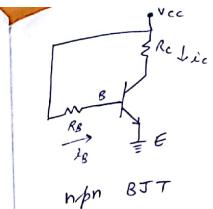


Assume active mode  $\Rightarrow V_{BE} = 0.7V$ .

$$I_B = \frac{V_{CC} - 0.7}{R_B} \quad I_C = \beta I_B$$

$$V_{CE} = V_{CC} - I_C R_C$$

Need  $V_{CE} > 0.2V$ .

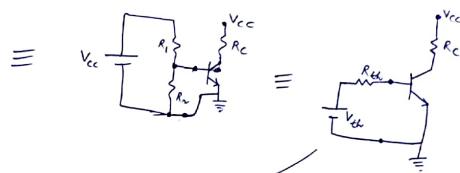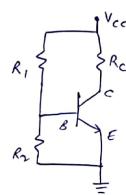

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{th} = \frac{V_{CC} \cdot R_2}{R_1 + R_2}$$

$$V_{th} = V_{BE} + I_B R_{th} + R_C (I_B + I_C)$$

Assume active  $\Rightarrow V_{BE} = 0.7V$

$$I_B = \frac{V_{th} - 0.7}{R_{th}}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - I_C R_C \quad \text{Need } V_{CE} > 0.2V$$

Self biasing circuit.

4)  $V_1 = V_{DD}$ ,  $V_2 = V_{DD} \Rightarrow M_1 = ON$ ;  $M_3, M_4 = OFF \Rightarrow I_D = 0$

$$M_2: V_{GS2} = V_2 - V_{DS} = V_{DD} - V_{DS}$$



$M_1$  ON but no current  $\Rightarrow V_{DS1} = 0 \Rightarrow V_{GS2} = V_{DD}$   
 $\Rightarrow M_2 = ON$ .

$M_2$  ON but no current  $\Rightarrow V_{DS2} = 0 \Rightarrow V_o = 0$ .

$V_1$	$V_2$	$V_o$
0	0	1
1	0	1
0	1	1
1	1	0


$\Rightarrow$  NAND Gate.


### CMOS NOR GATE:- HW

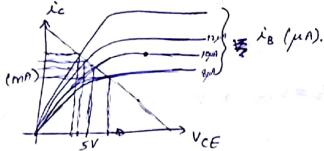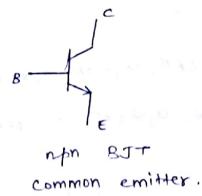


$$\frac{I_c}{I_B} = \beta = 100 \quad \Rightarrow \quad \frac{\Delta I_c}{\Delta I_B} = 100.$$

(active) current amplification

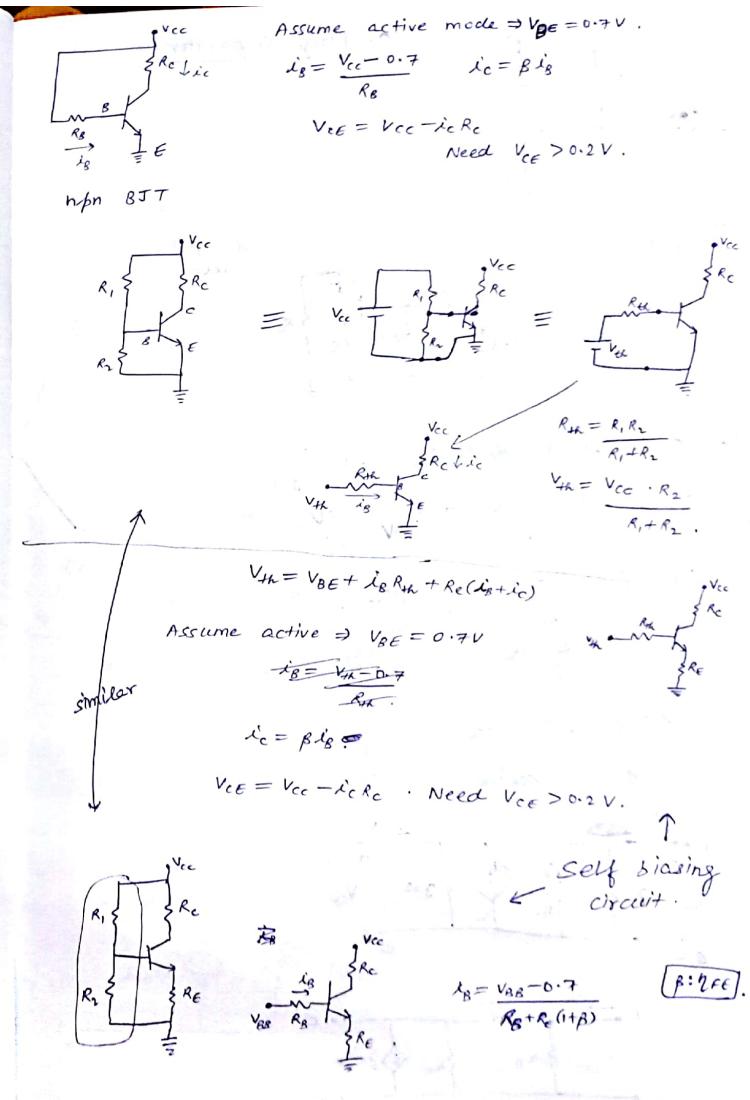

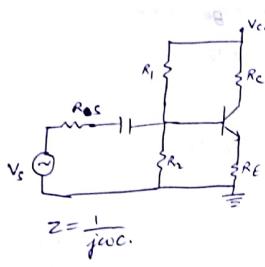

Coupling capacitor


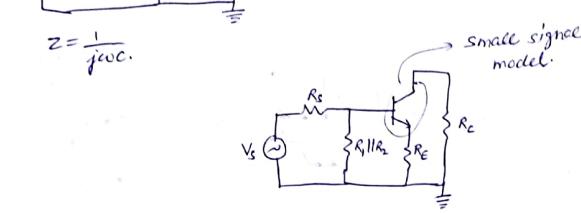


$$i_B \leftarrow S I_B = \left( \frac{\partial I_B}{\partial V_{BE}} \right) V_{BE} + \left( \frac{\partial I_B}{\partial V_{CE}} \right) V_{CE}$$

$$i_C \leftarrow S I_C = \left( \frac{\partial I_C}{\partial V_{BE}} \right) V_{BE} + \left( \frac{\partial I_C}{\partial V_{CE}} \right) V_{CE}$$

$$i_1 = g_{11} V_{be} + g_{12} V_{ce}$$

$$i_2 = g_{21} V_{be} + g_{22} V_{ce}$$

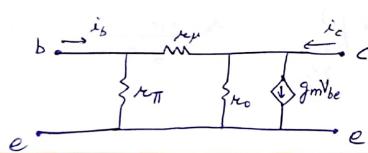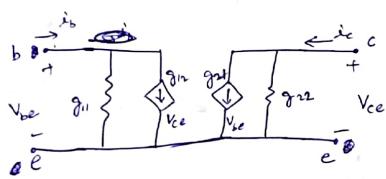

$$i_b = \frac{V_{be}}{r_\pi} + \frac{V_{be}}{r_\mu}$$

$$i_c = g_m V_{be} + \frac{V_{ce}}{r_o} + \frac{V_{ce}}{r_\mu} \rightarrow -V_{ce}$$

$$\text{Use: } V_{bc} = V_{be} - V_{ce}$$

$$i_b = \frac{V_{bc}}{r_\pi} + \frac{V_{bc}}{r_\mu} - \frac{V_{ce}}{r_\mu}$$

$$i_c = g_m V_{bc} + \frac{V_{ce}}{r_o} + \frac{V_{ce}}{r_\mu} \neq \frac{V_{bc}}{r_\mu}$$

$$g_{11} = \frac{1}{r_\pi} + \frac{1}{r_\mu}, \quad g_{12} = -\frac{1}{r_\mu}$$


$$g_{21} = g_m \neq -\frac{1}{r_\mu}, \quad g_{22} = \frac{1}{r_o} + \frac{1}{r_\mu}$$

Choose  $I_B, V_{ce}$

$$V_{BE}(I_B, V_{ce}), \quad I_C(I_B, V_{ce})$$

$$V_{be} = \left( \frac{\partial V_{BE}}{\partial I_B} \right) i_b + \left( \frac{\partial V_{BE}}{\partial V_{ce}} \right) V_{ce}$$
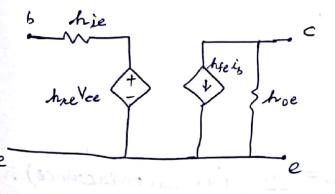
$$i_c = \left( \frac{\partial I_C}{\partial I_B} \right) i_b + \left( \frac{\partial I_C}{\partial V_{ce}} \right) V_{ce}$$



$$i_b = g_{11} V_{be} + g_{12} V_{ce}$$

$$i_c = g_{21} V_{be} + g_{22} V_{ce}$$

Assume active region,

$$g_{11} = \left( \frac{\partial I_B}{\partial V_{BE}} \right)_{V_{CE}}$$


$$I_B = A e^{V_{BE}/V_T}$$

$$= \frac{I_B}{V_T}$$

$$g_{12} = \left( \frac{\partial I_B}{\partial V_{CE}} \right)_{V_{BE}} \approx 0$$

$$g_{21} = \left( \frac{\partial I_C}{\partial V_{BE}} \right)_{V_{CE}} = \frac{I_C}{V_T}$$
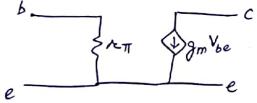
$$g_{22} = \left( \frac{\partial I_C}{\partial V_{CE}} \right)_{V_{BE}} \approx 0$$





$$\kappa_\mu = -\frac{1}{g_{12}}, \quad r_\pi = \frac{1}{g_{11} g_{12}}, \quad r_o = \frac{1}{g_{21} g_{22}}$$

$$\kappa_\mu = \frac{1}{g_{12}}, \quad r_\pi = \frac{1}{g_{11}}, \quad r_o \approx \infty$$

$$g_m = g_{21} - g_{12} = g_{21}$$

$$r_\pi = \frac{V_T}{I_B}, \quad g_m = \frac{I_C}{V_T}$$

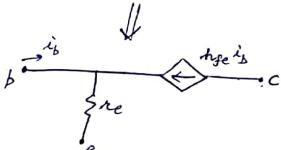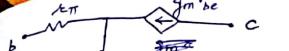
$$r_\pi g_m = \frac{I_C}{I_B} = \frac{I_C}{I_B} = h_{fe} \quad g_m = \frac{h_{fe}}{r_\pi} = (+\text{transconductance})$$



$$i_b = \frac{V_{be}}{r_\pi} - h_{fe} i_b$$

$$\Rightarrow i_b (1 + h_{fe}) = \frac{V_{be}}{r_\pi}$$
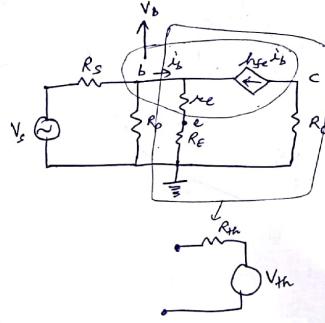
$$\Rightarrow r_e = \left( \frac{V_{be}}{i_b} \right) \cdot \frac{1}{(h_{fe} + 1)} = \frac{r_\pi}{(1 + h_{fe})}$$




$$R_{TH} = R_{TRE}: \quad R_{TH} = (1 + h_{fe})(R_E + r_\pi)$$

$$V_{TH} = 0.$$

$$V_o = \frac{I}{R_L} \cdot R_{TH} = \frac{V}{R_L}.$$

$$V = (I + h_{fe} I)(R_E + r_\pi)$$
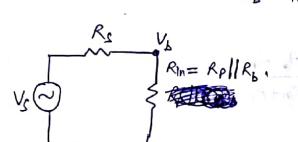
$$\Rightarrow \frac{V}{I} = (1 + h_{fe})(R_E + r_\pi) = R_{TH}$$



$$V_{OC} = 0 \Rightarrow \text{No } i_b \& no \text{ voltage.}$$

$$\Rightarrow V_{TH} = 0.$$

### AC Voltage gain


$$A_v = \frac{V_c}{V_b} = -\frac{R_c h_{fe} i_b}{R_b + R_E}$$

$$\Rightarrow A_v = -\frac{R_c}{h_{fe} + R_E}.$$

$$A_{VS} = \frac{V_c}{V_s}$$

$$V_b = \frac{R_{in}}{R_{in} + R_S} V_s$$
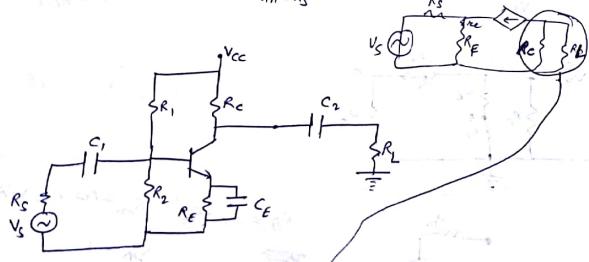
$$A_{VS} = \frac{V_c}{V_b} \cdot \frac{V_b}{V_s} = A_v \cdot \frac{R_{in}}{R_{in} + R_S}$$




$$R_b \approx (1+h_{fe}) (R_E + R_E)$$

$$R_{in} = R_2 // R_b$$


$$A_v = -\frac{R_C}{R_{in} + R_E}$$
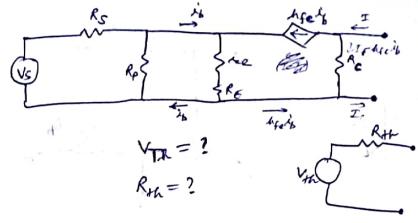
$$A_{VS} = \frac{A_v R_{in}}{R_{in} + R_S}$$



$$V_{TH} = ?$$

$$R_{TH} = ?$$

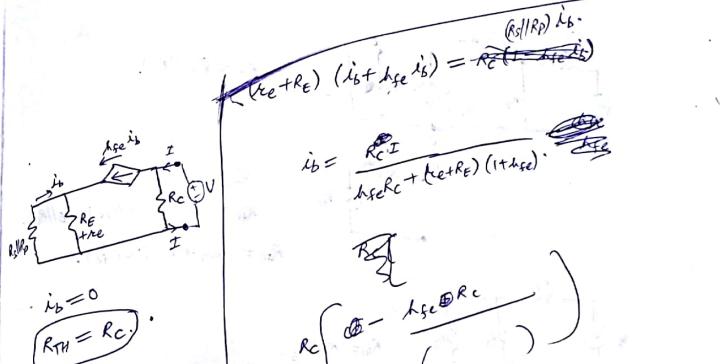

$$i_B = \frac{R_C I}{h_{fe} r_{ce} + (R_E + R_E) (1 + h_{fe})}$$

### AC current gain

$$A_i = \frac{i_L}{i_B} = \frac{[h_{fe} i_b] \cdot (R_C)}{R_C + R_L}$$

$$\Rightarrow A_i = \frac{h_{fe} R_C}{R_C + R_L}$$






$$i_B = \frac{R_P i_S}{R_P + R_b}$$

$$\Rightarrow A_{iS} = \frac{i_L}{i_S} = \left( \frac{i_L}{i_B} \right) \left( \frac{i_B}{i_S} \right)$$

$$R_C \left( 1 - \frac{R_C h_{fe}}{h_{fe} R_C + (R_E + R_E) (1 + h_{fe})} \right)$$

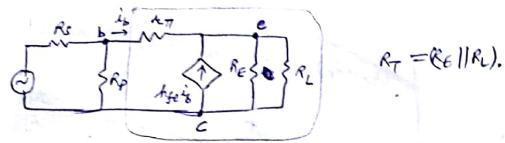
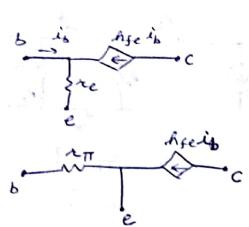
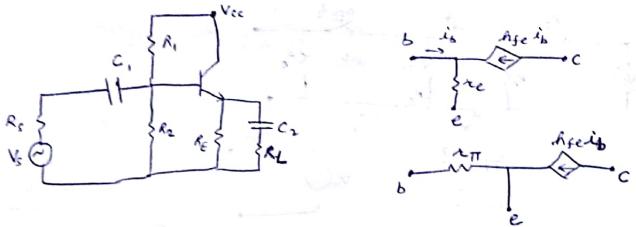
$$= R_C \cdot \frac{(R_E + R_E) (1 + h_{fe})}{h_{fe} R_C + (R_E + R_E) (1 + h_{fe})}$$



$$V_{be} = 0.$$

$$R_{in} = h_{ie} + (1 + h_{fe}) (R_E || R_L).$$

$$R_{out} = h_{re} + R_T (1 + h_{fe}).$$

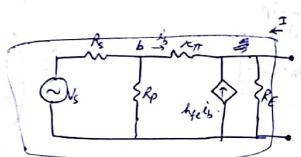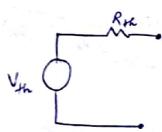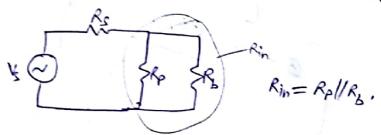

$$\lambda_b = -V/R$$

$$\lambda_{pE} = V/R_E$$



$$\Rightarrow i_b + h_{fe} i_b - \frac{V}{R_E} + I = 0$$

$$i_b (\lambda_{pE} + R_p || R_S) = R_E (1 + h_{fe}) (i_b + h_{fe} i_b + R_E I)$$

$$\Rightarrow (1 + h_{fe}) i_b = \frac{V}{R_E} - I. \Rightarrow V_I = R_E \parallel \frac{R}{(1 + h_{fe})}$$

buffer =  $\begin{cases} R_o \text{ small} \\ R_{in} \text{ large} \\ A_{vs} \approx 1 \end{cases}$


n-channel JFET

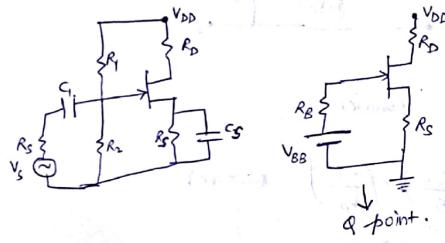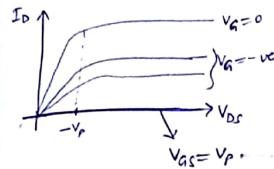

$$I_D = I_{DSS} \left[ 2 \left( \frac{V_{GS} - V_P}{V_P} \right) V_{DS} - \left( \frac{V_{DS}}{V_P} \right)^2 \right] \quad \text{ohmic region.}$$

$$I_{D, \text{sat}} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 \quad \text{sat.}$$

$$V_{D, \text{sat}} = V_{GS} - V_P$$

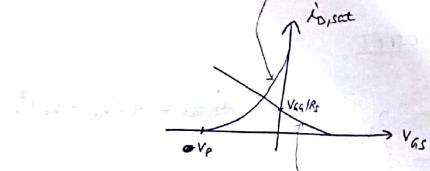

$$\text{Load line: } V_{GG} = I_D R_S + V_{GS}.$$


Need small signal model:-

$$I_D (V_{GS}, V_{DS})$$

$$I_G (V_{GS}, V_{DS})$$

$$i_{ds} = \left( \frac{\partial I_D}{\partial V_{GS}} \right) V_{GS} + \left( \frac{\partial I_D}{\partial V_{DS}} \right) V_{DS}$$

$$g_d \approx 0$$

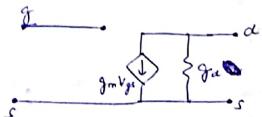


$$g_m = I_{DSS} \cdot \frac{2 V_{DS}}{V_P^2} \quad (\text{ohmic})$$

$$= 2 I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right) \cdot \left( \frac{-1}{V_P} \right) \quad (\text{active})$$



$$g_m = -\frac{2}{V_P} \sqrt{I_D \cdot I_{DSS}}$$

(enhancement)






n-channel MOSFET

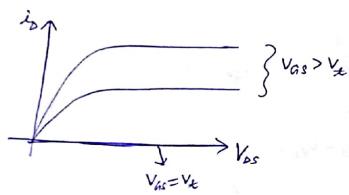
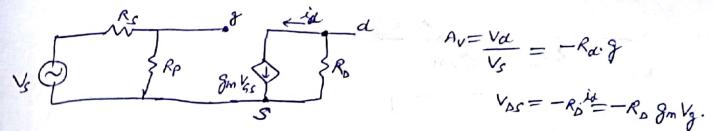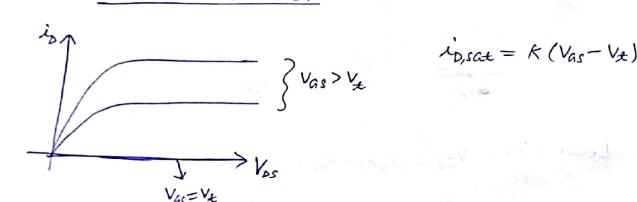
$$i_{D, \text{sat}} = K (V_{GS} - V_T)^2$$




Summary :-

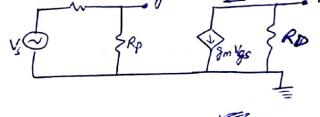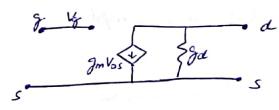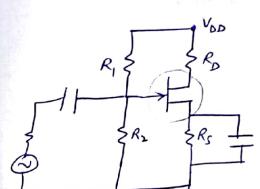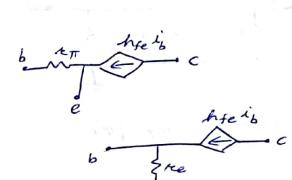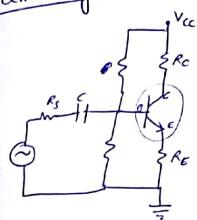


$$V_D = -g_m V_{GS} \cdot R_D$$

Common-drain amplifier  
buffer

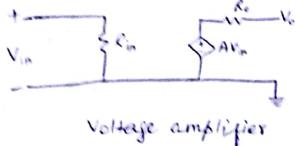
$$V_O \approx V_I, R_{out} \approx 0, R_{in} \rightarrow \infty$$




Voltage amplifier

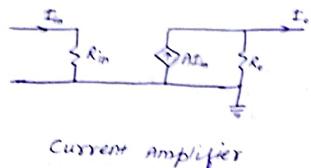


Current amplifier

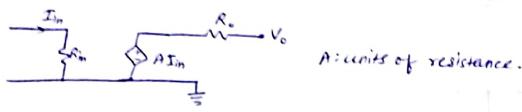

trans-resistance ampl.

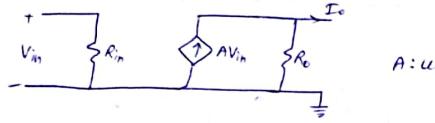

trans-conductance amp.

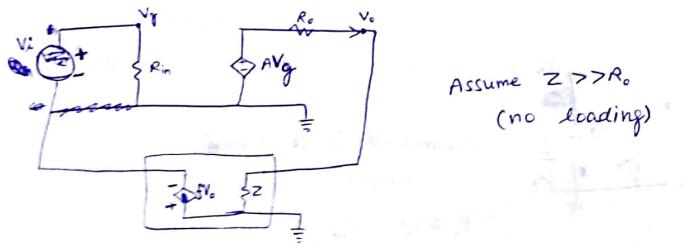

series-shunt feedback

Assume  $Z \gg R_o$   
(no loading)

$$\begin{aligned} V_o &= A V_g \\ V_g &= V_i - f V_o \end{aligned} \quad \Rightarrow \quad V_g = \frac{V_o}{A}$$

$$\Rightarrow \frac{V_o}{A} = V_i - f V_o$$

$$\Rightarrow V_o = V_i \left( \frac{A}{1+Af} \right), \quad \text{overall gain}$$

$$A_F = \frac{A}{1+Af}.$$

If  $Af = +ve$ , overall gain  $\downarrow$ . (-ve feedback)

If  $Af = -ve$ , overall gain  $\uparrow$ . (+ve feedback)

If  $Af = -1$ ,  $|A_F| \rightarrow \infty$ .

If  $Af = -2$ ,  $A_F = \frac{A}{-1} = -A \times$

for  $|Af| < 1$ ,  $A_F = A(1-Af + (Af)^2 - \dots)$

Gain =  $A$

feedback =  $-f$ .

Add  $-f V_o$  to  $V_{oi}$


extra input =  $-f A V_i$

Net output =  $A V_i - A_f A V_i$ .

extra input =  $f A f A V_i$ .

Net output =  $A V_i (1 - Af + (Af)^2 - \dots)$

Stability

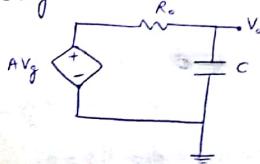

$$\Leftrightarrow C \frac{dV_g}{dt} = i$$

$$A V_g = i R_o + V_o = C \frac{dV_o}{dt} R_o + V_o$$

$$\text{Put } V_g = V_o - f V_o$$

$$CR_o \frac{dV_o}{dt} + (1+A_f) V_o = AV_i$$

Put  $V_i = 0$ . Then  $V_o = 0$  stable ??

Try  $V_o = V_o(t=0) e^{-\tau/t}$

$$\frac{dV_o}{dt} = -\frac{V_o}{\tau} \Rightarrow \frac{CR_o}{\tau} + (1+A_f) = 0$$

$$\Rightarrow \tau = \frac{CR_o}{1+A_f}. \quad \text{If } A_f < -1, \tau < 0$$

$V_o$  diverges.  
Not stable.

$$A_f = \frac{A}{1+A_f}$$

$A_f$  = loop gain


If  $A_f = -1$ , oscillations start

Barkhausen criteria


loading

$$V_o = A V_g \frac{Z}{R_o + Z} = \left( \frac{AZ}{R_o + Z} \right) V_g \xrightarrow{A'}$$
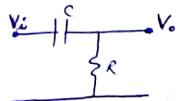
$$\begin{aligned} V_o &= A' V_g \\ V_g &= V_i - f V_o \end{aligned} \quad \left. \begin{aligned} A' &= \frac{A'}{1+A'f} \\ A' &= -1 \rightarrow \text{Barkhausen criteria.} \end{aligned} \right.$$






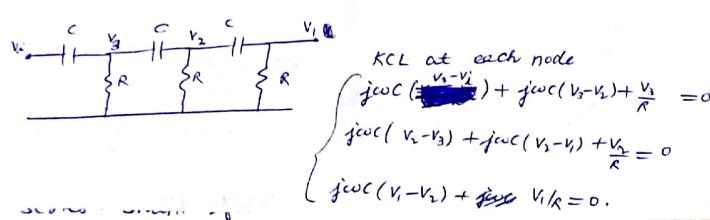
$$V_o = \frac{V_g}{R + \frac{1}{j\omega C}} \cdot R$$



Need

$$\frac{V_i}{V_o} = \dots$$
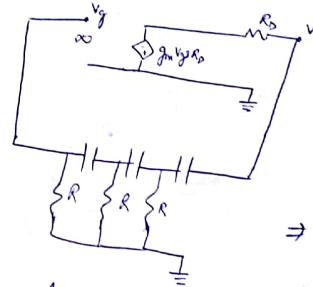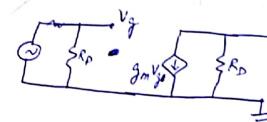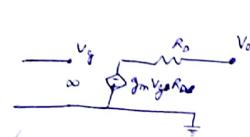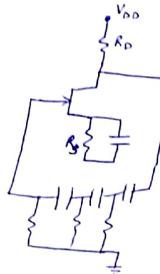
$$\text{At } \omega = \omega_0 = \frac{1}{RC\sqrt{2}}, \quad \frac{V_i}{V_o} = \frac{-1}{2\sqrt{2}}.$$



$$R \gg R_D \quad (\text{no loading})$$


$$\Rightarrow A = -g_m R_o$$

$$f = \frac{1}{2\pi} \text{ at } \omega = \omega_0 = \frac{1}{RC\sqrt{2}}$$


Need  $A_f \leq -1$ .

$$-\frac{g_m R_D}{2\pi} \leq -1 \Rightarrow g_m R_o \geq 2\pi$$

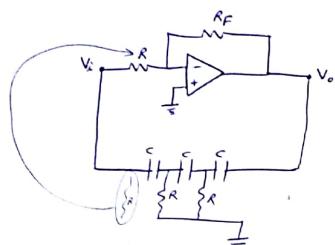
$$\boxed{g_m \geq \frac{2\pi}{R_D}} \quad \text{oscillations at } \omega = \omega_0$$


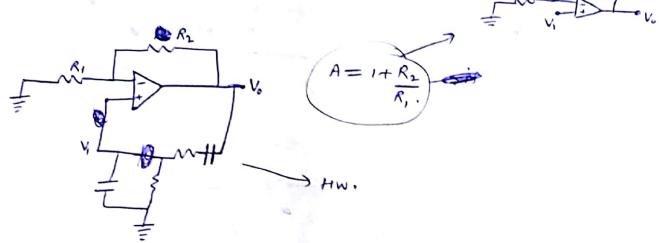
$$A = -\frac{R_F}{R} \quad (\text{gain})$$



H.W.

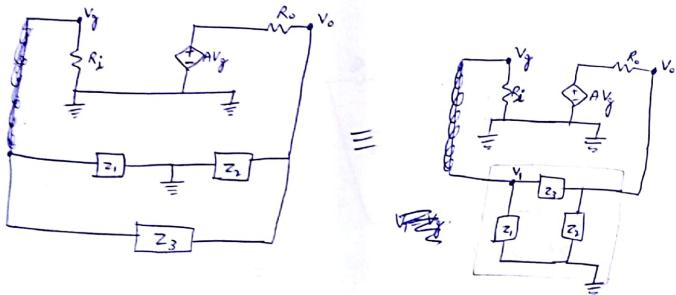

$$\frac{V_i}{Z_1} + \frac{V_i - V_o}{Z_3} = 0 \quad (R_0 \rightarrow \infty).$$

$$\Rightarrow V_i = \left( \frac{Z_1}{Z_1 + Z_3} \right) V_o \rightarrow -f.$$

$$\frac{V_o}{Z_2} + \frac{V_o - V_i}{Z_3} + \frac{V_o - A'V_g}{R_0} = 0 \quad \text{Plot}$$

Plot

$$V_o = A'V_g$$

$$A' = \frac{AZ_2(Z_1 + Z_3)}{R_0(Z_1 + Z_2 + Z_3) + Z_2(Z_1 + Z_3)}.$$

$$\text{Loop gain} = A'f = \frac{-AZ_1Z_2}{R_0(Z_1 + Z_2 + Z_3) + Z_2(Z_1 + Z_3)}.$$

$$\text{Assume } Z = jX$$

$$X = \omega L \quad (\text{ind.})$$

$$X = \frac{1}{\omega C} \quad (\text{cap.})$$

$$= \frac{AX_1X_2}{R_0(X_1 + X_2 + X_3) - X_2(X_1 + X_3)}$$

$$\text{Put } X_1 + X_2 + X_3 = 0$$


$$\text{loop gain} = -\frac{AX_1}{X_1 + X_3} = \frac{AX_1}{X_2}.$$

Choose  $X_1 = \text{cap.}$

$X_2 = \text{cap.}$

$X_3 = \text{ind.}$

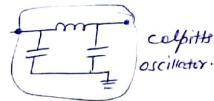Resonant circuit osc.  $\rightarrow (L-C \text{ circuit})$



$$\frac{1}{\omega C_1} = -\frac{1}{\omega C_2} + \omega L_3 = 0 \Rightarrow \omega = \frac{1}{\sqrt{L_3 \frac{C_1 C_2}{C_1 + C_2}}}.$$

$$A = -j\omega R_D$$


$$R_D j\omega \frac{C_2}{C_1} \geq 1.$$

$$X_1 = \text{ind.}$$

$$X_2 = \text{ind.}$$

$$X_3 = \text{cap.}$$
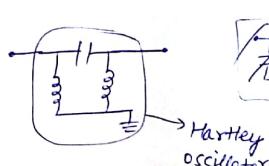
$$\omega_0^2 L_1 + \omega_0^2 L_2 - \frac{1}{\omega_0^2 C_3} = 0 \Rightarrow \omega_0 = \frac{1}{\sqrt{C_3(L_1 + L_2)}}$$




$$R_D j\omega \frac{L_1}{L_2} \geq 1.$$

Colpitts oscillator.


RESONANT

TUNNELING

DIODE (RTD)

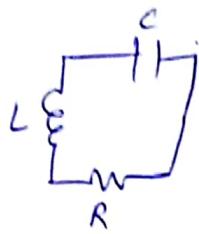

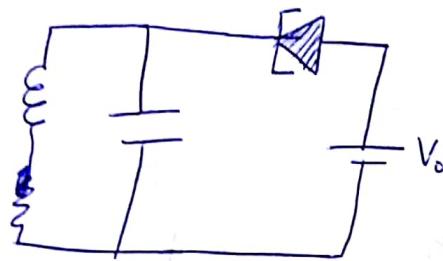
$$\text{differential resistance} = \frac{\partial V}{\partial I} = -\text{ve.}$$



$$(\int fg \, dx) \leq (\int g^2 \, dx) (\int f^2 \, dx).$$

$$V_{AV}(\hat{\theta}; \hat{o}) \geq \frac{1}{I(\hat{o})}$$


[EE 101]

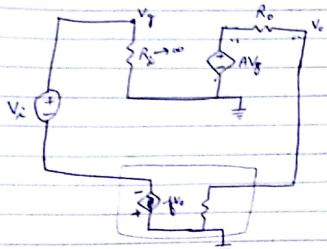

$$V_o = AV_g$$

$$V_g = V_x - fV_o$$

$$\Rightarrow V_o = \frac{A}{1+Af} V_x$$

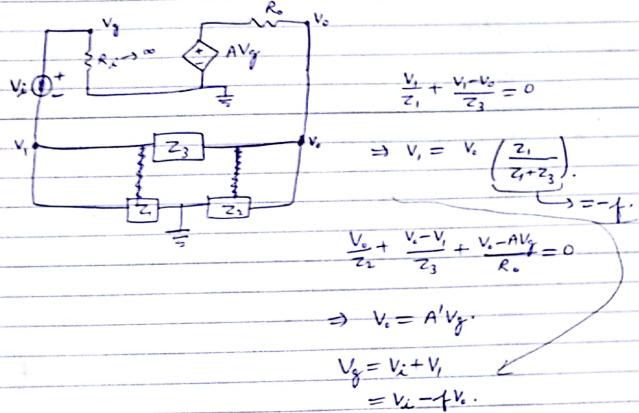

$$\frac{V_1}{Z_1} + \frac{V_o - V_1}{Z_3} = 0$$

$$\Rightarrow V_i = V_1 \left( \frac{Z_1}{Z_1 + Z_3} \right)$$

$$\frac{V_o}{Z_2} + \frac{V_i - V_1}{Z_3} + \frac{V_i - AV_g}{R_o} = 0$$

$$\Rightarrow V_i = A'V_g$$

$$V_g = V_i + V_1$$



$$= V_o - fV_o$$

$$V_{AV}(\hat{\theta}; \hat{o}) \geq \frac{1}{I(\hat{o})}$$

[EE 101]

### Resonant Tunneling Diode (RTD)

Vander Pol oscillator

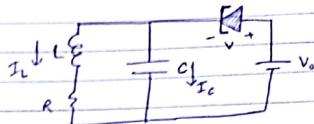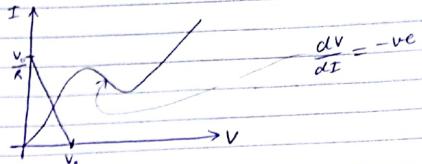

$$V_o = V + iR$$

$$I = I_c + I_L$$

$$\text{Put } I_c = C \frac{d}{dt}(V_o - V) \\ = -C \frac{dV}{dt}$$

$$V_L + i_L R = V_o - V$$

$$\Rightarrow L \frac{d}{dt} i_L + i_L R = V_o - V$$


$$\Rightarrow L \frac{d}{dt} (I - i_L) + i_L R = V_o - V \Rightarrow L$$

$$\Rightarrow L \frac{dI}{dt} + L \frac{cd^2V}{dt^2} + (f + C \frac{dV}{dt}) R = V_o - V$$

$$\downarrow \frac{df}{dv} \cdot \frac{dv}{dt}$$

$$\Rightarrow L C \frac{d^2V}{dt^2} + \left[ L \frac{df}{dv} + RC \right] \frac{dV}{dt} + Rf + V = V_o$$

$I = f(V)$  some function,

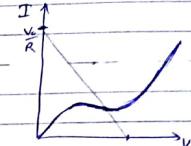

If  $V = \text{const.} \Rightarrow V = V_0$ .

Put  $V = V_0 + v(t)$


$$LC \frac{d^2v}{dt^2} + \left[ L \left( \frac{df}{dv} \right) + RC \right] \frac{dv}{dt} + Rf + v = 0.$$

$$\Rightarrow \frac{dv}{dt^2} + t \left[ \frac{1}{C} \left( \frac{df}{dv} \right) + \frac{R}{L} \right] \frac{dv}{dt} + \cancel{Rf} + \frac{v}{LC} = 0$$

Series RLC circuit

$$\text{Use } v = e^{st} \Rightarrow s^2 + \frac{R}{L}s + \frac{1}{LC} = 0.$$
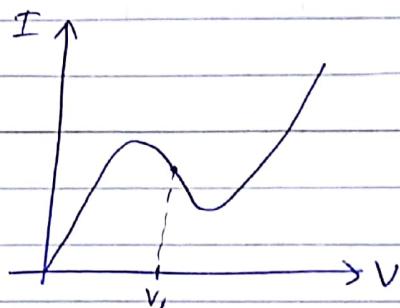
$$\Rightarrow s = \left( -\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}} \right) / 2.$$



$$j\dot{x} + \mu(x^2 - 1)x + \omega^2 x = 0$$

if  $|x| < 1$ , damping = -ve }  
if  $|x| > 1$ , damping = +ve }.

## Magnetic circuits


$$\vec{E} = \frac{1}{4\pi\epsilon_0} \cdot \frac{q}{r^2} \hat{r}$$



$$\vec{E} = \frac{1}{4\pi\epsilon_0} \int f(\vec{r}) \frac{\vec{r} \cdot \vec{r}'}{|\vec{r}-\vec{r}'|^3} \cdot d\vec{r}'$$

$$\vec{B} = \frac{\mu_0}{4\pi} \int J(\vec{r}) \times \frac{\vec{r} \cdot \vec{r}'}{|\vec{r}-\vec{r}'|^3} d\vec{r}' \Rightarrow H = \frac{1}{4\pi} \int$$

Permeability of vacuum.

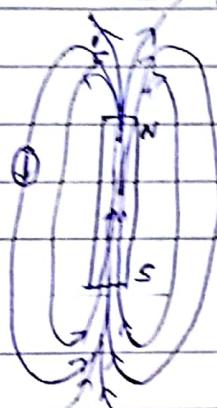

flux  
lines.

$$B = \frac{\Phi}{A} \quad \text{④} \frac{\text{Webers}}{\text{m}^2} = \text{tesla}$$

$$\vec{F} = q(\vec{v} \times \vec{B}) + q\vec{E}.$$


B = Magnetic flux density:

(magnetic induction)

$$B = \mu H.$$

H = Magnetic field

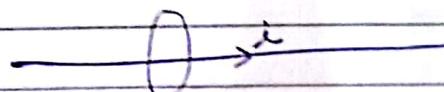
$$* \nabla \times \vec{H} = \vec{J} \Rightarrow \vec{H} \cdot d\vec{l} = i$$



$$H \cdot 2\pi r = i$$

$$\Rightarrow H = \frac{i}{2\pi r}$$

$$\Rightarrow B = \frac{\mu i}{2\pi r}$$

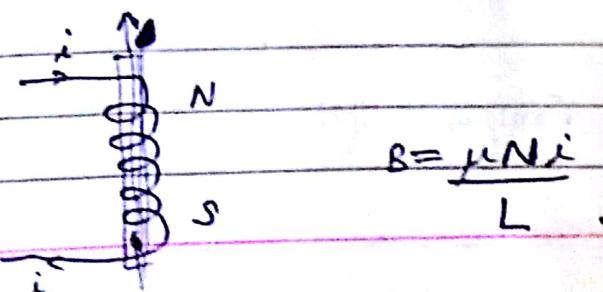

$$B = \mu_0 N i$$

$$L$$



$$\text{flux } \phi = BA$$

$$\phi = \frac{\mu_0 N A}{l} (i)$$

Magnetomotive force  $\mathcal{F} = Ni$ .

$$\phi = \frac{\mathcal{F}}{R}, R = \frac{l}{\mu A}$$

R: Reluctance.

Electrical  
Current i  
Voltage V  
Resist. R  
Ohm's law  $V = iR$   
 $(R = \frac{V}{i})$ .



Magnetic  
Flux  $\phi$

~~reluctance & mmf F~~

reluctance R


$$F = \phi R$$

$$(R = \frac{l}{\mu A})$$

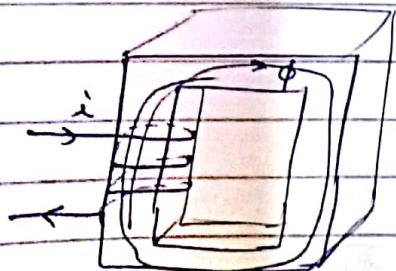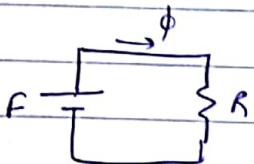

$$\left. \begin{array}{l} R_c = \frac{l}{\mu A} \\ \mathcal{F} = Ni \end{array} \right\} \phi = \frac{\mathcal{F}}{R_c}$$

$$B = \frac{\phi}{A}$$

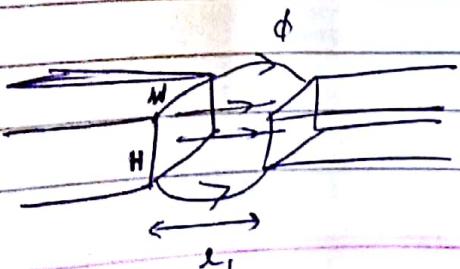

Fringing flux.

130 | 126



$$\text{Effective area} = (W + l_1)(h + l_1)$$

$$\mu = \mu_0$$


$$R = R_c + R_{\text{gap}}$$

$$R_{\text{gap}} \gg R_c$$
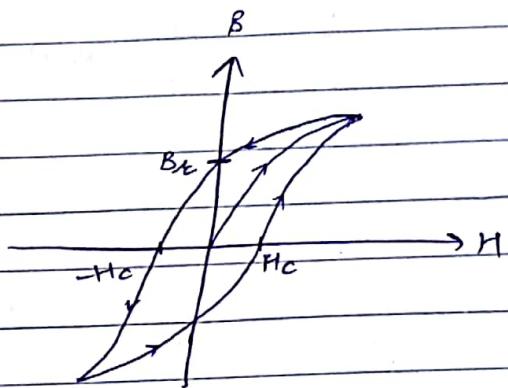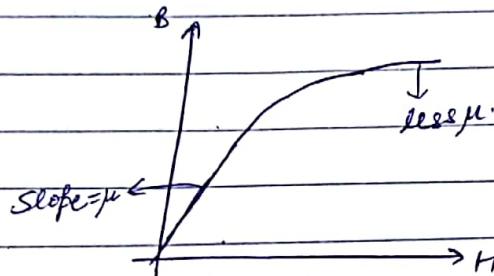
$$\mu \approx 1000 \mu_0, \quad B = \mu H.$$



### - TRANSFORMER :-

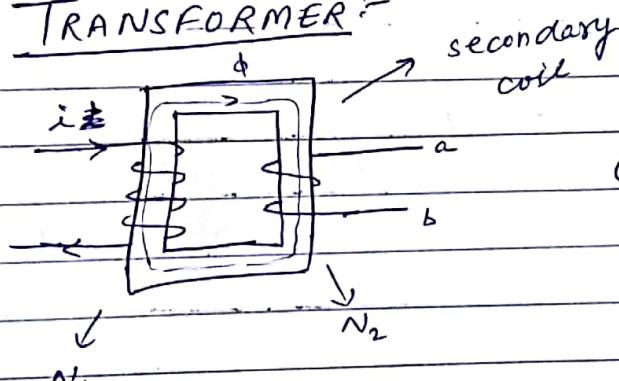

Hysteresis,  
↓  
(loss).

$$\phi = \frac{N_1 i}{R}$$

$$\text{inductance: } V(t) = \frac{d\phi}{dt}$$

$$V = \frac{di}{dt}$$

self  
inductance

Primary  
coil

Magnetically  
coupled:


$$V_{ab} = N_2 \frac{d\phi}{dt}$$

$$= \frac{N_2 N_1}{R} \frac{di}{dt}$$

Henry(H).

$$\Rightarrow V_{ab} = M \frac{di}{dt}$$

M: mutual  
inductance

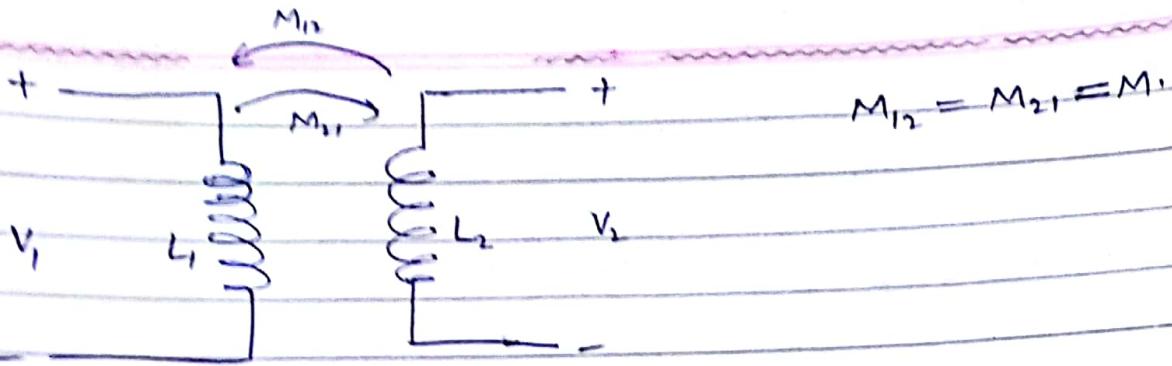

$$M_{12} = M_{21} = M_1$$

$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$\text{Energy stored (W)} = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2$$

$$V = L \frac{di}{dt}$$

$$\text{Energy} = \int V i dt$$

$$= \int L i \frac{di}{dt} dt$$

$$= \frac{1}{2} L i^2$$

$$\text{Energy} = \int (V_1 i_1 + V_2 i_2) dt$$


$$= \int \left( L_1 \frac{i_1}{dt} + L_2 \frac{i_2}{dt} + M i_1 \frac{d i_2}{dt} + M i_2 \frac{d i_1}{dt} \right) dt$$

$$= \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2$$

$$M \leq \sqrt{L_1 L_2} \quad \text{put } i_2 = x i_1$$

$$x \geq 0 \quad x \in \mathbb{R}$$

EE101

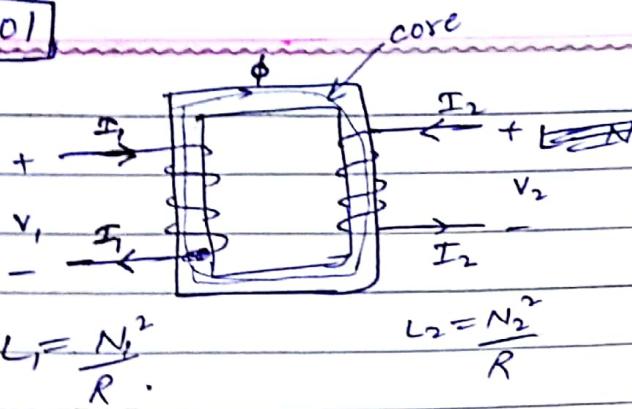


$$M \leq \sqrt{L_1 L_2}$$

$$L_1 = \frac{N_1^2}{R}$$

$$L_2 = \frac{N_2^2}{R}$$

$$\text{If } M = \sqrt{L_1 L_2} = \frac{N_1 N_2}{R} \Rightarrow K = 1.$$
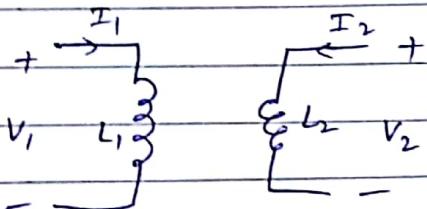
$$\text{Coupling coefficient } = \frac{M}{\sqrt{L_1 L_2}}.$$



$$\bar{V}_1 = j\omega L_1 \bar{I}_1 + j\omega M \bar{I}_2$$

$$\Rightarrow \bar{I}_1 = \bar{V}_1 - j\omega M \bar{I}_2$$

$$j\omega L_1$$

≠

$$\bar{V}_2 = \bar{V}_1 - j\omega L_2 \bar{I}_2$$

$$\bar{V}_2 = j\omega L_2 \bar{I}_2 + j\omega M \bar{I}_1$$

$$\bar{V}_2 = \frac{M \bar{V}_1}{L_1} - \frac{j\omega M^2 \bar{I}_2}{L_1} + j\omega L_2 \bar{I}_2$$

$$\text{Assume } K=1 \Rightarrow M=\sqrt{L_1 L_2}.$$

$$\bar{V}_2 = \sqrt{\frac{L_2}{L_1}} \bar{V}_1 = N \bar{V}_1.$$

$$L_2 = \frac{N_2^2}{R}, L_1 = \frac{N_1^2}{R} \Rightarrow N = \frac{N_2}{N_1}.$$

$N > 1 \Rightarrow$  Step up transformer

$N < 1 \Rightarrow$  Step down --


$N = 1 \Rightarrow$  Isolation.

$$\frac{\bar{V}_1}{j\omega L_1} - \frac{(M\bar{I}_2)}{L_1} = -N\bar{I}_2.$$

$L_1 \rightarrow \infty$   
 $L_2 \rightarrow \infty$   
 $N = \text{constt.}$   
 $K=1$   
Ideal transformer

$$\bar{I}_1 = -N\bar{I}_2 \quad \text{or} \quad \bar{I}_2 = -\frac{\bar{I}_1}{N}$$


$$\bar{V}_2 = N\bar{V}_1.$$

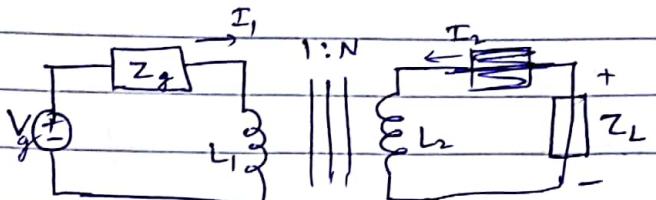

$$V_{OC} = ?$$

$$V_g = Z_g I_1 + V_1 = V_1.$$
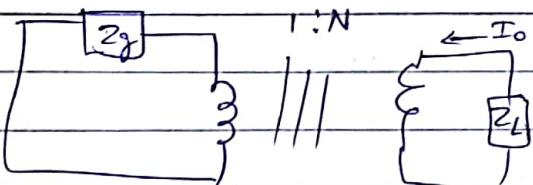
$$\Rightarrow V_{OC} = V_1 = NV_1 = NV_g.$$



$$V_1 = -Z_g I_1$$

$$= -Z_g (-N I_o)$$

$$= N Z_g I_o$$

$$V_o = N V_1 = N (N Z_g I_o)$$

$$Z_o = \frac{V_o}{I_o} = N^2 Z_g.$$

