

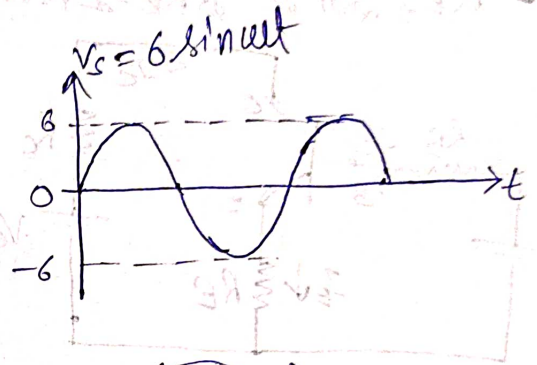


Tutorial(6)

Qus. 4)

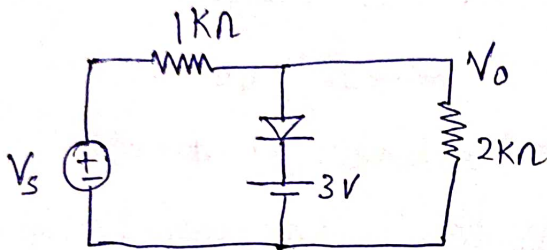

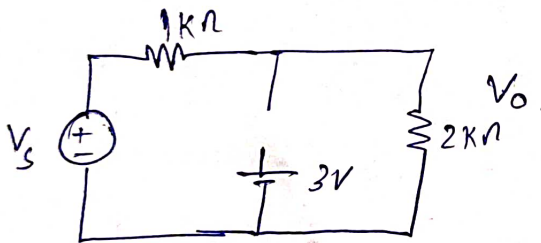initially diode OFF so, $(-6V \leq V_s \leq 4.5V)$




$$V_o = \frac{2}{3} V_s \Rightarrow V_o = 4 \sin \omega t$$

~~diode~~

for diode to be ON when $V_o > 3V$



from relation $V_o = \frac{2}{3} V_s$
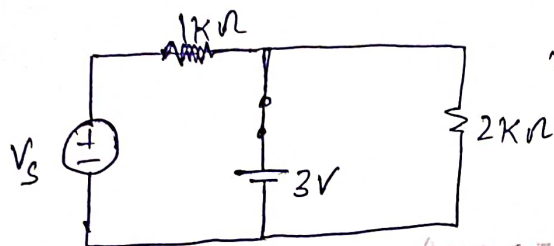
$$3 > \frac{2}{3} V_s \Rightarrow V_s > 4.5V$$




$$V_o = 3V$$

Transfer C/s 1:-

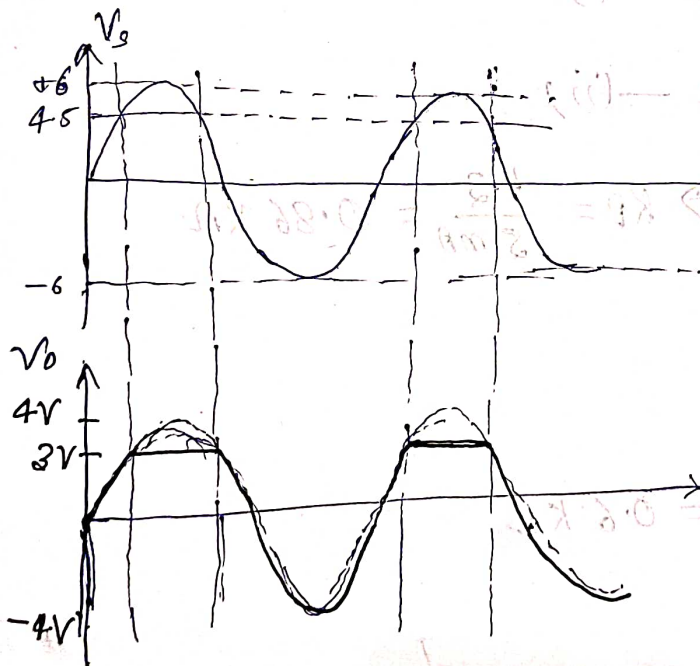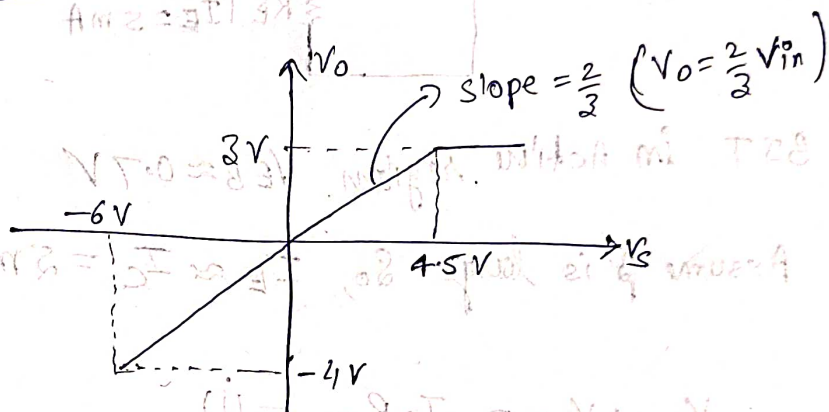


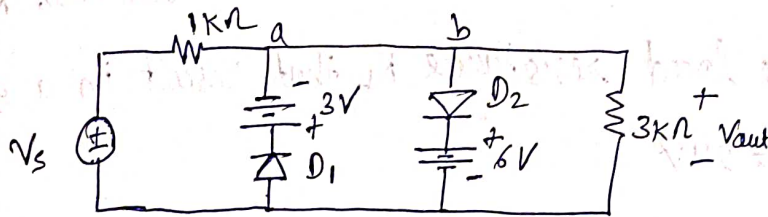Q1) $V_s = 12 \sin \omega t \text{ V}$, $V_{out} = ?$



Soln:-


Range of input	D_1	D_2	V_{out}
① $-12 \leq V_i \leq -4V$	ON	OFF	-3V
② $-4V \leq V_i \leq 8V$	OFF	OFF	$\frac{3}{4} V_s$
③ $8V \leq V_i \leq 12V$	OFF	ON	6V

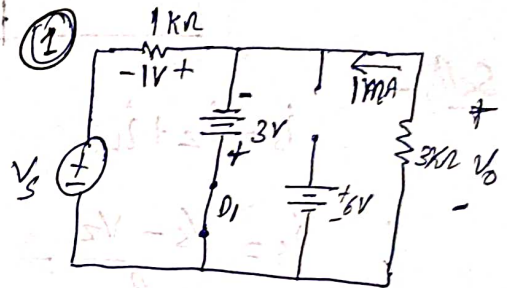

So, $V_o = -3V$
 $I = \frac{V_o}{3k\Omega} = 1mA$

$V_s = -1V + V_o$


$V_s = -4V$

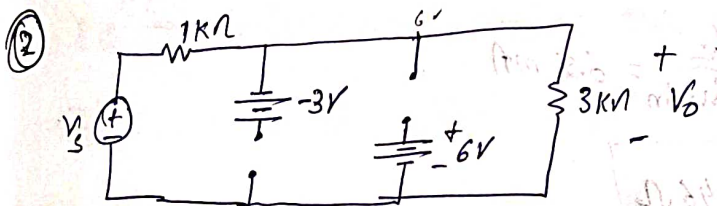

$V_o = \frac{3}{4} V_s$



If D_2 is going to ON then $V_o = +6V$ So condition for V_s

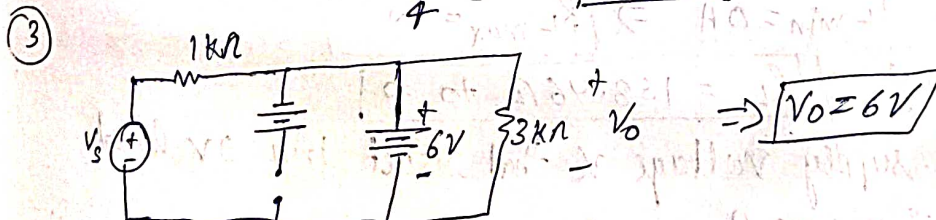is $6 = \frac{3}{4} V_s \Rightarrow V_s = 8V$




$\Rightarrow V_o = 6V$

Voltage transfer characteristics (VTC):

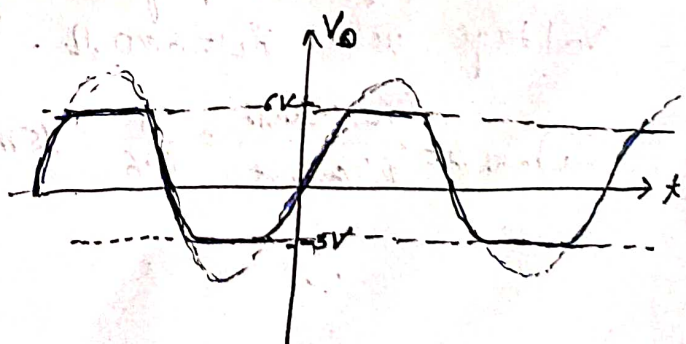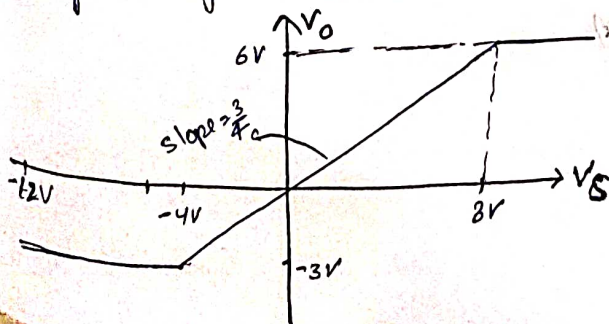

Q.2> Break down voltage of zener diode is 9V and operate with a reverse current between 10 and 100mA. Given that $R = 200\Omega$

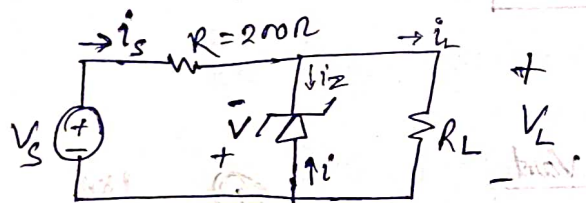(a) Find the range of the load resistance R_L that result in a 9V load voltage when $V_S = 24V$



Solⁿ:-

$$i_S = i_Z + i_L$$

$$i_S = \frac{V_S - V_Z}{R} = \frac{24 - 9}{200} = 75 \text{ mA}$$

$$i_L = \frac{V_Z}{R_L} = \frac{9}{R_L}$$

$$i_S = i_{Z \min} + i_{L \max}$$

$$75 \text{ mA} = 10 \text{ mA} + \frac{V_Z}{R_{L \min}} \Rightarrow \frac{V_Z}{R_{L \min}} = 65 \text{ mA}$$

$$R_{L \min} = \frac{9}{65} = 138.46 \Omega$$

for $(R_L)_{\max}$:-

$$i_S = i_{Z \max} + i_{L \min}$$

\therefore Supply current is constant = 75 mA and Zener can allow current = 100 mA. Hence total current will flow through Zener diode only.

$$\text{So, } i_{L \min} = 0 \text{ A} \Rightarrow R_{L \max} = \infty$$

$$\text{Range of } R_L = 138.46 \Omega \text{ to } \infty$$

(b) Find the range of supply voltage V_S that result in a 9V load voltage when $R_L = 600 \Omega$.

$$(I_L)_{\text{constant}} = \frac{(V_L)_{\text{constant}}}{(R_L)_{\text{constant}}} = \frac{9}{600} = 15 \text{ mA}$$

$$\frac{(V_s)_{\min} - V_Z}{R} = (I_Z)_{\min} + I_L$$

$$\frac{(V_s)_{\min} - 9}{0.2} = 10 + 15 = 25$$

$$\Rightarrow \boxed{(V_s)_{\min} = 14V}$$

$$\frac{(V_s)_{\max} - V_Z}{R} = (I_Z)_{\max} + I_L$$


$$\frac{(V_s)_{\max} - 9}{0.2} = 100 + 15 = 115$$

$$\boxed{(V_s)_{\max} = 32V}$$

Range $\boxed{14V \leq V_s \leq 32V}$

Ans 27 Given - $V_{CC} = V_{EE} = 5V$, $I_E = 5mA$, $V_{CB} = -2V$.
 $R_E, R_C = ?$

Solⁿ:-

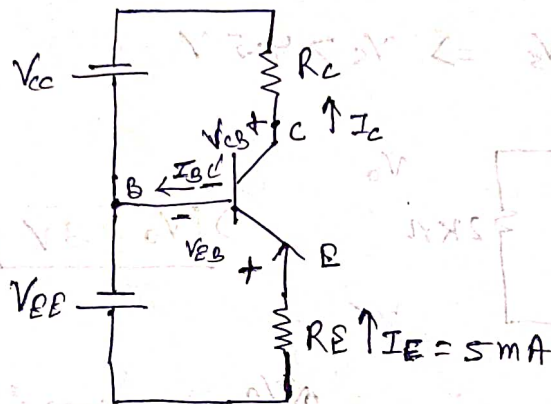

For BJT in Active region $V_{EB} \approx 0.7V$

Assume β is large So, $I_E \approx I_C = 5mA$

$$V_{CC} + V_{CB} = I_C R_C \quad \text{--- (i)}$$

$$I_E R_E + V_{EB} = V_{EE} \quad \text{--- (ii)}$$

$$5mA \times R_E = 5 - 0.7 \Rightarrow R_E = \frac{4.3}{5mA} = 0.86 k\Omega$$


from eqⁿ (i) -

$$5 - 2 = I_C R_C$$

$$R_C = \frac{3}{5} = 0.6 k\Omega$$

$$\text{So } \boxed{R_E = 860\Omega, R_C = 600\Omega}$$

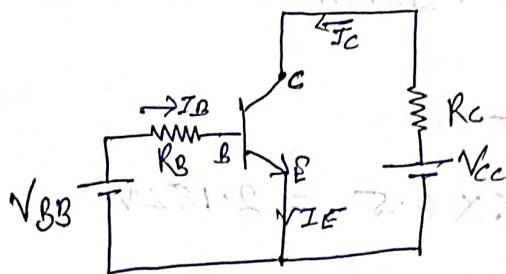Q4) Given - $R_B = 270\text{K}\Omega$, $V_{BB} = V_{CC} = 6\text{V}$, $\beta = 120$



Solⁿ:- Assuming BJT to be in active region when $R_C = 3\text{K}\Omega$

As B-E junction is forward bias, we can assume $V_{BE} \approx 0.7\text{V}$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{6 - 0.7}{270\text{K}} = 0.01963\text{mA}$$

$$I_C = \beta I_B = 120 \times 0.01963 = 2.3556\text{mA}$$


$$V_{CE} = V_{CC} - I_C R_C = 6 - 2.3556 \times 3 = -1.0668\text{V}$$

$$V_{BC} = V_{BE} - V_{CE} = 0.7 - (-1.0668) = 1.7668\text{V}$$

• BC junction is F.B, hence our assumption is not correct.

• BJT is not in active region, when $R_C = 3\text{K}\Omega$.

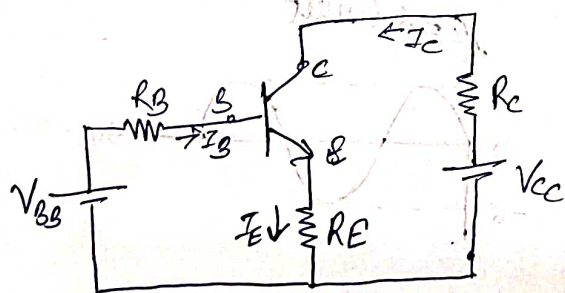Q5) Given - $R_E = 500\Omega$ ~~$R_C = 3\text{K}\Omega$~~



(i) Assuming BJT in active region, $V_{BE} \approx 0.7\text{V}$

$$V_{BB} - I_B R_B - 0.7 - I_E R_E = 0$$

$$I_E = I_C + I_B = (1 + \beta) I_B$$

$$I_B \cancel{R_E} \quad V_{BB} - 0.7 = I_B R_B + (1 + \beta) I_B R_E$$

$$I_B = \frac{6 - 0.7}{R_B + (1 + \beta) R_E} \approx 0.016\text{mA}$$

$$I_c = \beta I_B = 120 \times 0.016 = 1.92 \text{ mA}$$

$$V_{CE} = V_{CC} - I_c R_c - I_E R_E$$

$$V_{CE} = 6 - 1.92 \times 1.5 - 1.936 \times 0.5 = 2.152 \text{ V}$$

* B-E Junction in F.B and BC junction in R.B.

* BJT is operating in active region

(ii) when $R_c = 3 \text{ k}\Omega$, and assuming BJT is operating in active region.

$$V_{CE} = V_{CC} - I_c R_c - I_E R_E = -0.728 \text{ V}$$

• Our assumption is wrong

• BJT will not be operating in active region for $R_c = 3 \text{ k}\Omega$.