


EE 101: Introduction to Electrical and Electronic Circuits, 2019

Midsem


(Show all the steps in the solution properly. Weightage=24%)

1) Consider a piece of Si doped with certain impurities, at 300 K. It was found that the hole concentration is $2.25 \times 10^4 / \text{cm}^3$. Find out the impurity concentration. The impurity belongs to which group of the periodic table (III or V)? Is it p type or n type semiconductor? Assuming that mobility of electrons is $1300 \text{ cm}^2/\text{Vs}$ and holes is $500 \text{ cm}^2/\text{Vs}$, find out the resistivity of doped Si. [4 marks]

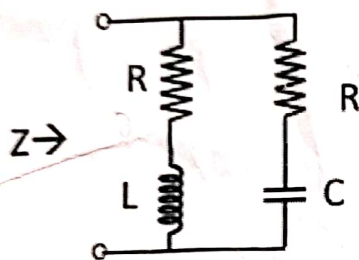
2) The impedance of the circuit shown below is found to be $2 \text{ k}\Omega$ (real) at all frequencies. If the value of inductor is 1 mH , find out the values of R and C . [5 marks]



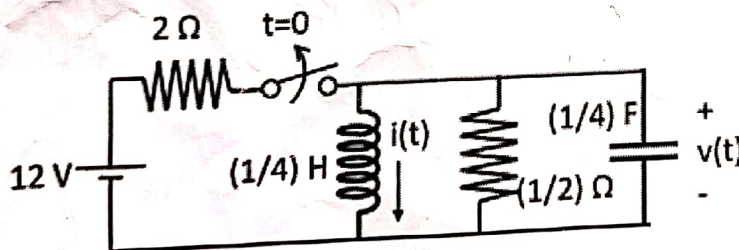3) For the circuit shown below, the switch opens at $t=0$. Find out and sketch $v(t)$ and $i(t)$, for $t=0$ to $t=\infty$. [6 marks]



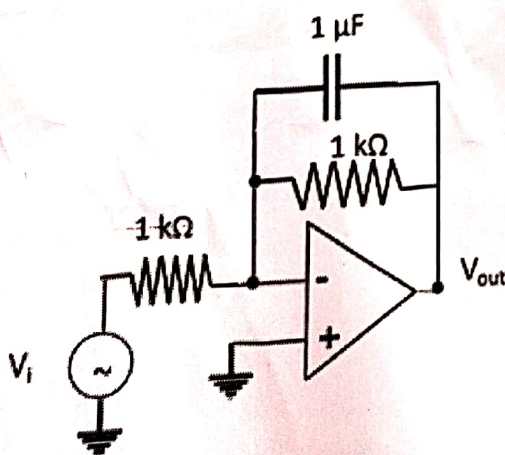4) Consider the op-amp circuit shown below. Find out the transfer function $H(\omega)$. ($H = V_{\text{out}}/V_i$). Plot the real and imaginary parts of H as a function of ω . [4 marks]



5) Consider an op-amp circuit shown below. Assume $R_1=10\text{ k}\Omega$, $R_2=20\text{ k}\Omega$, reference voltage $V_r=6\text{ V}$ and $V_{CC}=12\text{ V}$. Find out and plot the complete transfer characteristics (i.e. V_o as a function of V_i) . [5 marks]

