
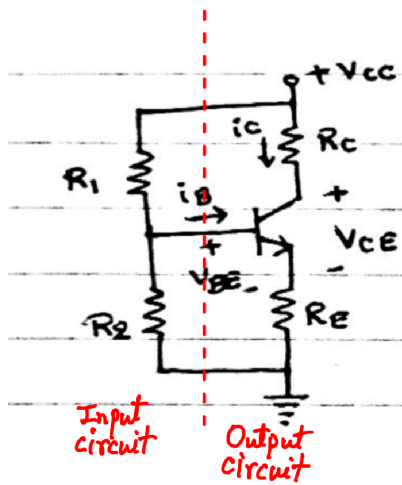


# Tutorial 11 Solution

Q.1

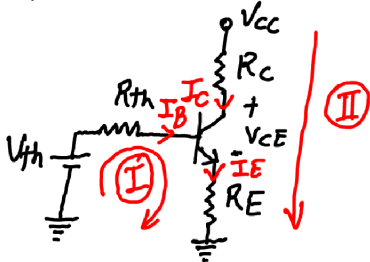

∴ The equivalent circuit becomes



∴  $I_{CQ} = 2\text{mA}$  and  $h_{FE} = 100$

∴  $I_B = \frac{I_{CQ}}{h_{FE}} = 20\mu\text{A}$

For loop (I), Applying KVL

$$V_{th} - I_B R_{th} - V_{BE} - I_E R_E = 0$$

$$\therefore V_{BE} = 0.8\text{eV and } I_E = (\beta + 1) I_B$$


$$\therefore V_{th} - I_B (R_{th} + (\beta + 1) R_E) - 0.8 = 0$$

$$\therefore R_E = \frac{V_{th} - 0.8 - R_{th}}{I_B (\beta + 1)} = \frac{5 - 0.8 - 13\text{k}\Omega}{20 \times 10^{-6} \times 101}$$

$$\therefore R_E \approx 1950.5\Omega \approx 1.9505\text{k}\Omega$$

Given :  $h_{FE} = 100 (\beta)$  ;  $R_1 = R_2 = 26\text{k}\Omega$  ;  $V_{CC} = 10\text{V}$   
Find  $R_C$  and  $R_E$  such that  $I_{CQ} = 2\text{mA}$  ;  $V_{CEQ} = 4\text{V}$   
and BJT is biased in active region

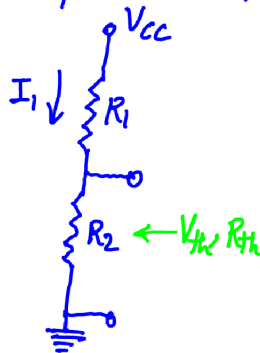For input circuit, finding Thevenin's equivalent circuit



For  $V_{th}$ , applying KVL in the circuit

$$V_{CC} - I_1 R_1 - I_1 R_2 = 0$$

$$\therefore I_1 = \frac{V_{CC}}{R_1 + R_2}$$

$$\therefore V_{th} = I_1 R_2 = \frac{V_{CC} R_2}{R_1 + R_2} = \frac{10 \times 26}{26 + 26} = 5\text{V}$$

For  $R_{th}$ , grounding voltage source

$$\therefore R_{th} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{26^2}{2 \times 26}$$

$$\therefore R_{th} = 0.5 R_1 = 13\text{k}\Omega$$

For loop (II), Applying KVL

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$\therefore I_E = \frac{\beta + 1}{\beta} I_C = 1.01 I_C$$


$$\therefore 10 - 2 \times 10^{-3} R_C - 4 - 1.01 \times 2 \times 10^{-3} \times 1950.5 = 0$$

$$\therefore 2 \times 10^{-3} R_C = 10 - 4 - 3.94 = 2.06$$


$$\therefore R_C = \frac{2.06}{2 \times 10^{-3}} \Omega = 1.03\text{k}\Omega$$

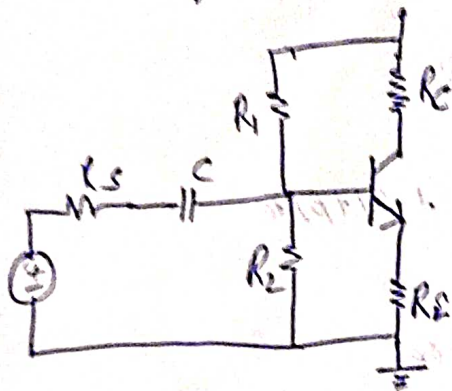6.2) Given -  $h_{FE} = h_{FE} = 100$ ,  $R_1 = R_2 = 26K\Omega$ ,  $R_E = 980\Omega$

$R_E = 2K\Omega$  and  $V_{CC} = 10V$   
 find (a)  $g_m$  (b)  $r_e$  (c)  $R_{in}$  (d)  $A_v$



for DC analysis - capacitor is open -

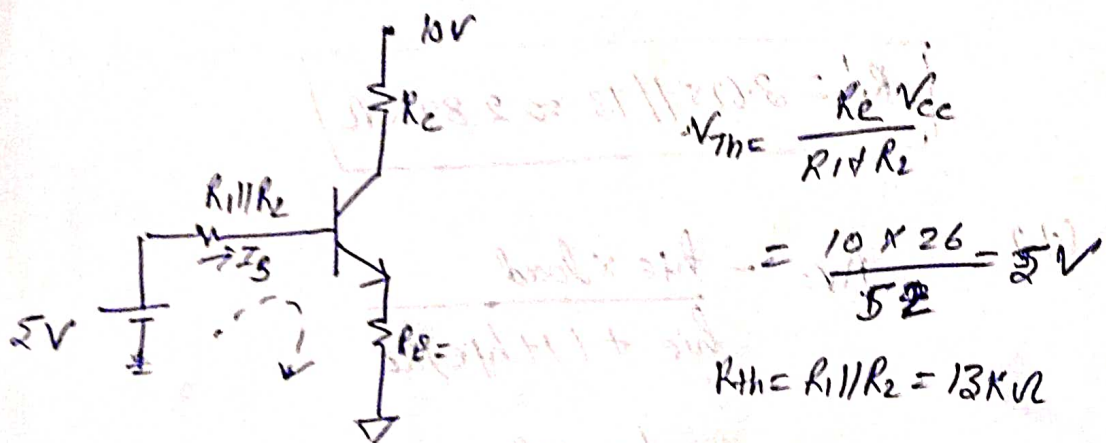

$$(9) g_m = \frac{I_C}{V_T}$$

KVL at input -  $\frac{10V}{2} = \frac{26}{52} - 5V$

$$5 - 13I_B - 0.7 - 2(1 + h_{FE})I_B = 0$$

$$4.3 = 13I_B + 202I_B$$

$$I_B = 0.02 \text{ mA}$$

$$I_C = \beta I_B = 2 \text{ mA}$$

$$g_m = \frac{2 \text{ mA}}{25 \text{ mV}} = 80 \text{ mS}$$

(b)  $r_e$  (from T-model)

$$r_e = \frac{1}{g_m} = 12.5 \Omega$$

(c) Input resistance with  $R_E$

$$R_i = h_{ie} + (1 + \beta)R_E + (1 + \beta)r_e$$

$$R_i \approx (1 + \beta)R_E + (1 + \beta)r_e$$

$$= 101 \times 2K + 101 \times 12.5$$

$$R_i = 2.2625 K\Omega$$

$$R_i' = 2.625 // 12 \approx 2.89 K\Omega$$

(d)  $A_v = - \frac{h_{fe} \times \text{load}}{h_{ie} + (1 + h_{fe})R_E}$

$$\approx - \frac{h_{fe} \times R_C}{(1 + h_{fe})R_E}$$

$$A_v \approx - \frac{R_C}{R_E} = \frac{2K\Omega}{980\Omega}$$


$$A_v \approx -2$$

$$A_{v_{mid}} = 0.5 \times 2 = 1$$

$$A_{v_{mid}} = 0.5 \times 2 = 1$$


$$f_{mid} = \frac{A_{v_{mid}}}{20} = \frac{1}{20} = 0.05$$

⇒

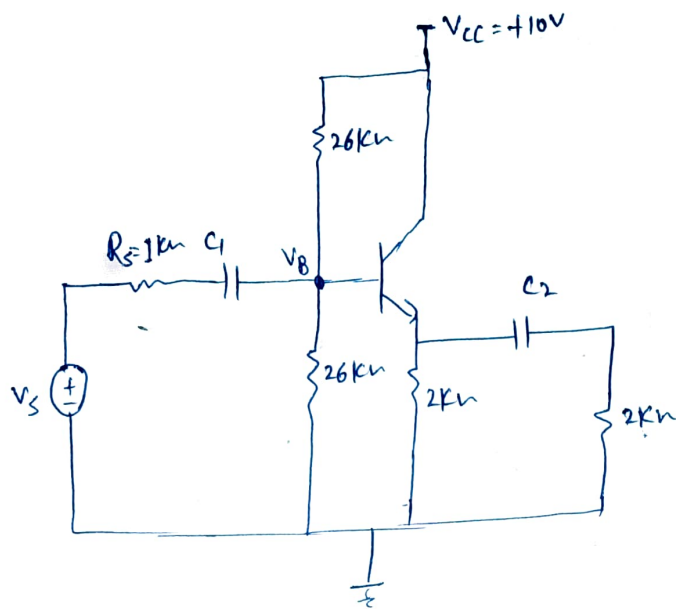

⇒ DC Analysis :

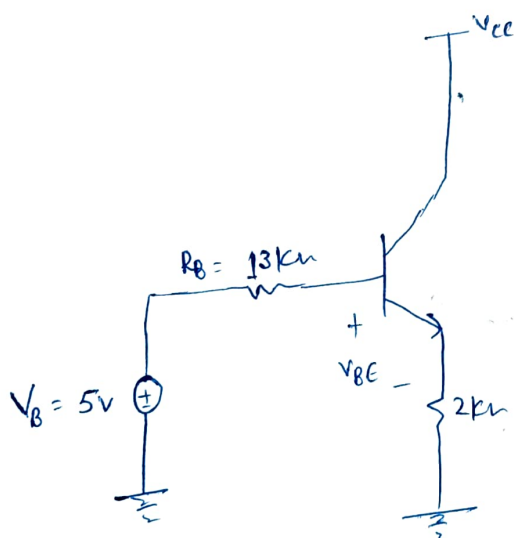Thevenin equivalent ckt : [Capacitors → O.C.]



$$\left[ \begin{aligned} V_B &= \frac{10}{26K + 26K} \times 26K = 5V \\ R_B &= R_1 \parallel R_2 = 26K \parallel 26K = 13K \end{aligned} \right]$$

By applying KVL @ i/p loop -

$$-5 + 13K \times I_B + V_{BE} + (I_C + I_B) \times 2K = 0$$


$$I_B = \frac{4.3}{215K}$$

$$I_C = I_B \times h_{fe} = 100 \times \frac{4.3}{215K} = 2mA$$




$$r_e = \frac{\eta V_T}{I_C} \approx \frac{26 \text{ mV}}{2 \text{ mA}} \approx 13 \Omega$$

⇒ Small Signal Model :-

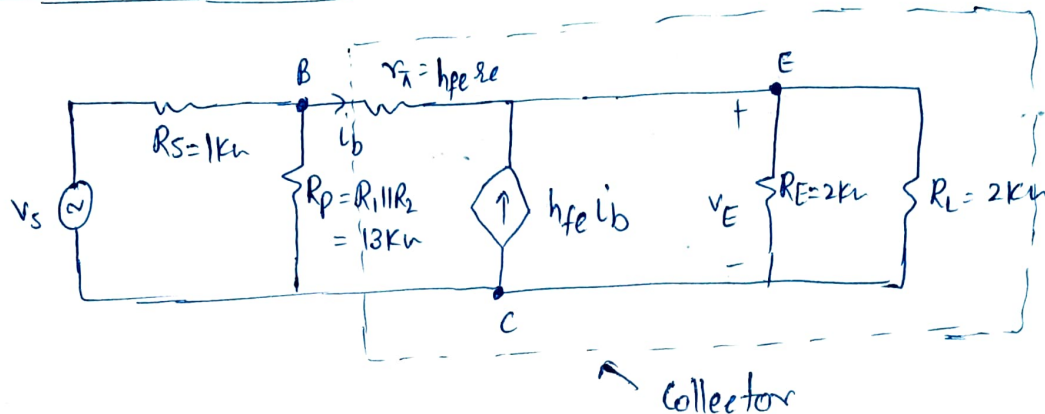

→ input resistance :

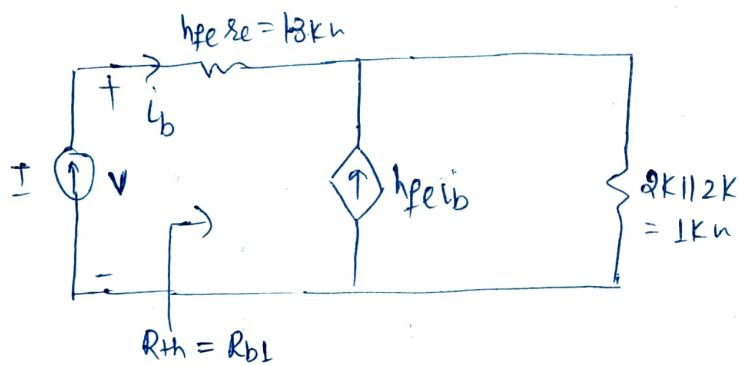


$$v = 1.3 \text{ K} \times i_b + 1 \text{ K} \times (1 + h_{fe}) i_b$$

$$R_{th} = \frac{v}{i_b} = 1.3 \text{ K} + 101 \text{ K} \quad [i_b = I]$$

$$R_{b1} = R_{th} = 102.3 \text{ K}$$

Now, Total i/p resistance from source -

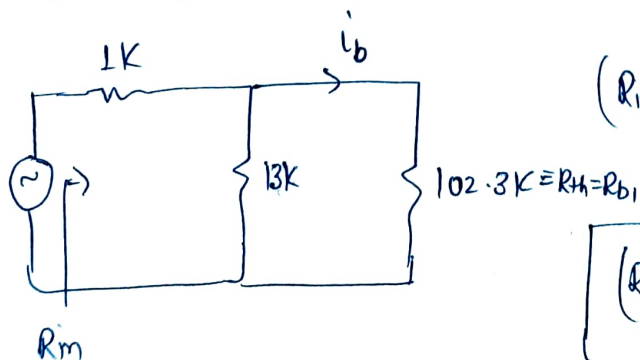

$$(R_m)_{total} = 1 \text{ K} + (13 \text{ K} || 102.3 \text{ K})$$

$$= 1 \text{ K} + 11.53 \text{ K}$$

$$(R_m)_{total} \approx 12.5 \text{ K}$$

$\Rightarrow$  Ac voltage gain -  $A_v = \frac{V_e}{V_b} = ?$

$$V_e = (1 + h_{fe}) i_b \times (R_E \parallel R_L)$$

$$V_e = 101 \times 1K i_b$$



And  $V_b = i_b \times R_{Th} = i_b \times R_{b1}$

$$\text{so, } V_e = \frac{101 \times 1K \times V_b}{R_{Th}}$$

$$\frac{V_e}{V_b} = \frac{101K}{102.3K}$$

$$\boxed{\frac{V_e}{V_b} = 0.987 \approx 1}$$

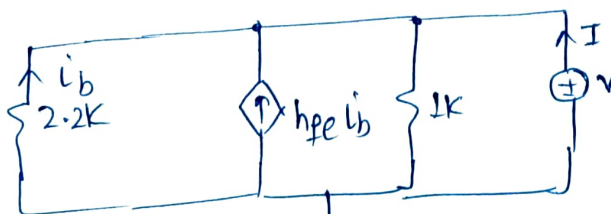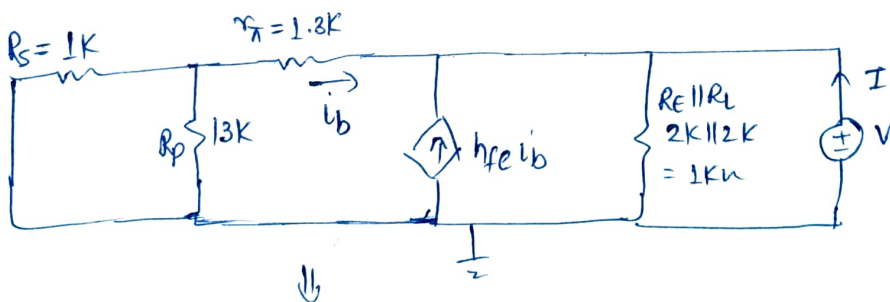$\Rightarrow$  Output resistance  $R_o$  :- [ $V_s \rightarrow$  S.C.]



$$\frac{V}{2.2K} + \frac{V}{1K} = I + h_{fe} i_b \quad \left[ i_b = \frac{-V_o}{2.2K} \right]$$

$$\frac{(1 + 2.2)V}{2.2K} = \frac{2.2KI + h_{fe}(-V_o)}{2.2K}$$

So,

$$\frac{V}{I} = \frac{22K}{103.2} = 22\Omega = R_{out}$$