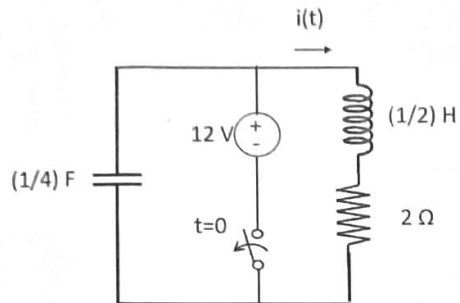


EE 101: Introduction to Electrical and Electronic Circuits, 2018


Endsem

(Show all the steps in the solution properly. Weightage=50 %)

- 1) The switch in the circuit below was closed for a long time and opened at $t=0$. Find $i(t)$ for $t>0$. [6 marks]



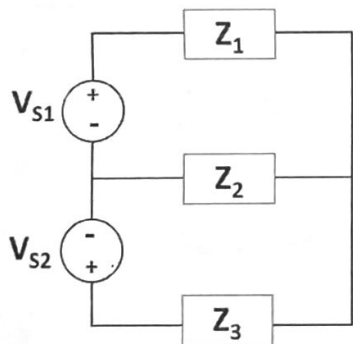- 2) For the circuit shown below, $V_{S1}=2\cos(\omega t)$ and $V_{S2}=2\sin(\omega t)$, where $\omega=10$ rad/s. Find out the average power absorbed by each element in the circuit (including power sources). Assume $Z_1=Z_2=Z_3=10-10j \Omega$. [6 marks]



- 3) For the oscillator circuit shown below, assume that the op-amp is ideal. Find out the frequency of oscillation. Find out the minimum value of R for which oscillations occurs. [7 marks]

