

①


$$V_{rms} = 220 \text{ V}, f = 60 \text{ Hz}, I_{rms} = 20 \text{ A}$$

$$Pf = 0.75 \text{ (lagging)} = \cos \phi$$

$$\phi = \cos^{-1}(0.75) = 41.40^\circ$$

$$\begin{aligned} \text{a) Average power absorbed} &= V_{rms} \times I_{rms} \times \cos \phi \\ &= 220 \times 20 \times 0.75 \\ &= 3.3 \text{ kW} \end{aligned}$$

b)

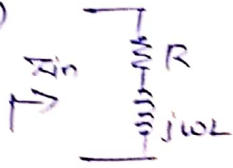

$$\begin{aligned} Z_{in} &= R + j\omega L = \left| \frac{V_{rms}}{I_{rms}} \right| \angle \phi \\ &= \left| \frac{220}{20} \right| \angle 41.40^\circ \\ &= 11 \angle 41.40^\circ \end{aligned}$$


$$R + j\omega L = 8.25 + j7.27$$

Comparing on both sides

$$R = 8.25 \Omega$$

$$\omega L = 7.27 \Omega$$
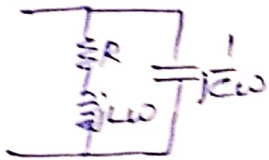
$$L = \frac{7.27}{2\pi f} = \frac{7.27}{2\pi \times 60} = 19.3 \text{ mH}$$



If Pf is unity, impedance looking into input terminals is purely resistive

$$Y = \frac{1}{R + j\omega L} + j\omega C$$

$$= \frac{R - j\omega L}{R^2 + (\omega L)^2} + j\omega C = \frac{R}{R^2 + (\omega L)^2} + j \left( \frac{\omega C - \omega L}{R^2 + (\omega L)^2} \right)$$

equating imaginary part to zero,


$$\omega C = \frac{\omega L}{R^2 + \omega^2 L^2}$$

$$R^2 + \omega^2 L^2 = 14$$


$$C = \frac{19.3 \times 10^{-3}}{(8.25)^2 + (2\pi \times 60)^2 (19.3 \times 10^{-3})^2}$$

$$\therefore C = 0.135 \mu\text{F}$$

②  
a)

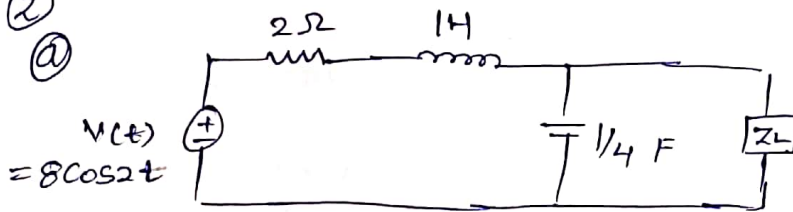

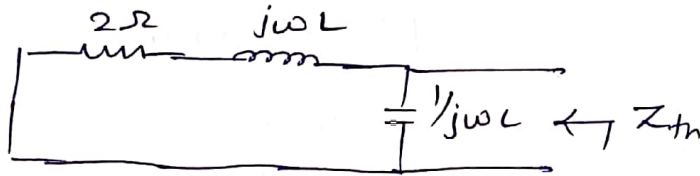~~Deleting~~ Evaluating thevenin equivalent impedance of the circuit by disconnecting the load and shorting the voltage source



$$Z_{th} = (2 + j\omega L) \parallel \frac{1}{j\omega C}$$

$$= (2 + j\omega) \parallel \frac{1}{j\omega}$$


$$= (2 + j2) \parallel \frac{2}{j} = \frac{(2 + j2)(-2j)}{2 + j2 - 2j} = -2j + 2$$

For maximum power transfer,  $Z_L = Z_{th}^*$

$$\therefore Z_L = 2 + 2j$$

③ for maximum power transfer  
 $R_L = \sqrt{2^2 + 2^2} = 2\sqrt{2} \Omega$

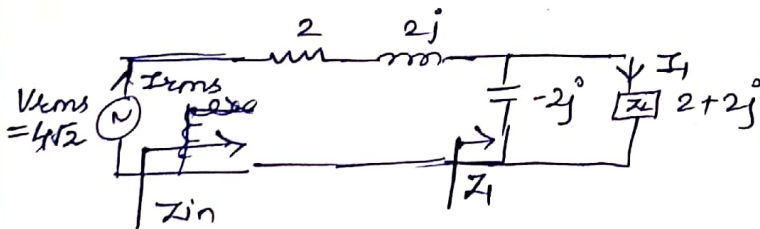lets calculate maximum power absorbed by  $R_L$



$$Z_1 = \frac{(-2j)(2 + 2j)}{2 + 2j - 2j} = -2j + 2$$

$$Z_{in} = 2 + 2j + Z_1 = 2 + 2j - 2j + 2 = 4$$


$$I_{rms} = \frac{V_{rms}}{Z_{in}} = \frac{4/\sqrt{2}}{4} = \sqrt{2} \text{ A}$$

$$I_1 = \sqrt{2} \times \frac{(-2j)}{(2 + 2j - 2j)} = -\sqrt{2}j = \sqrt{2} \angle -90^\circ$$

power absorbed by resistive load is

$$P_{abs} = I_1^2 \times R_L$$
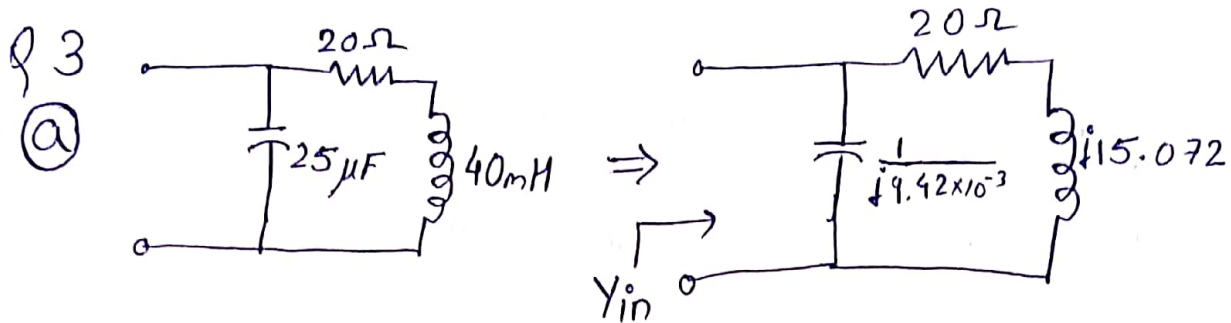
$$= (\sqrt{2})^2 \times 2 = 4 \text{ W}$$



$$Y_{in} = j 9.42 \times 10^{-3} + \frac{1}{20 + j 15.072}$$

$$\Rightarrow Y_{in} = j 9.42 \times 10^{-3} + \frac{20 - j 15.072}{400 + 227.16}$$

$$\Rightarrow Y_{in} = j 9.42 \times 10^{-3} + \frac{20}{627.16} - j \frac{15.072}{627.16} \Rightarrow \frac{20}{627.16} + j \left( 9.42 \times 10^{-3} - \frac{15.072}{627.16} \right)$$

$$\Rightarrow Y_{in} = 31.89 \times 10^{-3} + j(-14.61 \times 10^{-3})$$


Now, Power factor angle  $\phi = \tan^{-1} \left( \frac{-14.61}{31.89} \right) = \underline{\underline{-24.61^\circ}}$

So, Power factor  $\Rightarrow \cos \phi = \cos(-24.61) = \underline{\underline{0.9091}}$

Q 3

(b) For  $Y_{in} = \frac{I}{V}$ , Power factor angle is coming out to be  $-24.61^\circ$ , which suggests that current is lagging behind voltage by  $24.61^\circ$ .

Q3 (C)

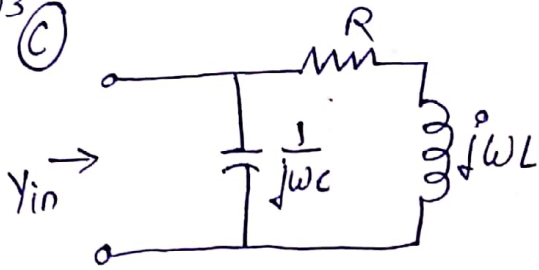

$$\begin{aligned}
 \Rightarrow Y_{in} &= j\omega C + \frac{1}{R + j\omega L} \\
 &= j\omega C + \frac{R - j\omega L}{R^2 + (\omega L)^2} \\
 &= j\left(\omega C - \frac{\omega L}{R^2 + (\omega L)^2}\right) + \frac{R}{R^2 + (\omega L)^2}
 \end{aligned}$$

Now, for Power factor to be '1', circuit should be Purely resistive.

$\therefore$  equating imaginary Part to '0'

$$\Rightarrow \omega C - \frac{\omega L}{R^2 + (\omega L)^2} = 0 \Rightarrow C = \frac{L}{R^2 + (\omega L)^2}$$

$$C = \frac{40 \times 10^{-3}}{(20)^2 + (60 \times 40 \times 10^{-3})^2} \Rightarrow \boxed{C = 96.36 \mu F}$$

Q5

a)

$$V(t) + \int V dt = 10 \cos t$$

taking derivative on both sides

$$\Rightarrow \dot{V}(t) + V(t) = -10 \sin t$$

Converting it into phasor form,

$$\cancel{V(t)} \times \cancel{(1+j\omega)} \times \cancel{e^{j\omega t}} = \cancel{10} \times \cancel{e^{j\omega t}}$$

$$\text{let } x(t) = -10 \sin t$$

$$\Rightarrow \dot{V}(t) + V(t) = x(t)$$

Converting to Phasor form

$$(j\omega + 1)V(\omega) = x(\omega)$$

$$\frac{V(\omega)}{x(\omega)} = f(\omega) = \frac{1}{1+j\omega}, \text{ } \because \omega = 1 \Rightarrow f(\omega) = \frac{1}{1+j}$$

$$\text{Now, } |f(\omega)| = \frac{1}{\sqrt{2}} \text{ \& } \angle f(\omega) = -45^\circ$$

as i/p is sinusoidal, we can directly multiply  $|f(\omega)|$  with magnitude of sinusoid & add their phases.

$$\Rightarrow V(t) = -10 \times \left(\frac{1}{\sqrt{2}}\right) \sin(t - 45^\circ)$$

$$\boxed{V(t) = 5\sqrt{2} \sin(t - 225^\circ)}$$

b)

$$\frac{dV(t)}{dt} + 5V(t) + 4 \int V(t) dt = 20 \sin(4t + 10^\circ)$$

taking derivative on both sides

$$\Rightarrow \dot{V}(t) + 5\dot{V}(t) + 4V(t) = +80 \cos(4t + 10^\circ)$$

Converting to Phasor form.

$$\Rightarrow V(\omega) [(j\omega)^2 + 5j\omega + 4] = x(\omega)$$

$$\Rightarrow \frac{V(\omega)}{x(\omega)} = \frac{1}{[(j\omega)^2 + 5j\omega + 4]} = \frac{1}{(1+j\omega)(1+4j\omega)}$$



After applying Partial fraction

$$\frac{V(\omega)}{X(\omega)} = \frac{-1}{3(1+j\omega)} + \frac{4}{3(1+j4\omega)}$$

$$\omega = 4 \Rightarrow \frac{V(\omega)}{X(\omega)} = \frac{-1}{3(1+j4)} + \frac{4}{3(1+j16)} = \frac{+1}{3} \times \frac{1 \angle 180^\circ}{4.123 \angle 75.96^\circ} + \frac{4}{3} \times \frac{1}{16.03 \angle 86.42^\circ}$$

$$\frac{V(\omega)}{X(\omega)} = 80.84 \times 10^{-3} \angle 104.04^\circ + 83.17 \times 10^{-3} \angle -86.42^\circ$$

$$\Rightarrow \frac{V(\omega)}{X(\omega)} = -0.0196 + j0.0784 + 5.19 \times 10^{-3} - j0.083$$

$$\Rightarrow \frac{V(\omega)}{X(\omega)} = -0.01441 + j4.6 \times 10^{-3} \\ = 0.0151 \angle -162.3^\circ$$

using same procedure as described in Q5@

$$v(t) = 20(0.0151) \sin(4t + 10^\circ - 162.3^\circ)$$

$$\boxed{v(t) = 0.302 \sin(4t - 152.3^\circ)}$$